
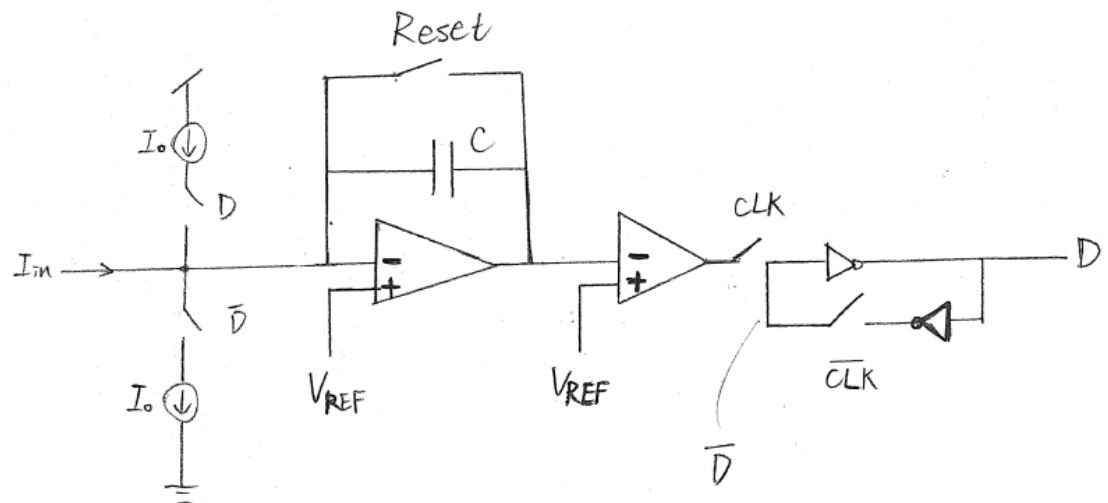


ESE 562_Project 3

Po Hsu Chen, 448031

System level architecture with component values (C, I_o, CLK, V_{REF}, V_{CMP})

V_{dd} = 3V

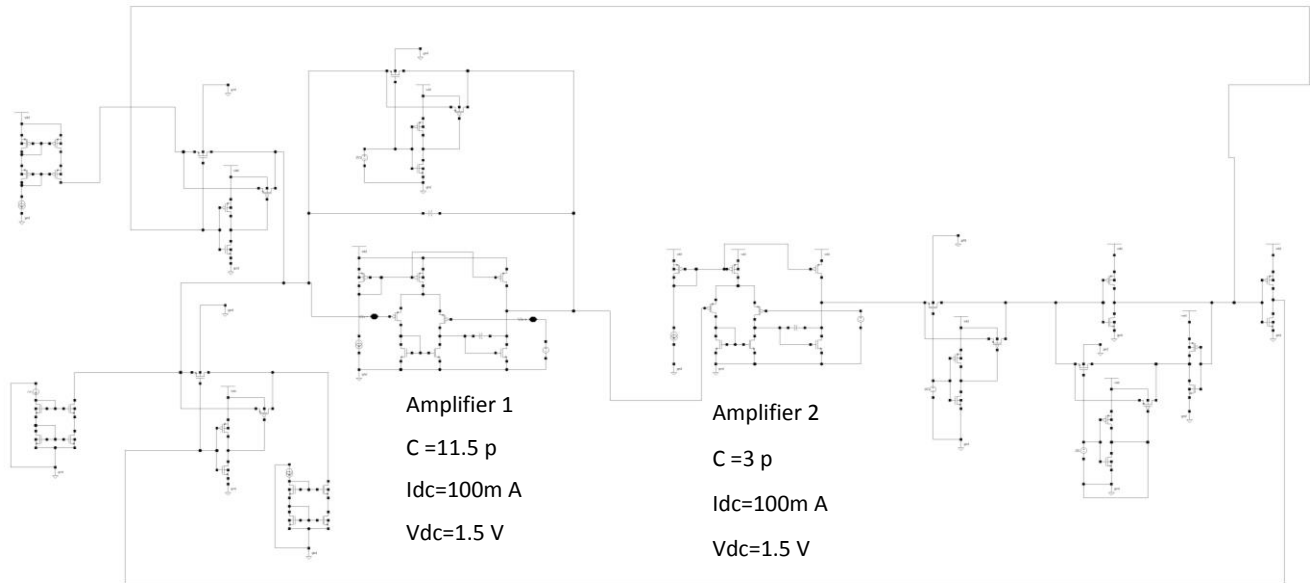


C	I _o	CLK	V _{ref}	V _{CMP}
3p	130n A	V pulse 0 ~ 3V (3~0V)	1.5 V	1.5 V
		Pulse width 20u s		
		Period 40u s		


Amplifier Implementation

I chose the amplifier as the one in project 1.

Amplifier 1.

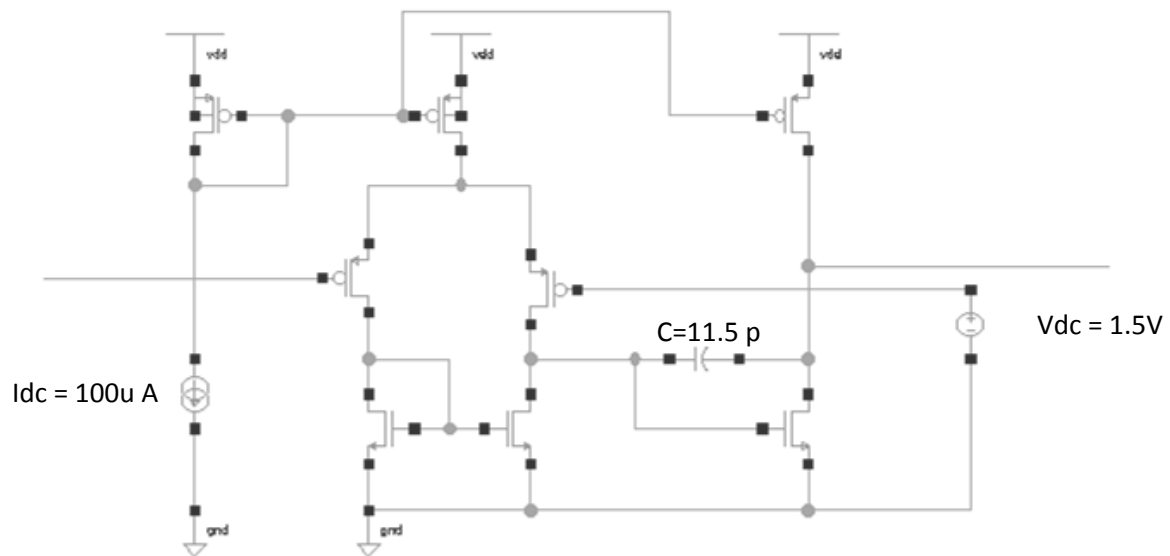


Amplifier 2.


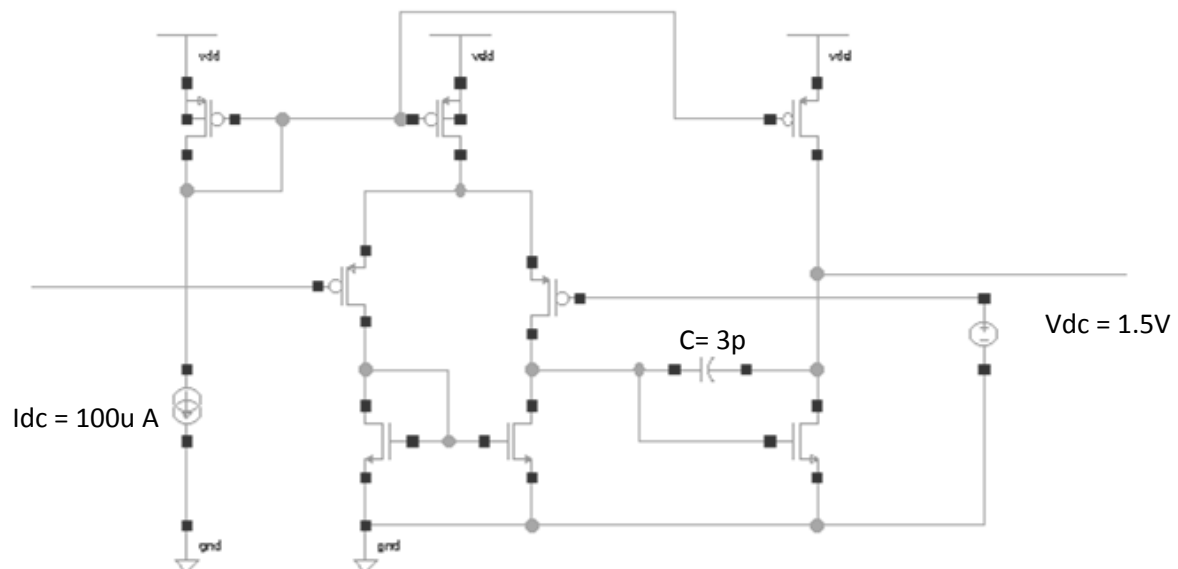


Implementation



Current Source and Sink

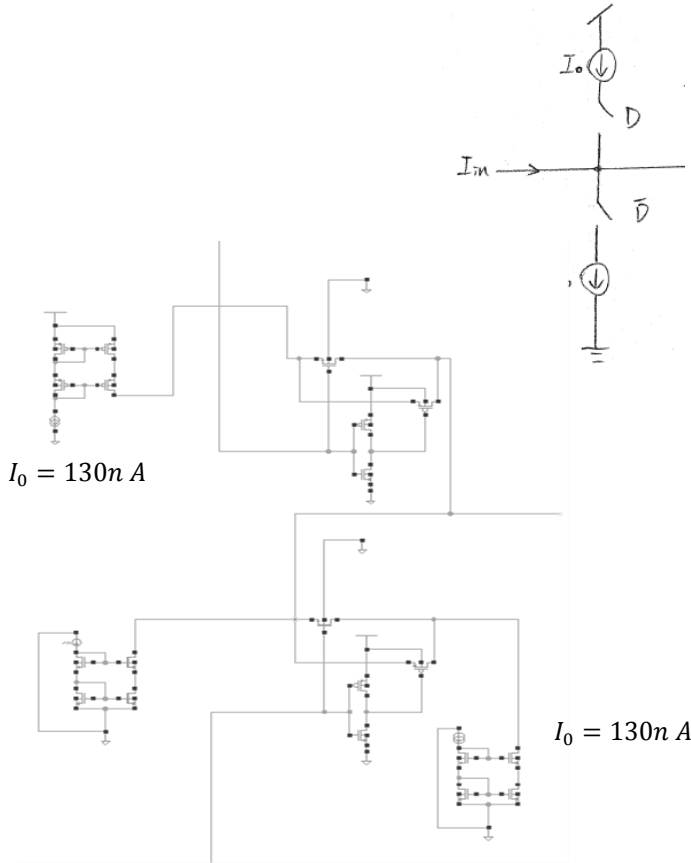

CMOS Switch

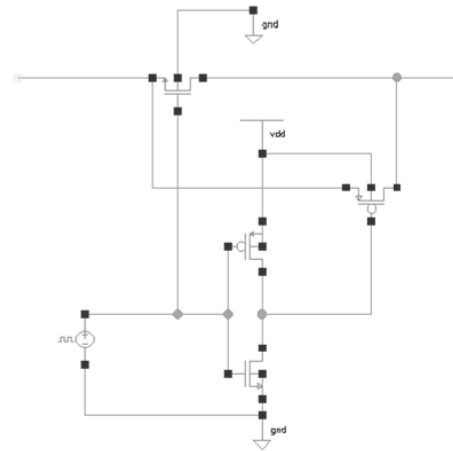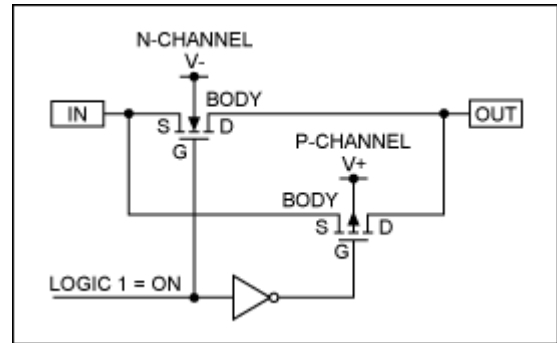


Latched Comparator

 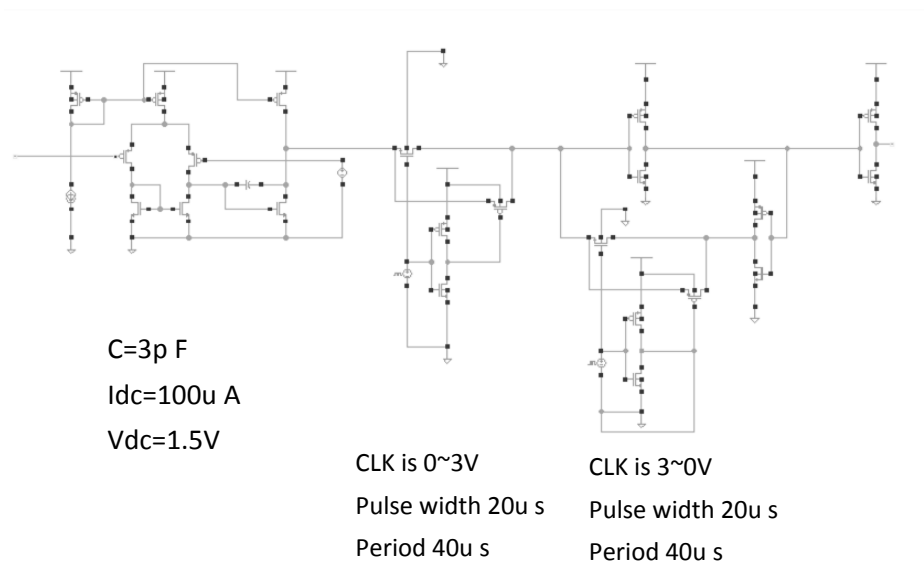


Output of the modulator and voltage V_x


I_{in}

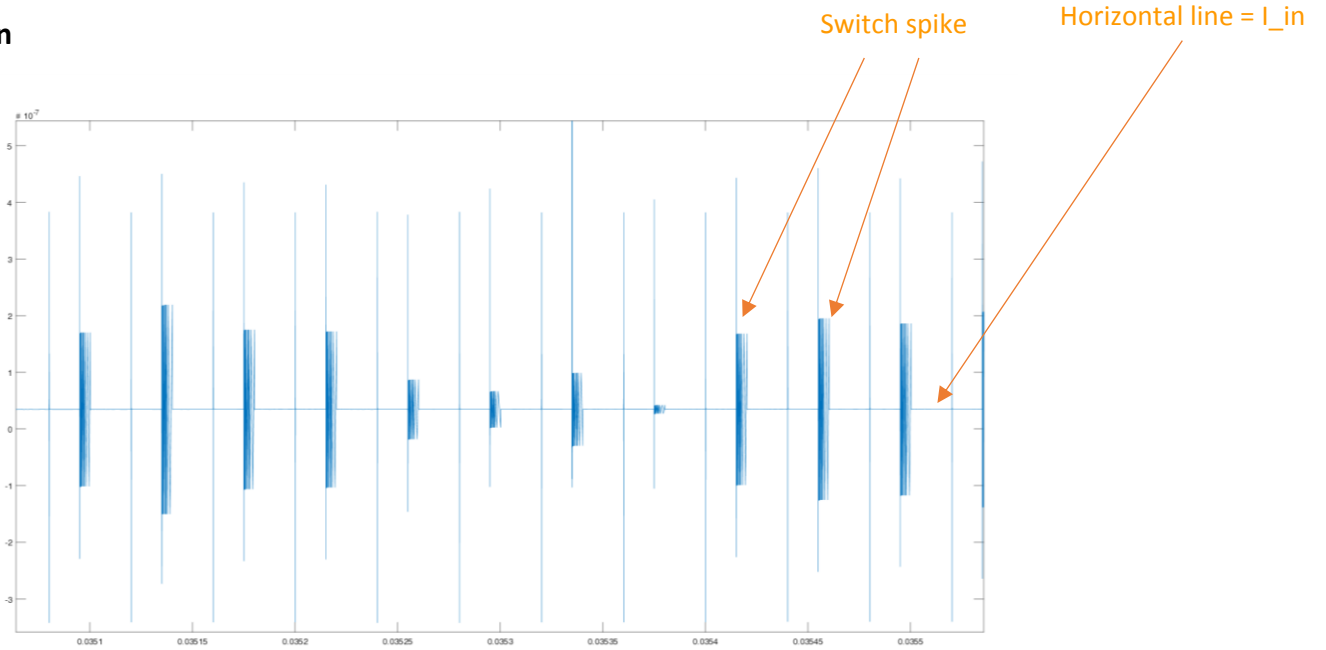



V_{reset} :

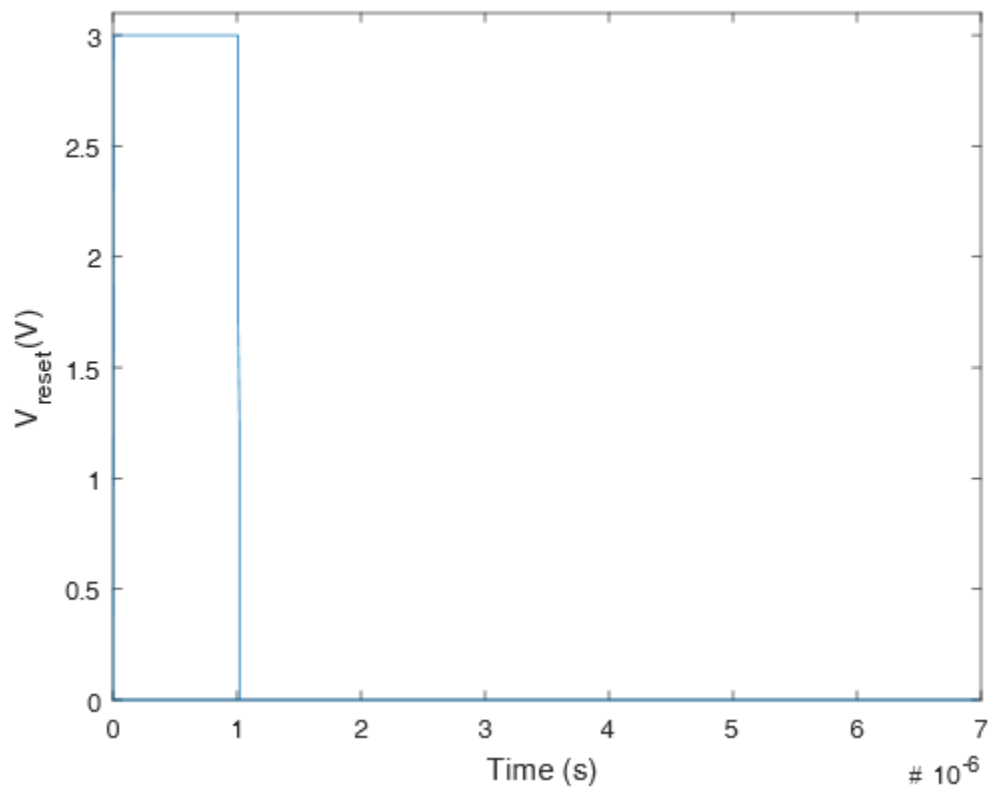

V_x

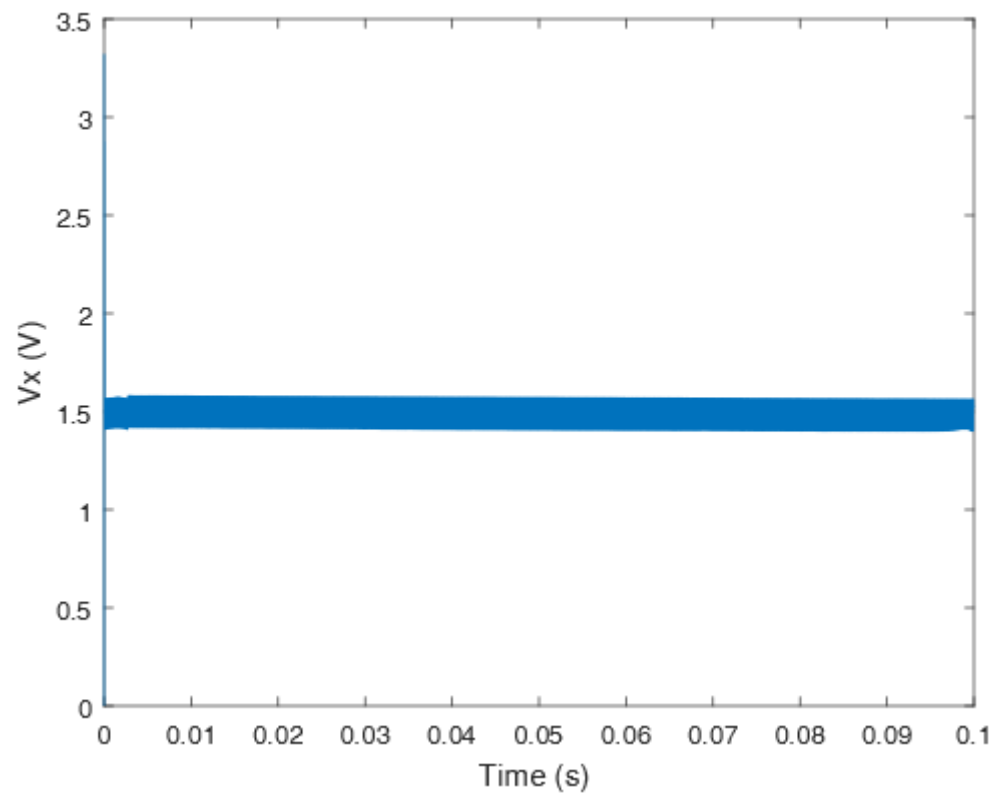

V_{Dn} and Duty Cycle

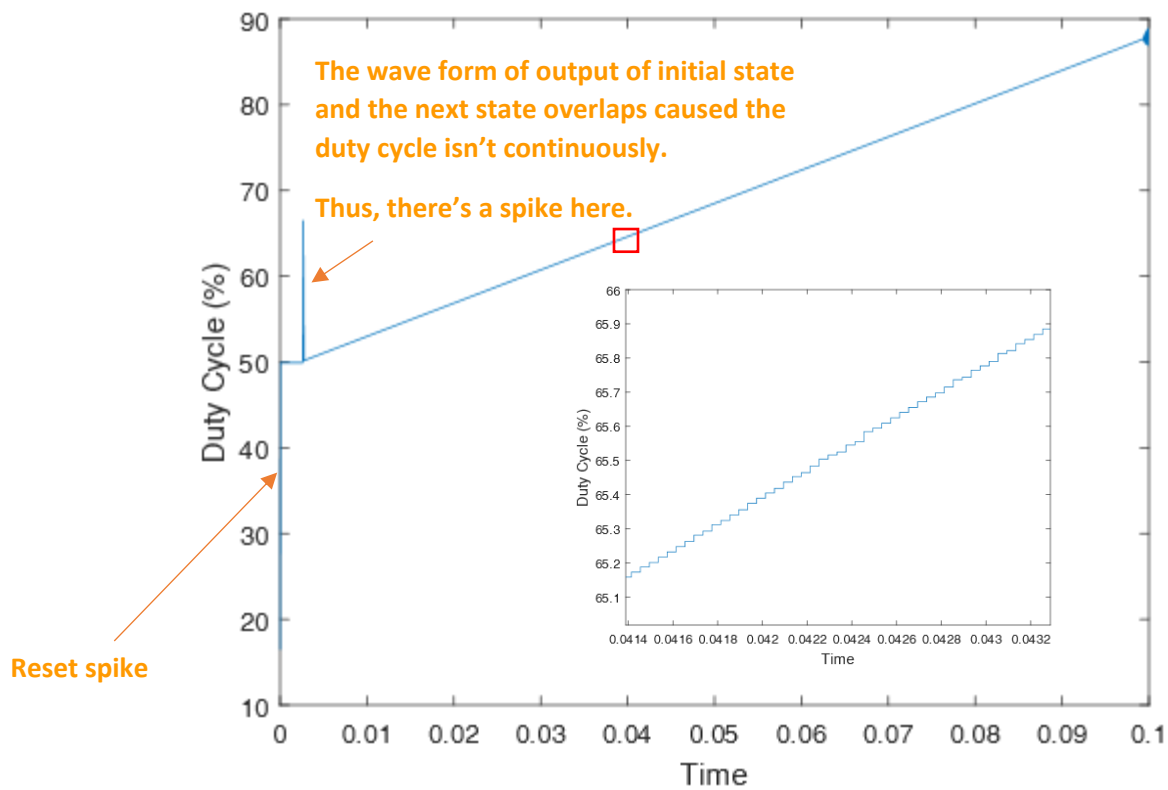 

Speed:

CLK is 0~3V and 3~0V

Pulse width 20u s

Period 40u s

Resolution:

Since there are 2410 data points in duty cycle.

$$\log_2 2410 = 11.2348174$$

=>The resolution is 11.2 bit.

Power Dissipation:

$$P = I * V$$

$$P = 399 \mu A * 3 V = 1.2 m Watt$$