




Power Dissipation



CSE562: Analog Integrated Circuits

Shantanu Chakrabartty

 


Power dissipation in basic circuits




- Power dissipation Resistor

$$P_{diss} = V.I = I^2 R = V^2 / R$$

 

- Energy stored in a capacitor


 
$$E_{stored} = \frac{1}{2} C V^2 = \frac{Q^2}{2C}$$



- Energy dissipated in a generic system

$$P_{diss} = \sum_{i=1}^N \text{Re}\{V_i I_i\}$$

Power dissipation

  

- Power dissipation occurs only when voltage and current are in phase.


$$E_{diss} = \int_0^{\infty} \frac{1}{R} [V - V_x(t)]^2 dt$$

$$E_{diss} = \frac{1}{2} CV^2$$

- Total energy dissipated through the resistor is the energy stored on the capacitor and independent of the resistor – Why ?

$$P_{trans} = \frac{dE}{dt} = CV \frac{dV}{dt} = V \frac{dQ}{dt} = V \cdot I$$

 
Energy dissipated in switched capacitor circuits



- Power dissipation occurs only when voltage and current are in phase – or when stored energy is dissipated to the ground.

$$E_{diss} = \frac{1}{2} C (V^+ - V^-)^2 = \frac{1}{2} C \Delta V^2$$

Energy dissipation in digital circuits

 

$$P_{diss} = P_{static} + P_{transient}$$

- Static power dissipation
 - Junction leakage (diodes)
 - Sub-threshold leakage
- Transient power dissipation
 - Dynamic power dissipation
 - charge or discharge load capacitance.
 - Shoot-through power dissipation – both pmos and nmos active.

$$P_{av} = P_{switching} + P_{short-circuit} + P_{leakage}$$

$$P_{av} = \alpha_{0 \rightarrow 1} C_L V_{dd}^2 f_{clk} + I_{sc} V_{dd} + I_{leakage} V_{dd}$$

Energy Optimization



- Power optimization at different levels
 - Technology level
 - Circuit level and layout level
 - Logic level
 - System and architectural level
 - Algorithmic level
- At higher levels more degrees of freedom available to optimize energy dissipation. Most important – algorithmic optimization.

Technology Level Optimization

- Reduce supply voltage

$$P_{diss} \propto C_{gs} V_{dd}^2$$

$$T_d \propto \frac{C_{gs}}{V_{dd}}$$

- Reduce supply voltage by factor of 2, power dissipation reduces by a factor of 4, delay increases by a factor of 2.
- Reduce feature size (gate capacitance) by a factor of 2, power dissipation reduces by a factor of 2, delay reduces by a factor of 2.
- For the same delay, a reduced feature size (smaller process) leads to 8 times reduction in power if the supply voltage is reduced by 2.
- Trade-off is noise-margin reduces with reduction in supply voltage.

Technology Level Optimization



- Threshold voltage optimization

$$I_{lk} = I_0 \exp\left(-\frac{V_{th}}{U_T}\right) \exp\left(\kappa \frac{V_g}{U_T}\right) \exp\left(-\frac{V_s}{U_T}\right)$$

- Reduce threshold voltage reduces noise margin but increases sub-threshold leakage current – increases static power dissipation.
- Same process allows fabrication of transistors with different threshold voltages. E.g. stanford ultra-low-power CMOS or silicon-on-sapphire technology.

Technology Level Optimization



- Reduction in leakage currents

- Each transistor which is turned off - conducting approximately current of 10pA. A billion transistor IC would consume a current of 10mA – power dissipation of 10mW @ 1V.


$$\frac{I_{d1}}{I_{d2}} = \exp\left(\kappa \frac{V_{g1} - V_{g2}}{U_T}\right) \quad \Delta V_g = \frac{U_T}{\kappa} \log 10$$

- Sub-threshold slope determines how effectively the transistor can be shut off. Maximum sub-threshold slope is 60mV/dec when $\kappa = 1$.
- Silicon-on-sapphire technology can get close to the theoretical limit.

Circuit level optimization


- Reduce the capacitance of the line which has the highest switching activity.

 - Which of the output lines O_1 or O_2 should be connected to a shorter interconnect? Assume the inputs A and B are random.



- Transistor size optimization.

- $N = (W/L)$, C_p = parasitics

 

$$T_d \propto \frac{C_P + NC_{gs}}{NC_{gs}} \frac{V_{dd}}{(V_{dd} - V_{th})^2} \propto \frac{(1 + \frac{\alpha}{N})}{V_{dd}}$$

$$V_{dd}'' = \frac{(1 + \frac{\alpha}{N})}{(1 + \alpha)} V_{dd}$$

$$P_d = (C_P + NC_{gs}) V_{dd}''^2 f$$

$$F \propto \frac{N(1 + \frac{\alpha}{N})^3}{(1 + \alpha)^3}$$


- Significant parasitics increase in transistor sizes reduces power dissipation – otherwise NO !

Circuit Level Optimization

- Reduce switching activity
 - Minimize the number of transistors in a function.
 - Power off inactive blocks (power management).



Logic optimization: Dynamic or static or adiabatic

 - NAND – Output is high 25% of time.
- Adiabatic logic – asymptotically zero power.



Circuit Level Optimization

  - Logic topology
 - For the two logic circuits which output shows the most switching activity ?
 - What are the advantages and disadvantages of each of the logic topologies ?



- Clock gating or power off inactive blocks
 - For e.g. for a comparator $A > B$, gate the rest of the circuit if MSB of $A > \text{MSB of } B$.

Architecture Level Optimization


- Parallel hardware

- Break a task in ``n'' independent components, that can be performed in parallel.
- Reduce the frequency of operation by a factor of ``n''.
- Reduce the supply voltage by a factor of ``n'' – same speed
- Area increases by a factor of ``n''.

$$P_{diss} = n \times \alpha_{0 \rightarrow 1} C_L \left(\frac{V_{dd}}{n} \right)^2 \left(\frac{f_{clk}}{n} \right)$$


- Number representation

 - Use gray codes instead of binary codes.
- Order the inputs such that correlated signals appear in the system.



Algorithm Level Optimization



- Minimize the number of operations (e.g. use binary search instead of a linear search)
- Use signal statistics
- Multiplication with a constant (use shift operation or a look-up table approach).
- Use finite precision algorithms.
- Fundamental limits of power dissipation
 - Viewed as energy transfer problem – need to transfer more energy than thermal energy.
 - Logic gate resistance – R. Thermal noise: $e_n^2 = 4KTR\Delta f$
 - Power transferred $P_{th} = \frac{e_n^2}{4R}$ $P_s > P_{th} = KT\Delta f$
 - Fundamental limit for a logic transition: $E_s > KT$

 

Power Estimation and Optimization: Analog


For analog circuits the power dissipation is determined by:

  - Signal-to-noise ratio
- Frequency of operation or bandwidth
- Fundamental limit determined by power consumption per pole.



Aim: Maintain the signal above the noise floor.

 Power Estimation and Optimization: Analog



- Signal-to-noise ratio: $SNR = \frac{V_{pp}^2 / 8}{KT / C}$

- Power consumed to maintain a target voltage level.

$$P = V_{dd} f C V_{pp} = f C V_{pp}^2 \frac{V_{dd}}{V_{pp}}$$

- Power per pole: $P_d / pole = 8KTf SNR \frac{V_{dd}}{V_{pp}}$
- For $V_{pp} = V_{dd}$


$$P_d / pole = 8KTf SNR - \text{Compare with digital fundamental limit.}$$

Analog Power Optimization Rules



- Reduce the number of capacitances. Capacitances increases the power dissipation to achieve a specific bandwidth – use more capacitances ONLY if it reduces the noise power by the same amount.
- Optimize the power for the bias circuitry. Inadequate bias schemes increase the noise and power dissipation (e.g. cascoding optimizes the bias).
- Maintain rail-to-rail signal at internal nodes.
- Reduce additional sources of noise, unnecessary transistors or devices.
- Low power dissipation and low precision.
- Use sub-threshold biasing when speed is not critical.

 Fundamental limits using power-delay product



- Time constant: $\tau = C / g_m$

- Power dissipation: $P = V_{dd} I_{bias}$


- Power-delay product: $P\tau = \frac{I_{bias}}{g_m} C V_{dd}$

- Increase $\frac{g_m}{I_{bias}}$


- Use sub-threshold biasing $\frac{g_m}{I_{bias}} = \frac{K}{U_T}$

- Reduce V_{dd} and C – determined by the KT/C noise and the input/output dynamic range.

 - Use compressive signaling at the capacitor (log-domain).



 - Low-voltage cascodes
- Eliminate gate-voltage drops
- Maintain transistors on the verge of saturation to maximize output swing.



Dynamic Biasing Techniques

