



...

Noise Analysis



...

CSE562: Analog Integrated Circuits
Shantanu Chakrabartty



What is noise ?



- Any input that is not relevant to the signals of interest.

Sources of noise


- **External sources**
 - Coupling from outside of the system of interest. E.g. substrate coupling, interconnect noise, power supply noise.
 - Can be eliminated by careful circuit design, shielding and layout.
- **Fundamental sources**
 - Noise generated from within the device.
 - Fundamental and microscopic in nature and in principle can never be eliminated but can be reduced.



Characterization of noise



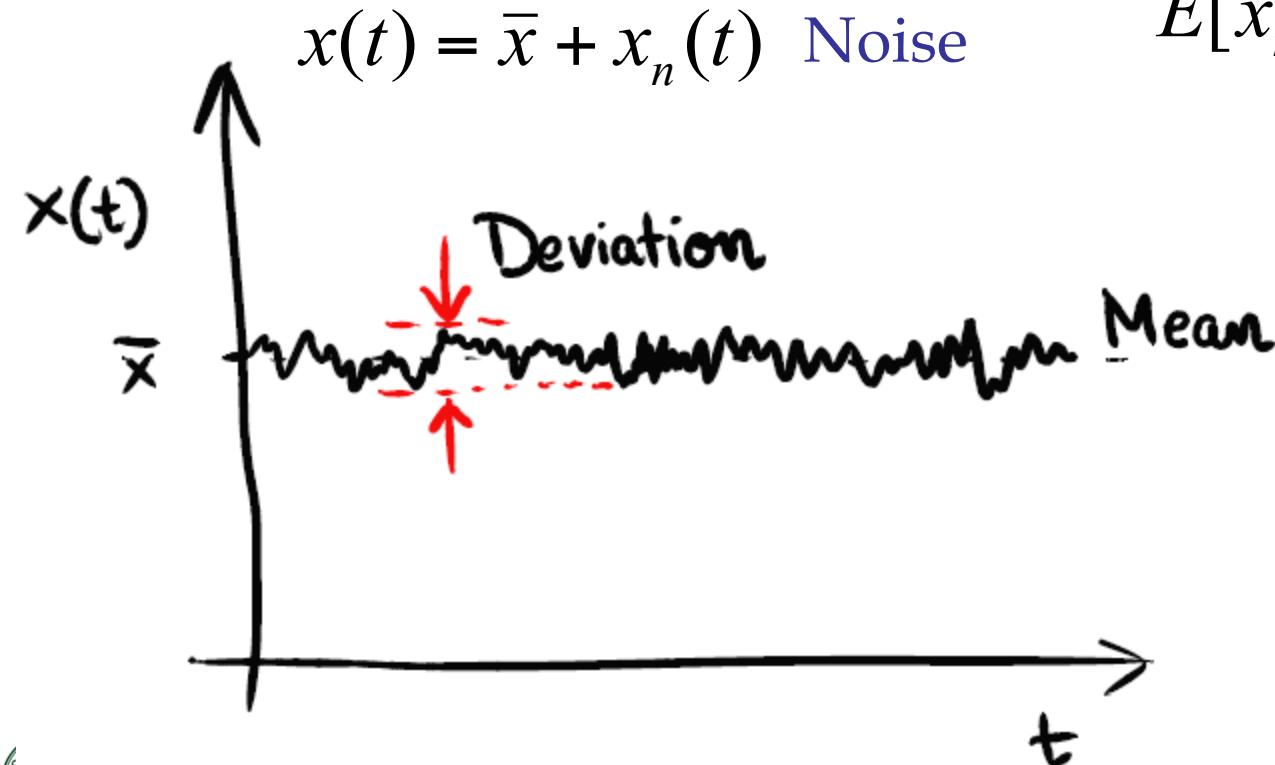
- Stochastic signal - follows an underlying probability distribution.
- Stationary - Statistical property of the signal remains constant with respect to time.



- Mean
- $$E[x_n(t)] = \lim_{\tau \rightarrow \infty} \frac{1}{\tau} \int_0^\tau x_n(t) dt = 0$$
- Variance - energy in the error signal/noise
- $$\bar{x}_n^2 = E[x_n^2(t)]$$
- Autocorrelation
- $$R(\tau) = E[x_n(t)x_n(t + \tau)]$$


Combination of noise sources

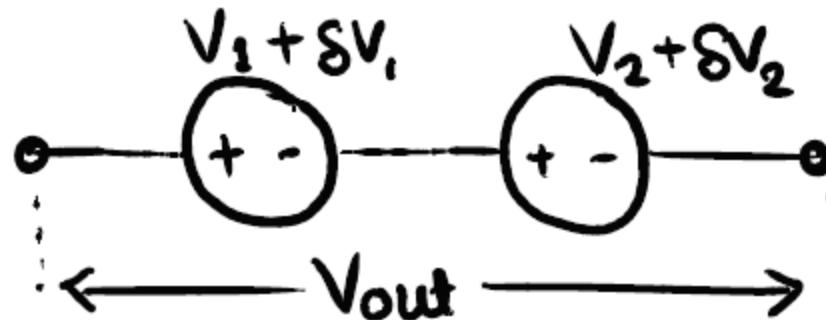- Unrelated noise sources are statistically independent.




$$V_{out} = V_1 + V_2$$
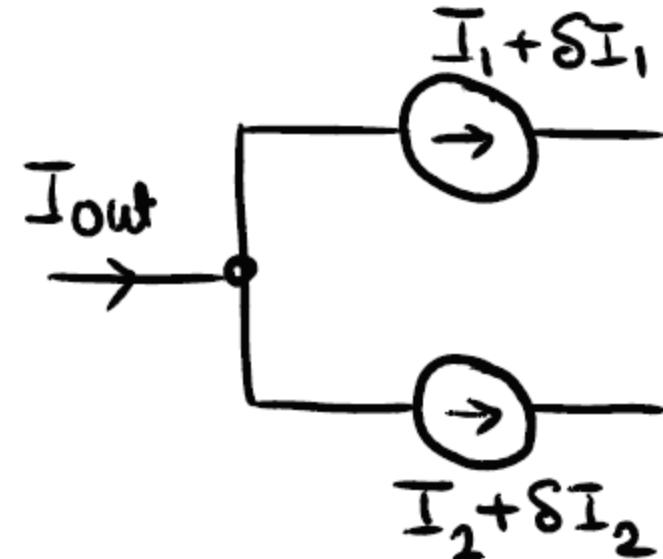
$$\bar{V}_{out}^2 = \bar{V}_{n1}^2 + \bar{V}_{n2}^2$$



$$\begin{aligned} I_{out} &= I_1 + I_2 \\ \bar{I}_{out}^2 &= \bar{I}_{n1}^2 + \bar{I}_{n2}^2 \end{aligned}$$

- What about this circuit ?

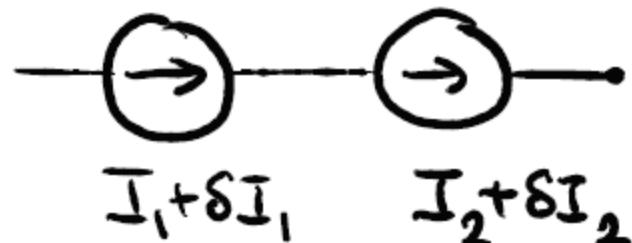

Frequency domain characterization



- Distribution of noise power over frequency/spectrum.
- Characterized by noise power spectral density.

$$\bar{e}_n^2 = \lim_{\tau \rightarrow \infty} \frac{1}{\tau} \int_{-\tau}^{\tau} e_n^2(t) dt = \lim_{\tau \rightarrow \infty} \frac{1}{\tau} \int_{-\infty}^{\infty} e_n^2(t) W^2(t, \tau) dt$$

- Window function

- Parseval's theorem

$$\bar{e}_n^2 = \lim_{\tau \rightarrow \infty} \frac{1}{2\pi\tau} \int_{-\infty}^{\infty} |E(\omega, \tau)|^2 d\omega$$

$$\bar{e}_n^2 = \frac{1}{2\pi} \int_0^{\infty} \lim_{\tau \rightarrow \infty} \frac{1}{\tau} 2|E(\omega, \tau)|^2 d\omega$$

$$\bar{e}_n^2 = \frac{1}{2\pi} \int_0^{\infty} S_E(\omega) d\omega$$

One sided power spectrum

White noise



- **Shot noise :** Generated by a source of carriers. Noise due to variability in generation and arrival time of carrier at the source.
 - Requires a current flow.
 - Noise in diodes, BJTs, vacuum diodes, MOSFET biased in sub-threshold.
- **Thermal noise:** Noise due to variability in carrier transport within a transport channel. Due to thermal fluctuations.
 - Requires no current flow.
 - Proportional to temperature.
 - Noise in resistors, MOSFET (above-threshold) and JFETs.




White noise: Frequency domain



- White noise: power of noise constant within any frequency band.
- Statistically the easiest noise to work with.


$$S_E(f) = A$$

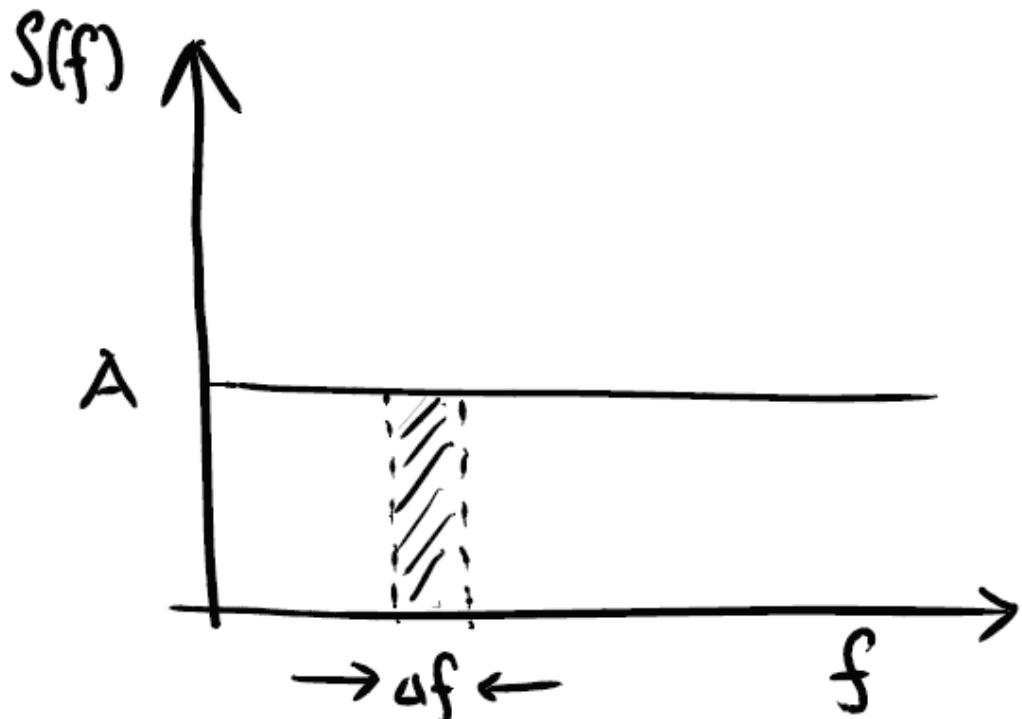


Flicker noise: Frequency domain




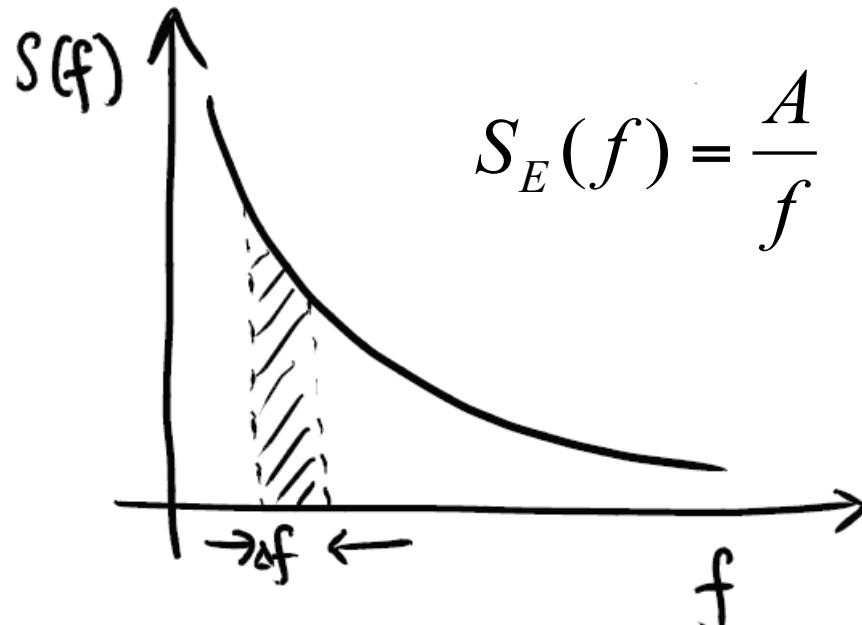
- Flicker noise or $1/f$ noise : noise power concentrated at lower frequencies



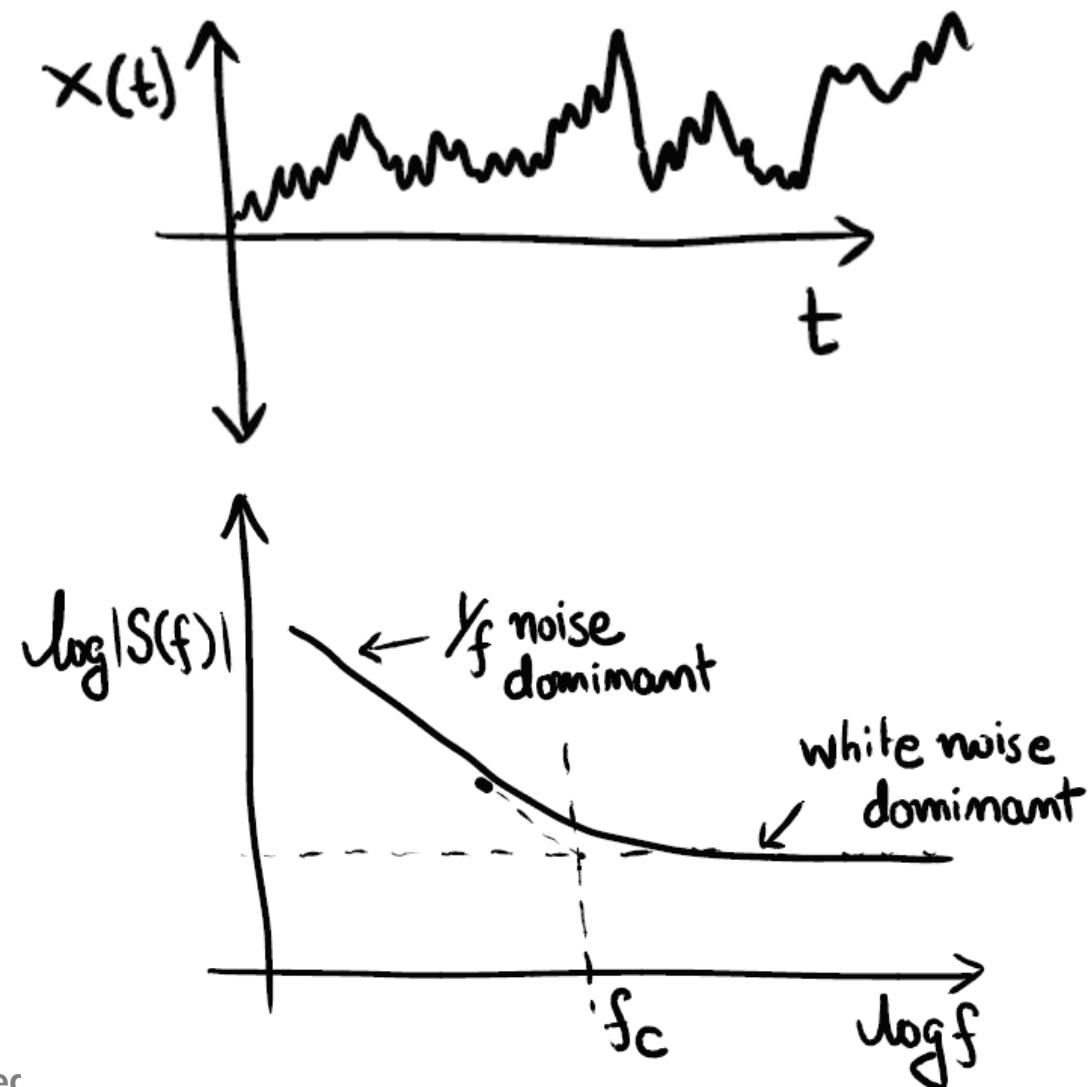- Most system has both noise components.
- Corner frequency (f_c): where white noise and flicker noise are equal.



Derivation of thermal noise in resistors

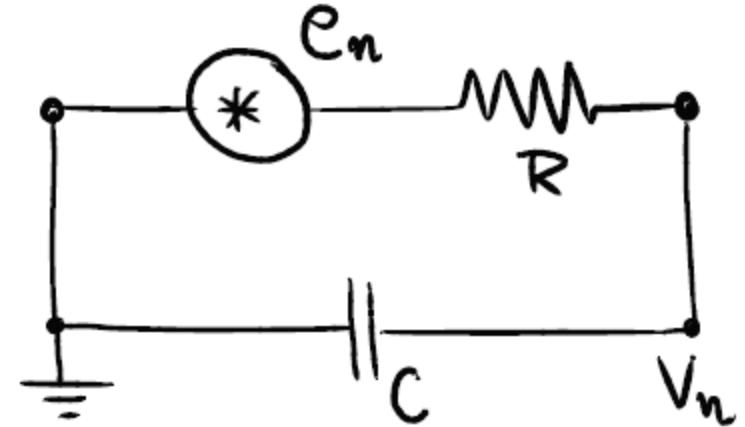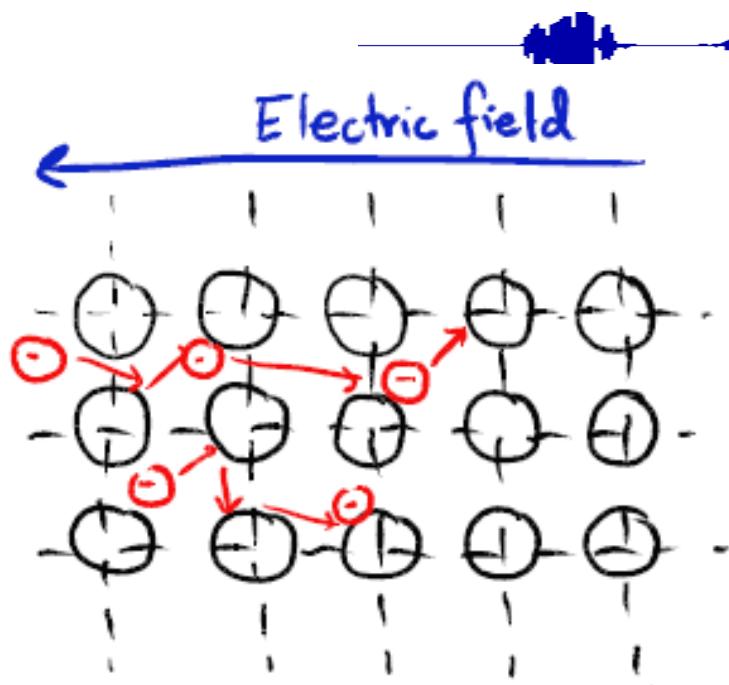

$$v_n(t) + i_n(t)R = e_n(t)$$

$$v_n(t, \tau) + i_n(t, \tau)R = e_n(t, \tau)$$

$$|V_n(\omega, \tau)|^2 = \frac{|E_n(\omega, \tau)|^2}{(1 + \omega^2 R^2 C^2)}$$



Derivation of thermal noise in resistors




$$\bar{v}_n^2 = \frac{1}{2\pi} \int_0^\infty \lim_{T \rightarrow \infty} \frac{1}{T} 2|V(\omega, \tau)|^2 d\omega$$

$$\bar{v}_n^2 = \frac{1}{2\pi} \int_0^\infty \left(\frac{1}{1 + \omega^2 R^2 C^2} \right) \lim_{T \rightarrow \infty} \frac{1}{T} 2|E(\omega, \tau)|^2 d\omega$$

$$\bar{v}_n^2 = \frac{A}{2\pi} \int_0^\infty \left(\frac{1}{1 + \omega^2 R^2 C^2} \right) d\omega = \frac{A}{4RC}$$

$$\bar{e}_n^2 = \frac{1}{2\pi} A \Delta \omega \quad \bar{e}_n^2 = \frac{2}{\pi} C \bar{v}_n^2 R \Delta \omega$$

$$\boxed{\bar{e}_n^2 = 4KTR\Delta f}$$

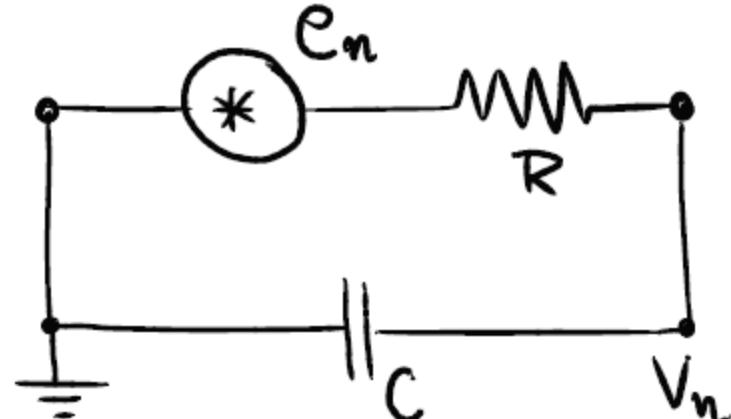

Thermal equilibrium:
Average potential
energy equals thermal
energy

$$\boxed{\frac{1}{2} C \bar{v}_n^2 = \frac{1}{2} KT}$$

$$\boxed{\bar{i}_n^2 = 4KTG\Delta f}$$

Thermal noise: Limits



$$\bar{e}_n^2 = 4KTR\Delta f$$


- When is the white noise formula valid ?
- Note that the formula implies infinite energy if integrated over all the frequency bins.
- Include quantum limits – modified version of Plank's law

$$\frac{1}{2} C \bar{v}_n^2 = \frac{1}{2} \frac{hf}{e^{hf/KT} - 1} + \frac{1}{4} hf$$

- At TeraHz frequencies hf comparable to the thermal energy KT .
- At photonic frequencies the uncertainty/noise comes from Heisenberg's uncertainty principle.



Derivation of shot noise

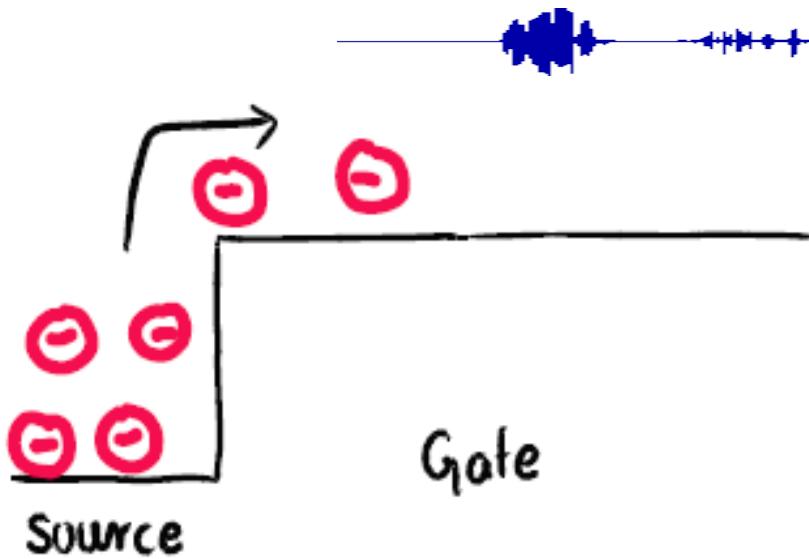

- Randomness in the electrons that jump a potential barrier.
- Can be modeled as a Poisson process – number of electrons jumping the barrier.

$$P(n) = \frac{\lambda^n}{n!} e^{-\lambda}$$

$$\bar{n} = \lambda; \bar{n}^2 = \lambda$$

- Current $\bar{i} = \frac{e}{\Delta t} \bar{n}$

$$\bar{i}^2 = \left(\frac{e}{\Delta t} \right)^2 \bar{n}^2 = \left(\frac{e}{\Delta t} \right)^2 \bar{n} = \frac{e}{\Delta t} \bar{i}$$

- Double sided spectral density.


$$\bar{i}^2 = e \bar{i} \Delta f$$

- Single sided spectral density.

$$\bar{i}_n^2 = 2e \bar{i} \Delta f$$



Thermal noise from Shot noise

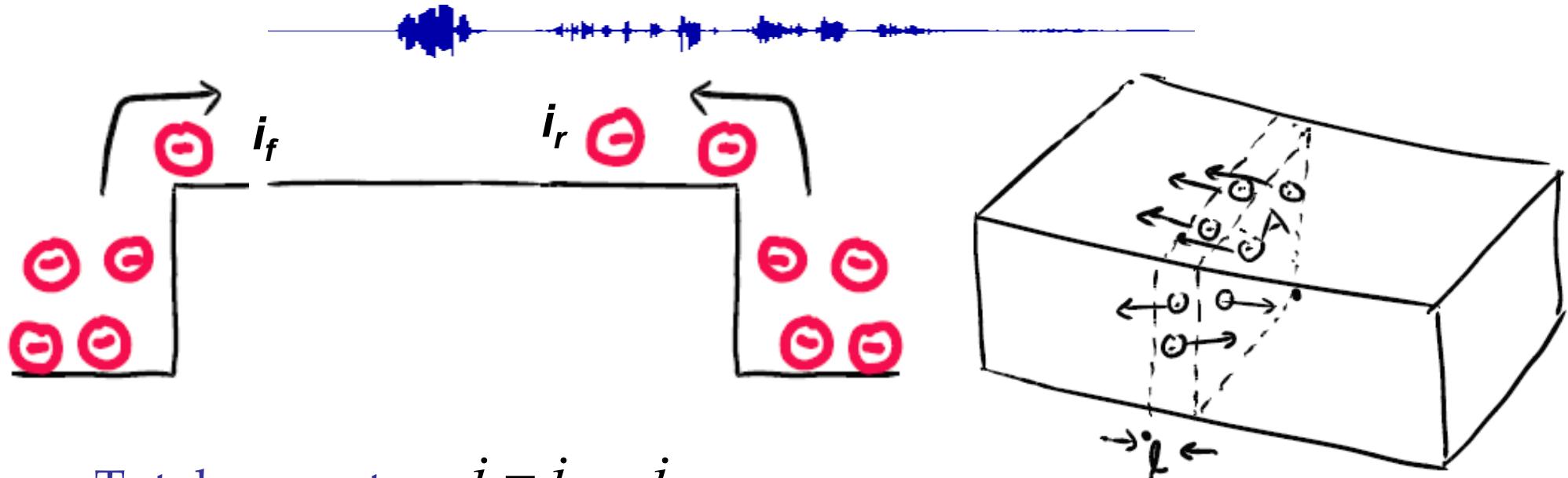

- Total current $i = i_f - i_r$
- Total noise $\bar{i}_n^2 = \bar{i}_{nf}^2 + \bar{i}_{nr}^2$
- Electrons diffuse $\bar{i}_{f,r} = enD \frac{A}{l}$
- Einstein's relationship



$$D = \left(\frac{KT}{e} \right) \mu$$

$$\bar{i}_n^2 = 4KT \frac{e\mu nA}{l} \Delta f = 4 \frac{KT}{R} \Delta f$$

Noise on a capacitor



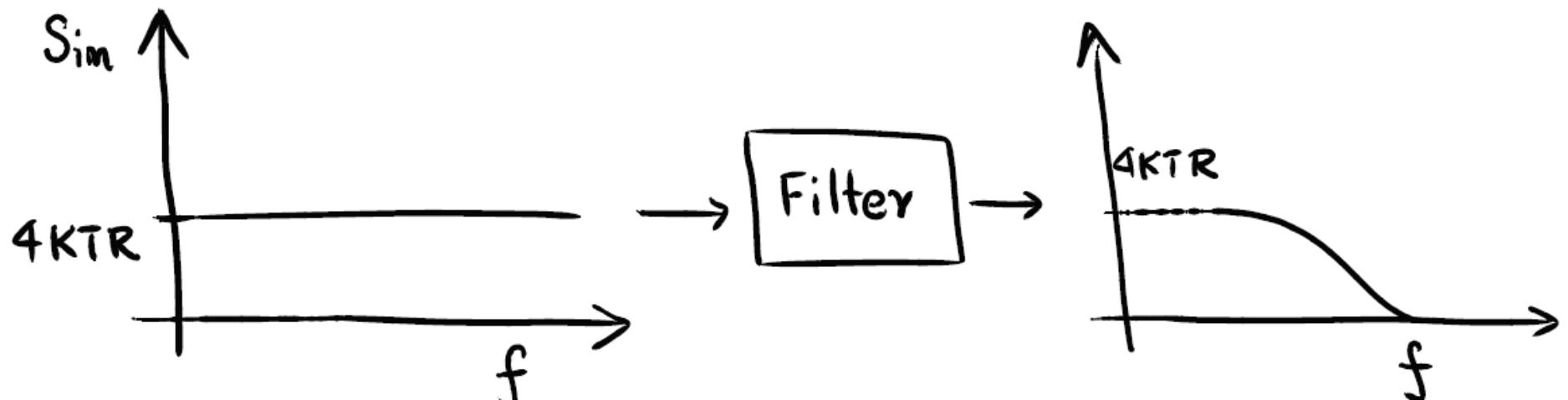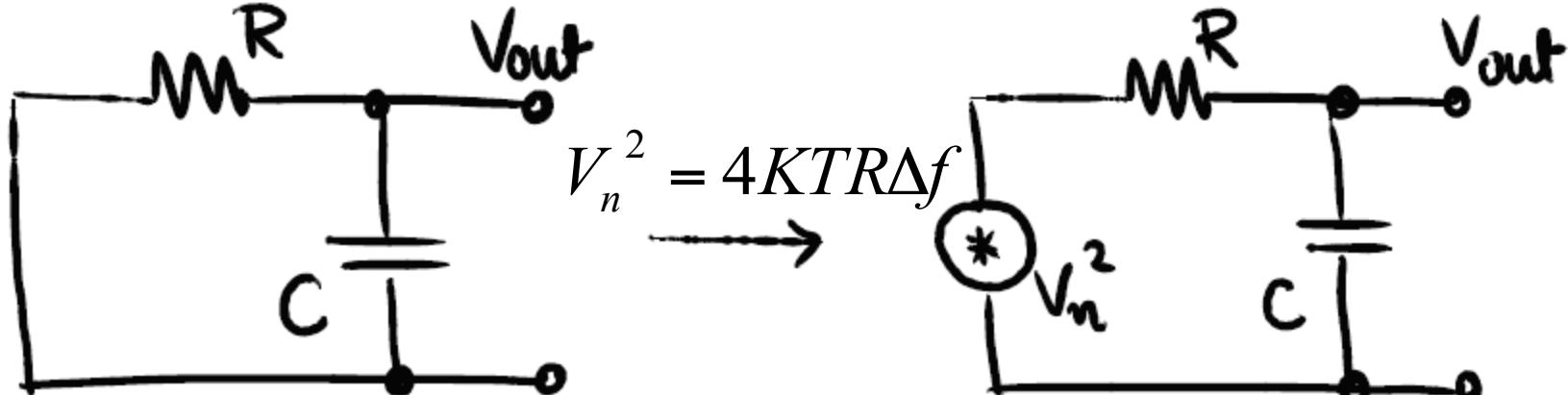- An ideal capacitor itself is noiseless.




$$\bar{v}_{out}^2 = \frac{4KTR}{2\pi} \int_0^{\infty} \frac{1}{(1 + 4\pi^2 f^2 R^2 C^2)} df = \frac{KT}{C}$$

- Independent of the resistor

Noise on a capacitor



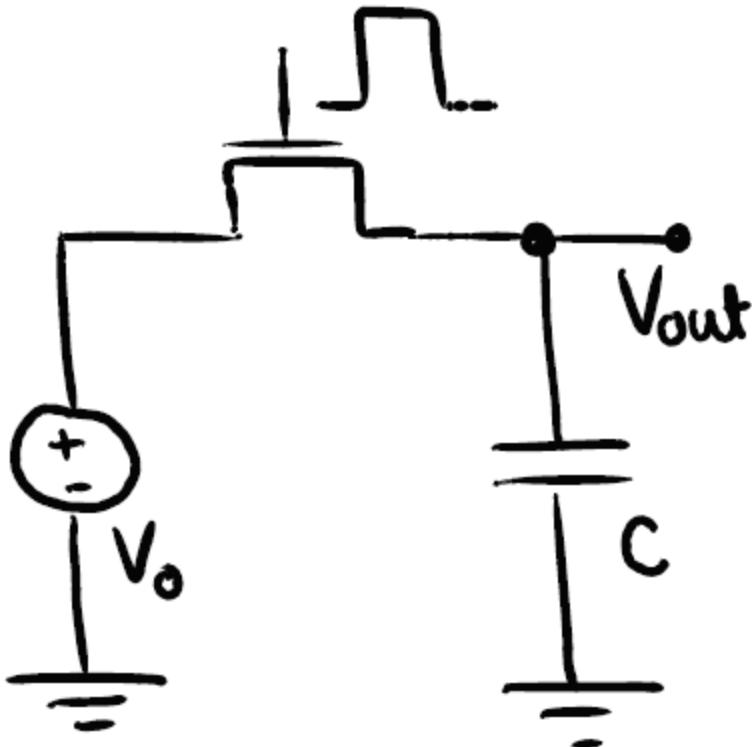- For a 1pF capacitor charging and discharging during every cycle will contribute to a noise voltage of $\pm 64\mu V$.
- Large value of capacitor is required for reducing the effect of noise.
- For white noise use averaging - sample the voltage multiple times.



$$V_{sum} = V_{out1} + V_{out2} + \dots + V_{outN}$$

$$\bar{V}_{out1} = \bar{V}_{out2} = \dots = \bar{V}_{outN} = V_{out}$$


$$\text{Signal Power} = N^2 V_{out}^2$$

$$\text{Noise Power} = N \frac{KT}{C}$$

$$SNR \propto N$$




Noise in MOSFET

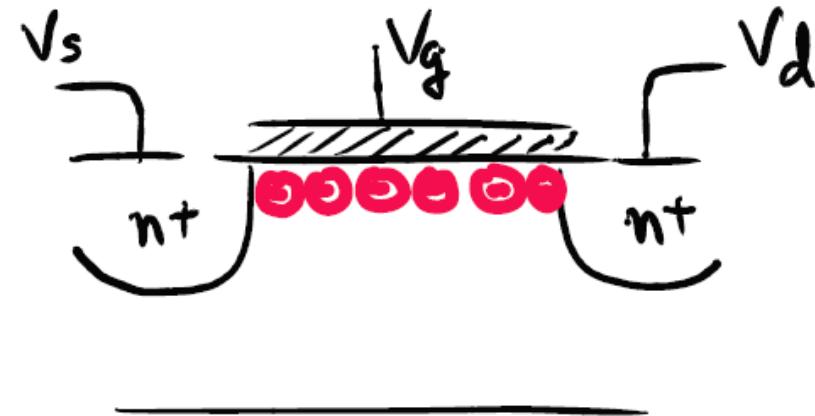

- Above threshold: Each element of the channel acts as resistor.

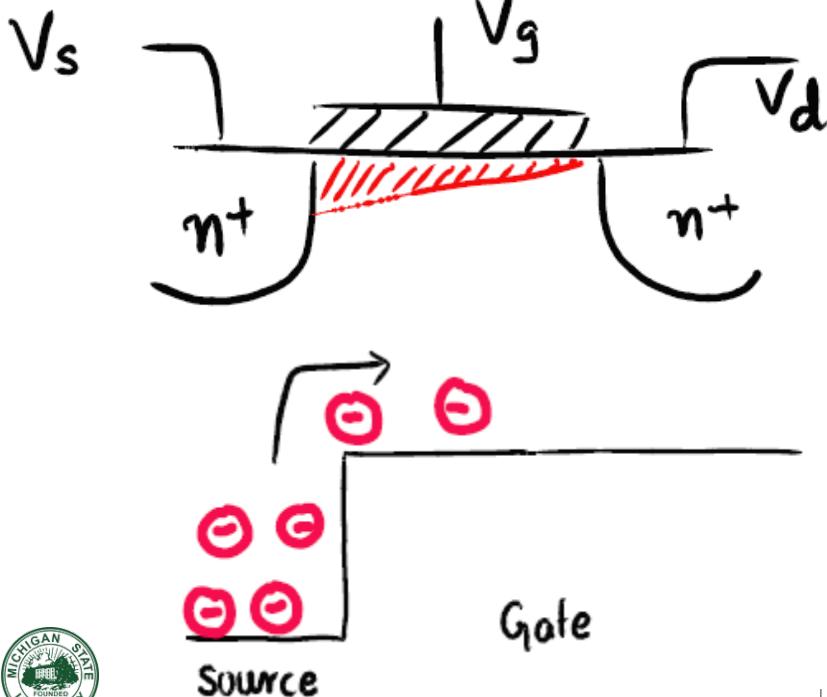
$$R_{ON} = \frac{1}{\frac{\partial I_{ds}}{\partial V_{ds}}} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{gs} - V_{th})} \approx \frac{1}{g_m}$$



- However the channel width is graded

$$\bar{i}_n^2 = 4KT\gamma g_m \Delta f$$

$$\gamma \approx 2/3$$

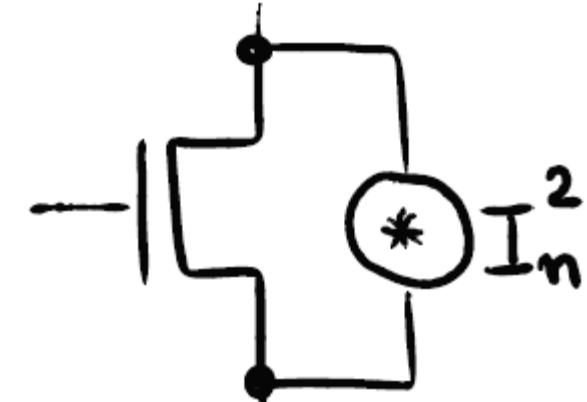


- Sub-threshold: The source and drain act as a random source.

$$\bar{i}_n^2 = 2ei\bar{i}\Delta f$$



Flicker noise in MOSFET

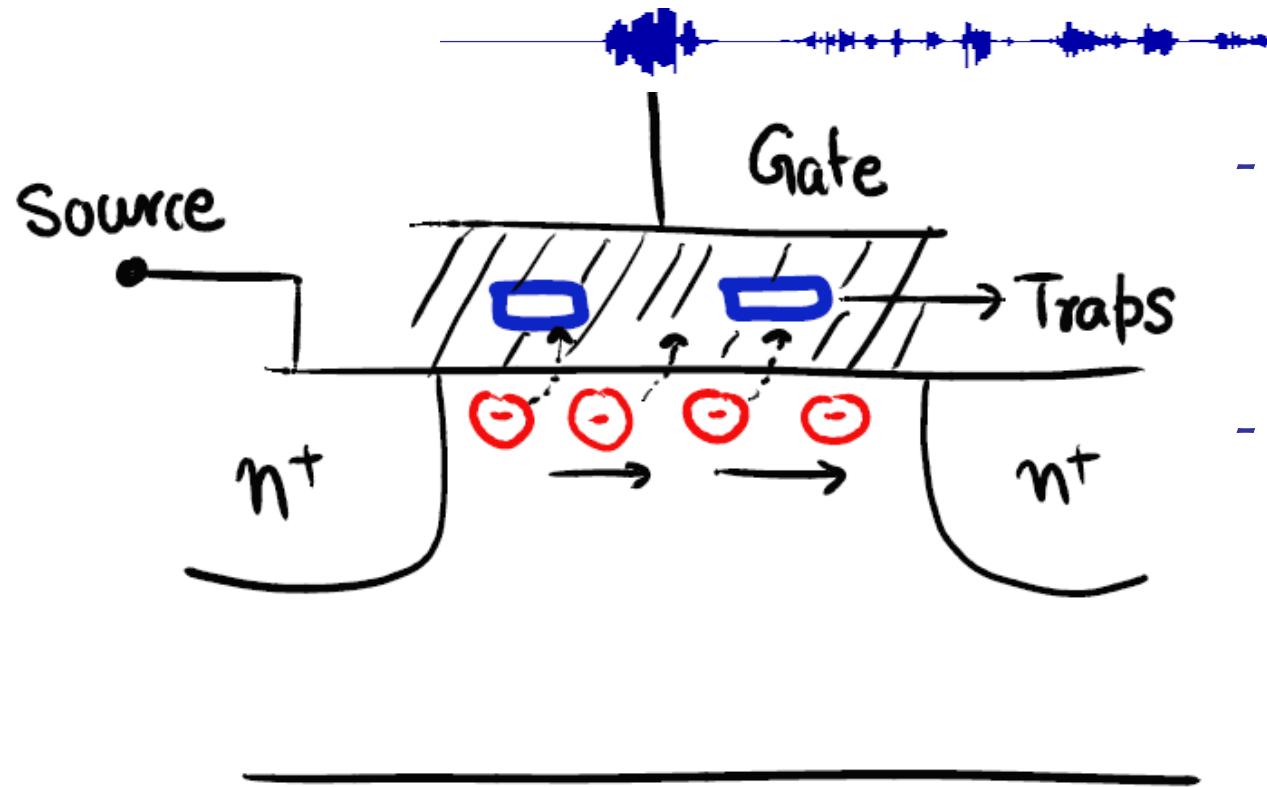

- Due to presence of dangling bonds and surface imperfections.
- The dangling bonds create traps that capture electrons/holes and then later release them back into the channel.


- Trapping and de-trapping is a slow process. Trapping charge leads to change in threshold voltage - changes the conductance and current. PMOS has lower flicker noise.

$$S_{Id}^2(f) = \frac{KF I_d^{AF}}{f^{EF} C_{ox} WL_{eff}}$$

Noise analysis



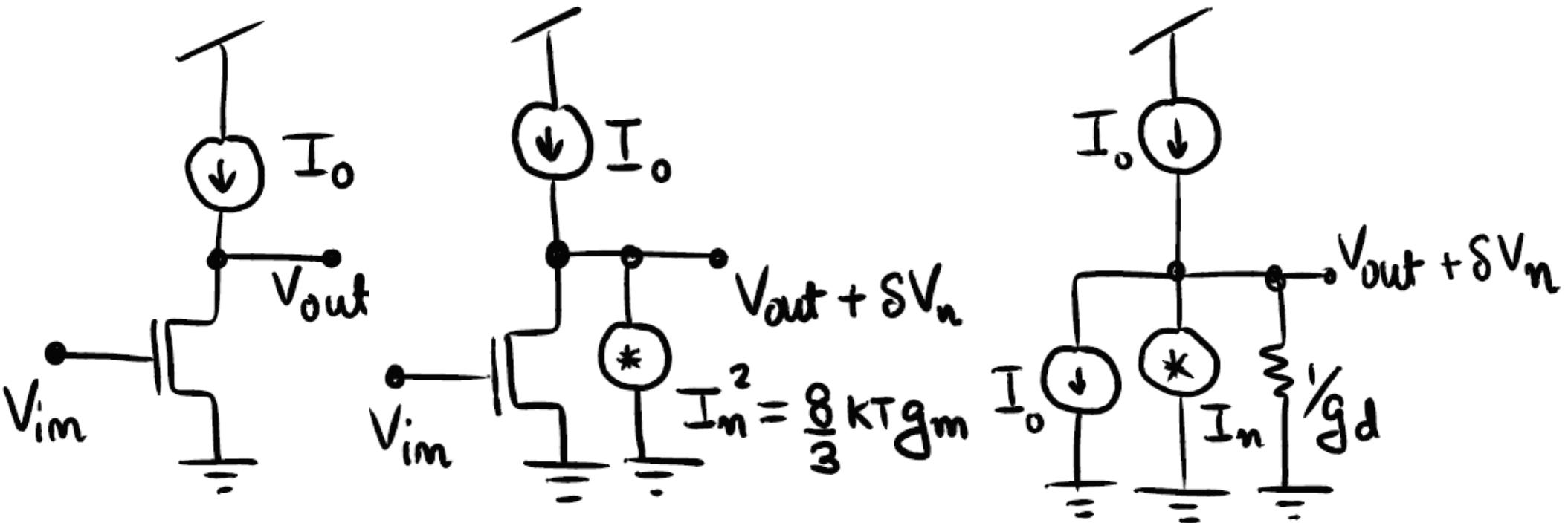- Thermal and flicker noise can be analyzed in a similar manner.
- Use the amplifier equivalent circuit we discussed before.



$$\bar{V}_{out} = \frac{1}{g_d} I_n$$



$$\bar{V}_{out}^2 = \frac{1}{g_d^2} \bar{I}_n^2$$

$$\bar{V}_{out}^2 = \frac{8}{3} KT \frac{g_m}{g_d^2} \Delta f$$

Input referred noise



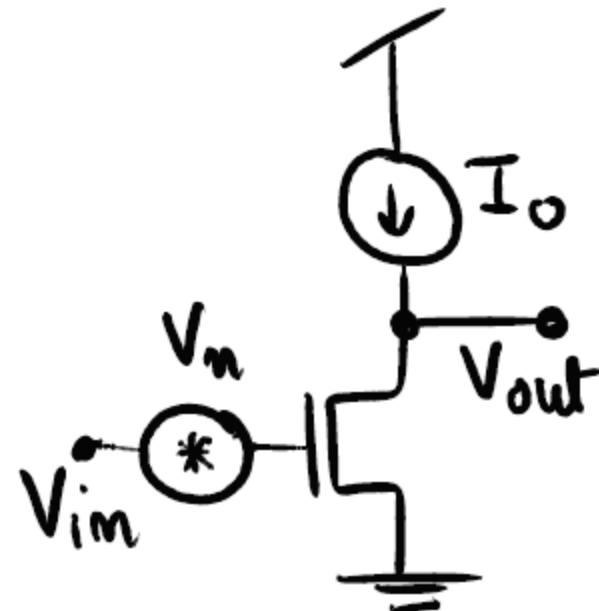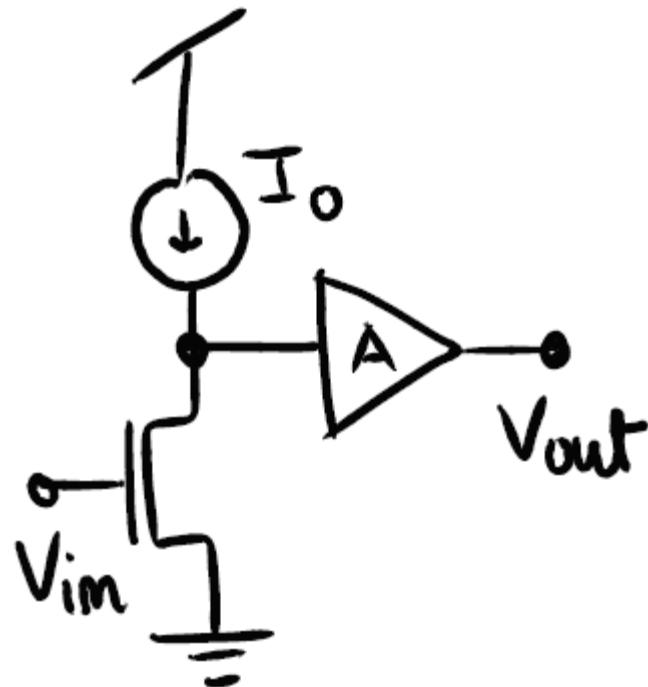- Analyzing only the output noise leads to a biased perception.
- Standard: Refer the output noise to the input of the amplifier.




$$\bar{V}_{out}^2 = \frac{8}{3} KTA^2 \frac{g_m}{g_d^2} \Delta f$$

$$\bar{V}_{in}^2 = \frac{\bar{V}_{out}^2}{(Gain)^2}$$

$$\bar{V}_{in}^2 = \frac{8}{3} KT \frac{1}{g_m} \Delta f$$






Common source amplifier

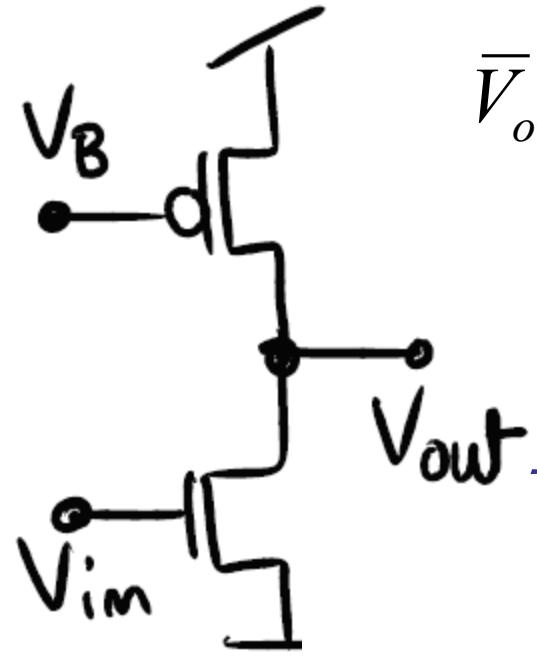




$$\overline{V}_{out}^2 = \frac{8}{3} KT \frac{g_{m1}}{(g_{d1} + g_{d2})^2} \Delta f + \frac{8}{3} KT \frac{g_{m2}}{(g_{d1} + g_{d2})^2} \Delta f$$

$$\overline{V}_{in}^2 = \frac{8}{3} \frac{KT}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}} \right) \Delta f$$

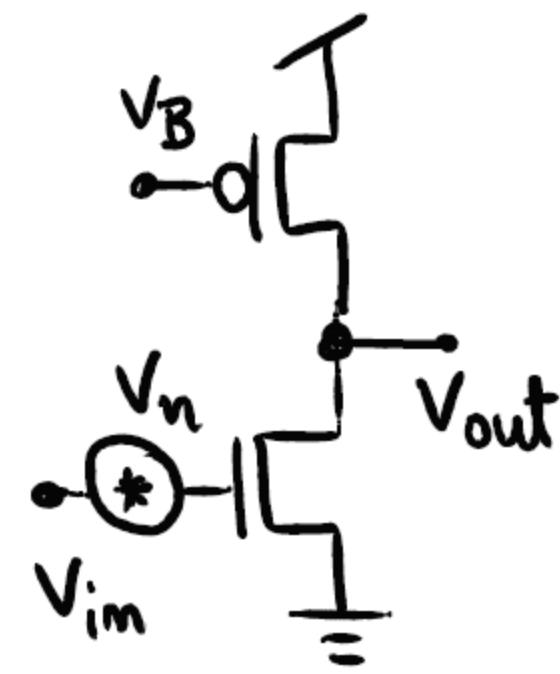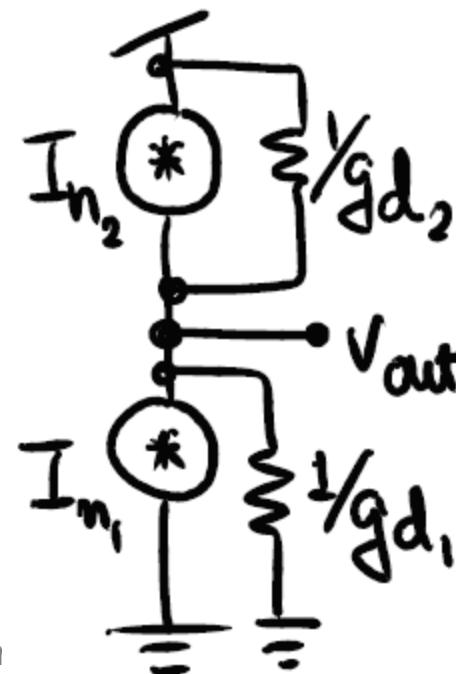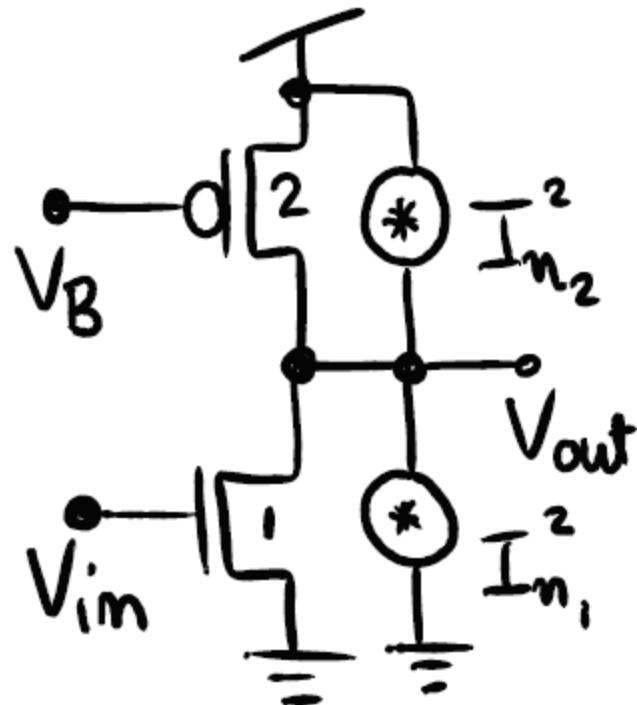For a fixed amplifier gain, low noise design means reduce the transconductance of current source.




Common gate and cascoded amplifier

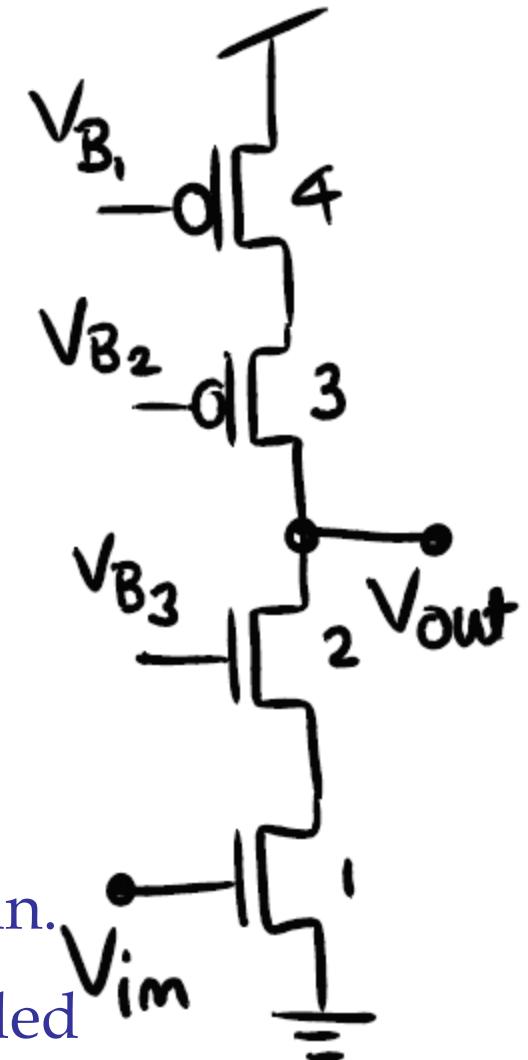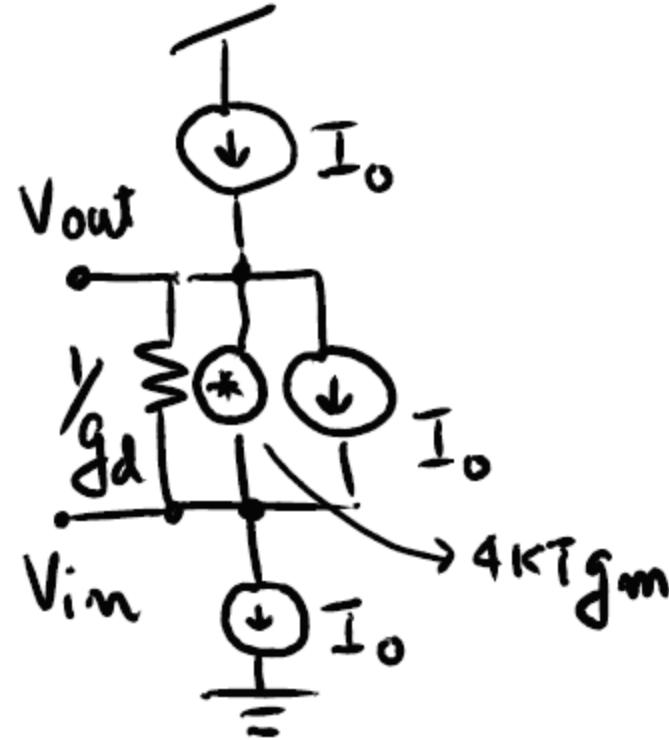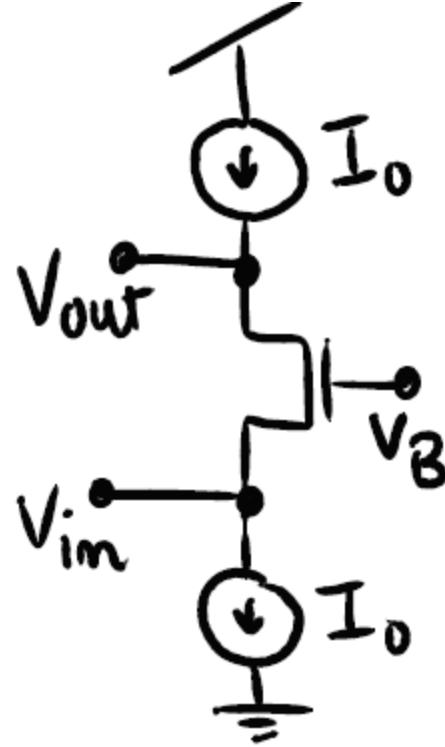

- Common source amplifier – no noise current gain.
- What is the effect of transistors 2 and 3 in cascoded amplifier – does it add to the amplifier noise ?

Differential amplifier

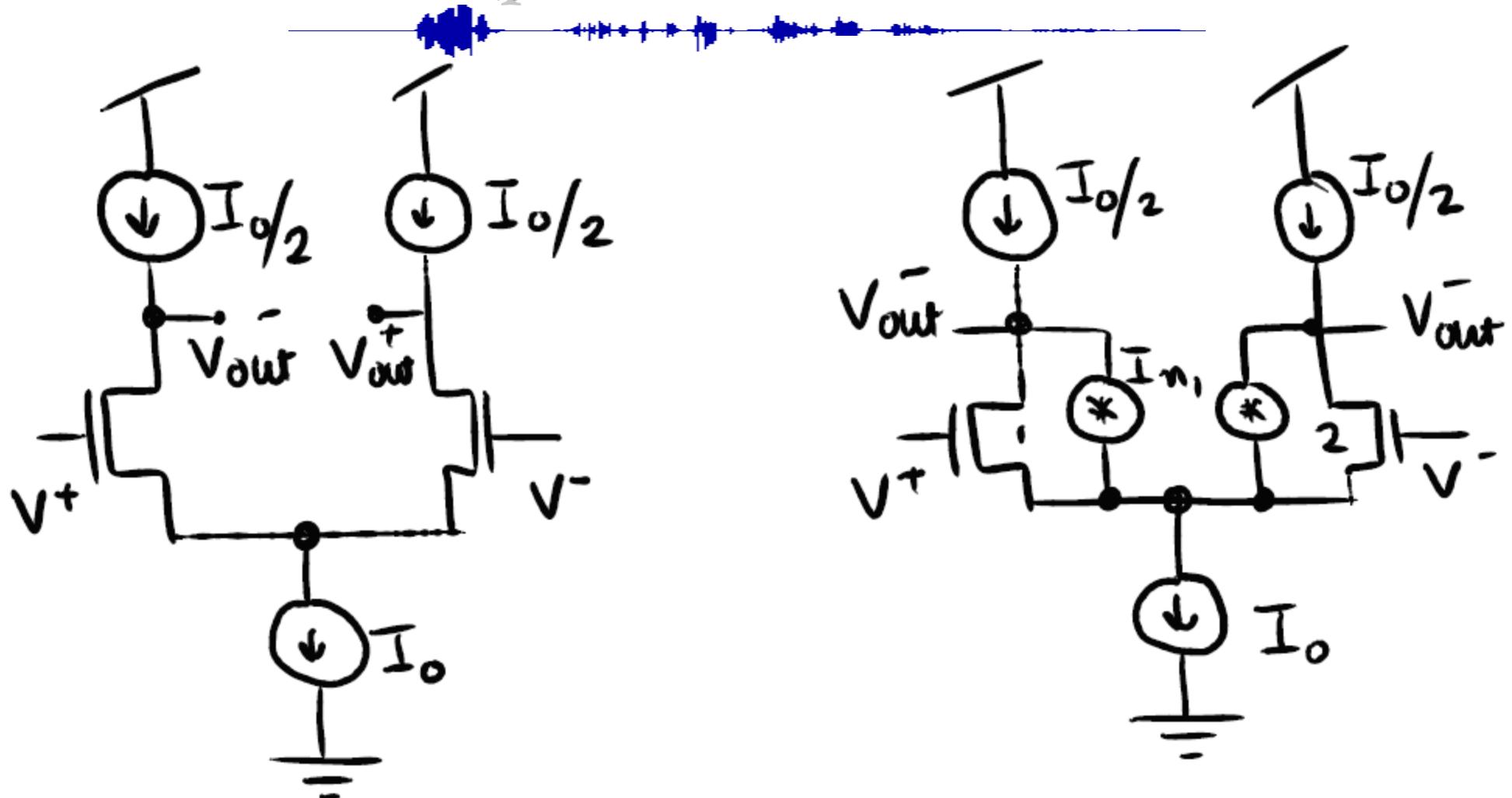

- Use symmetry to create two common source amplifiers.
- Noise in differential pair – twice the noise as a single stage amplifier – why then choose a differential topology ?



Noise in Differential Amplifier



- Easier to refer the noise current as a gate voltage noise.


$$\bar{i_n^2} = \frac{8}{3} K T g_m \Delta f$$
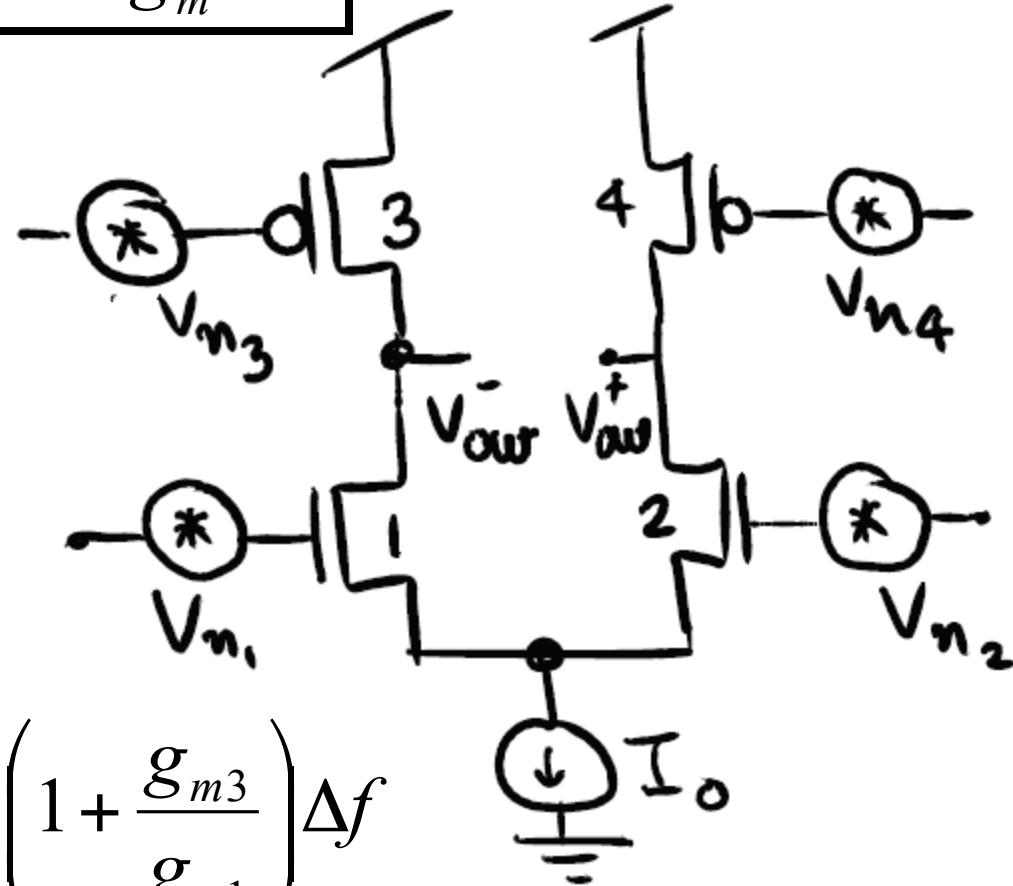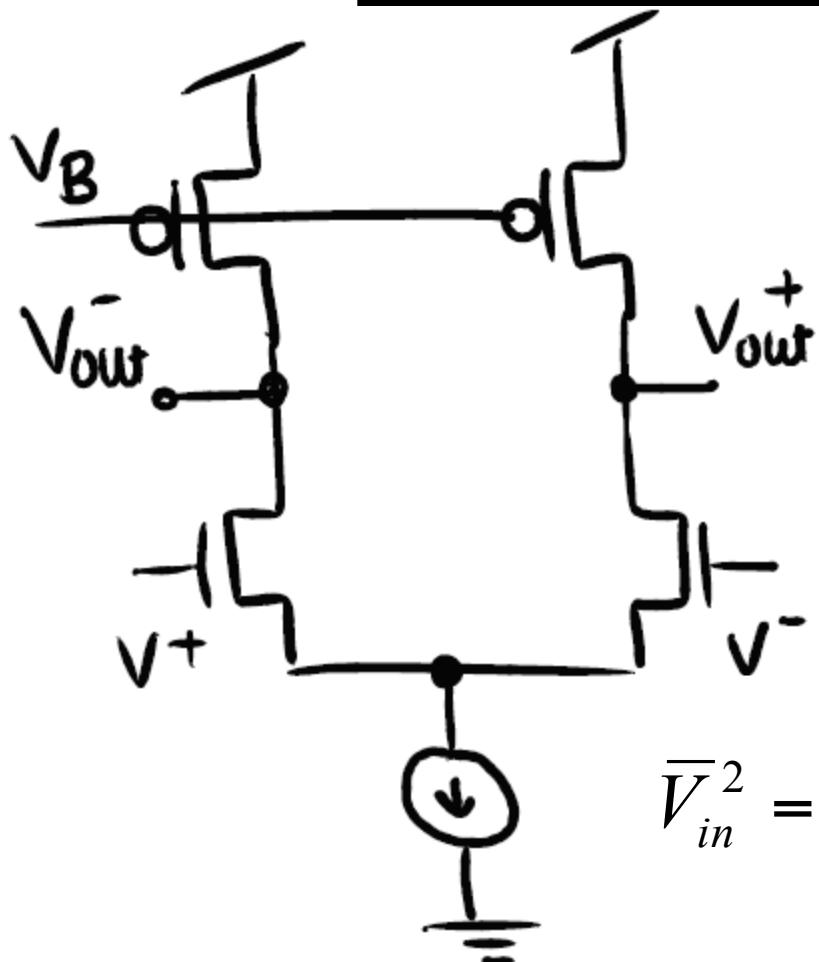
$$\bar{v_n^2} = \frac{8 K T}{3 g_m} \Delta f$$



$$\bar{V_{in}^2} = \frac{16}{3} \frac{K T}{g_{m1}} \left(1 + \frac{g_{m3}}{g_{m1}} \right) \Delta f$$

Noise in Differential Amplifier

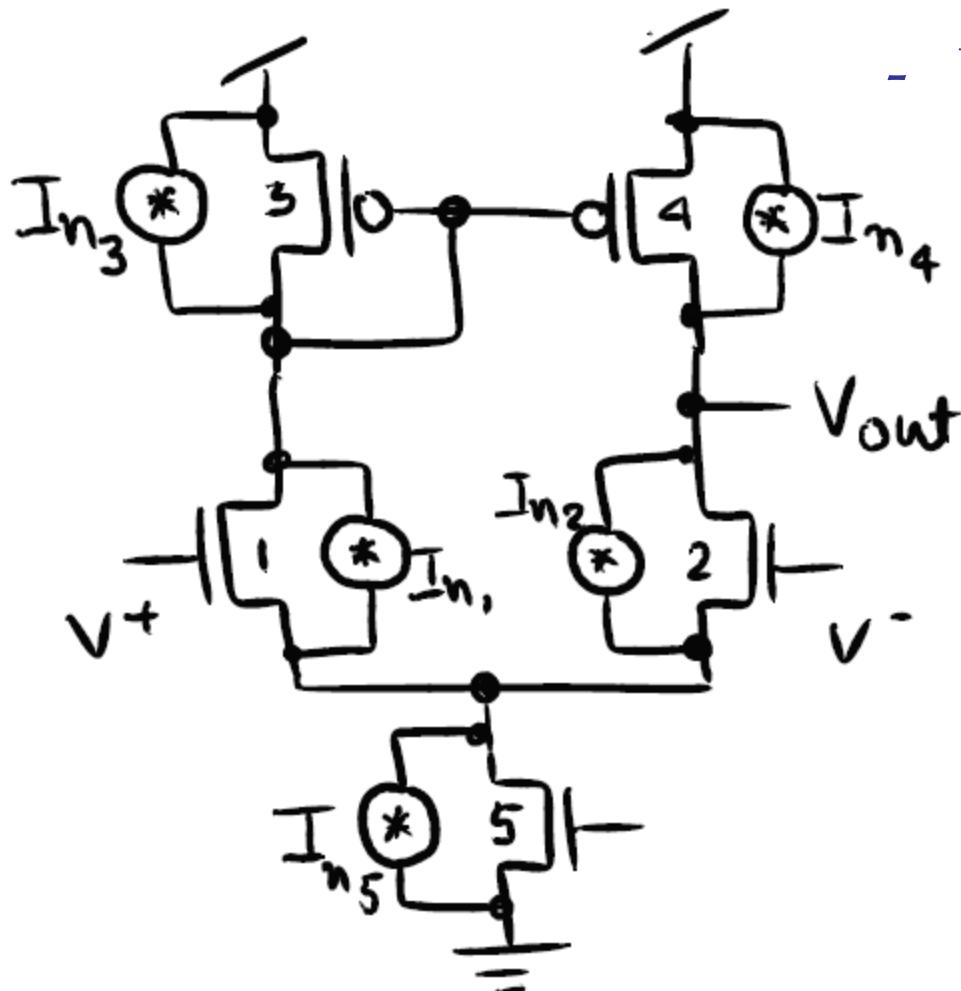


- What about the noise in transistor 5 ?

$$\overline{V_{in}}^2 = \frac{16}{3} \frac{KT}{g_{m1}} \left(1 + \frac{g_{m3}}{g_{m1}} \right) \Delta f$$


Noise Analysis Principles

- Put noise voltage sources at the gates of the transistors.
- Calculate the effective gain from the voltage sources to the output using superposition.
- Divide by the total gain of the system.

Low noise amplifier

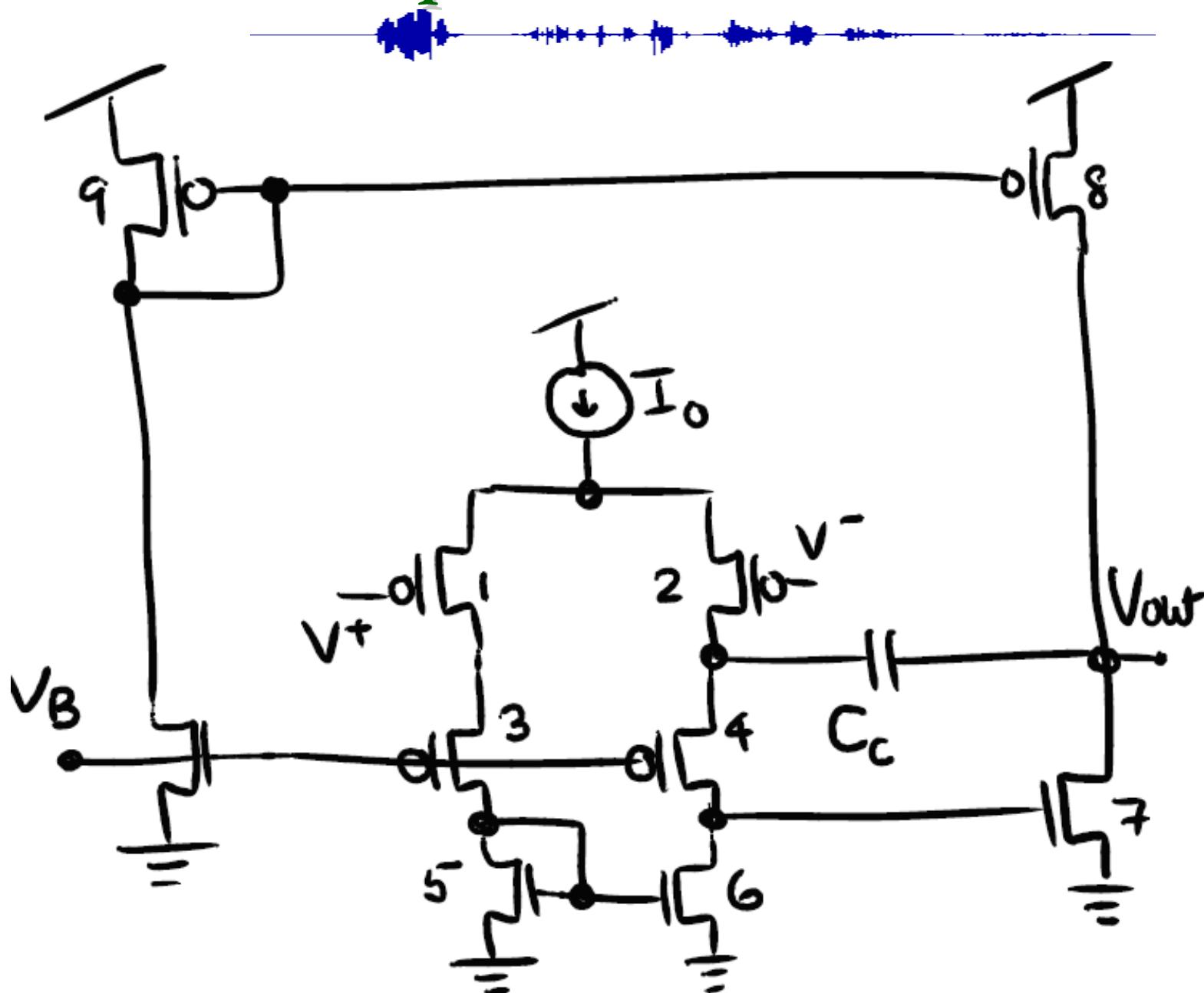

Noise analysis in a feedback network

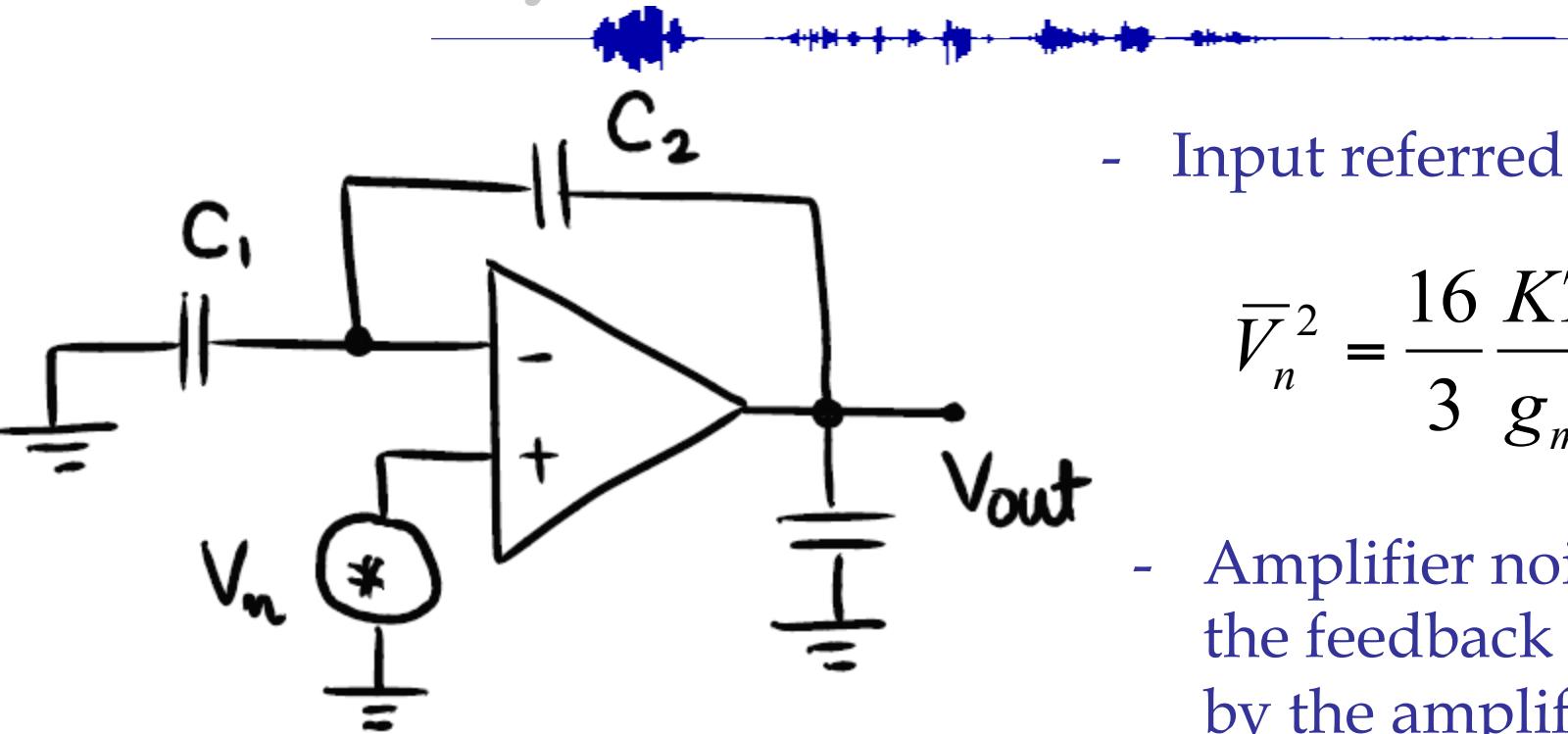


- Input referred amplifier noise
- Amplifier noise is filtered by the feedback system formed by the amplifier, C_1 and C_2 .
- Open loop amplifier - single pole
- Feedback amplifier with capacitor feedback.

$$H_{amp}(s) = \frac{g_m}{2g_d} \frac{1}{(1 + \frac{sC_L}{2g_d})} (V_{in}^+ - V_{in}^-)$$

$$H(s) = \frac{(1 + C_1 / C_2)}{1 + s[C_L / (1 + C_1 / C_2)g_m]}$$

Noise analysis in a feedback network

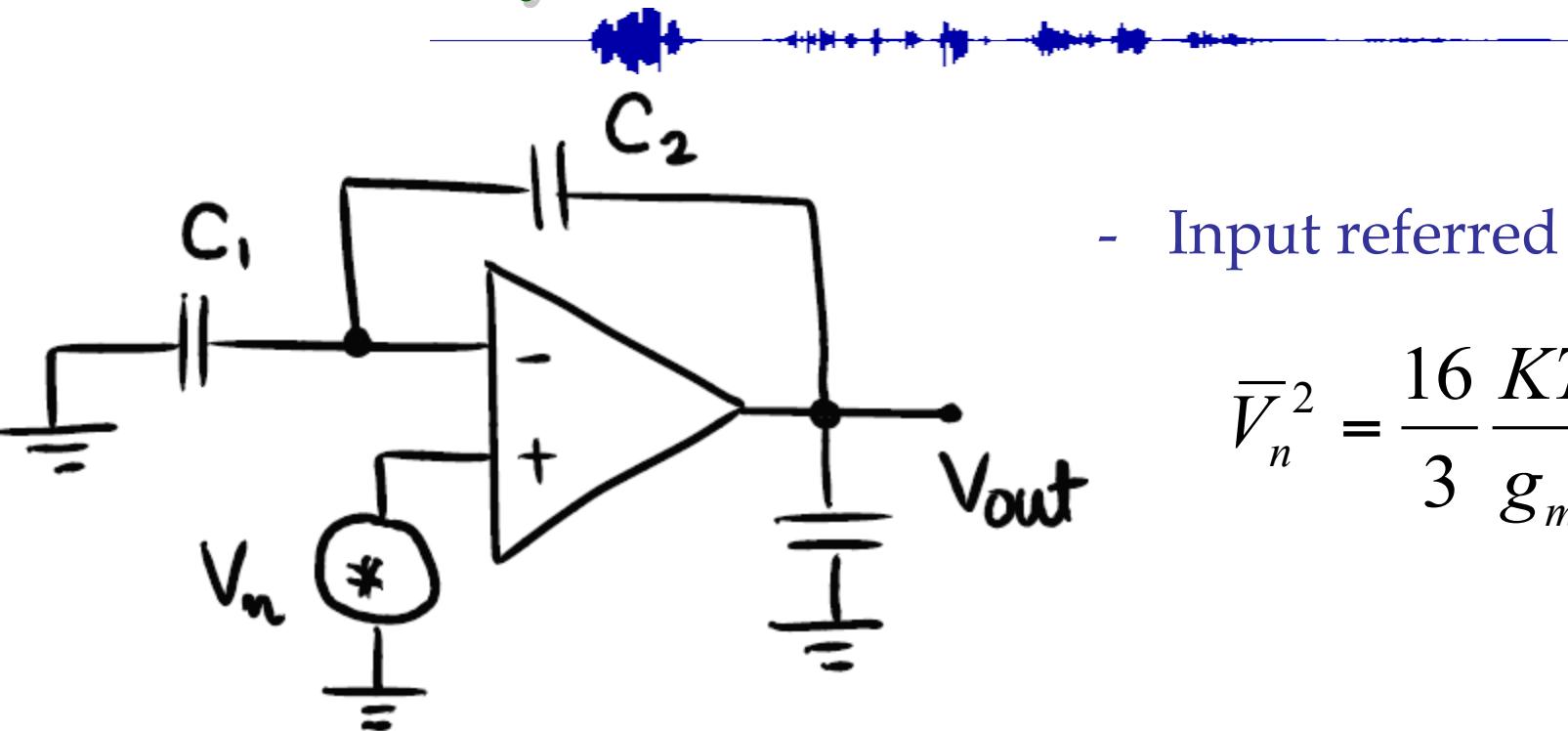

- Input referred amplifier noise



$$\bar{V}_n^2 = \frac{16}{3} \frac{KT}{g_{m1}} \left(1 + \frac{g_{m3}}{g_{m1}} \right) \Delta f$$

- Output noise due to input referred amplifier noise.

$$\bar{V}_{out1}^2 = \int_0^\infty |H(f)|^2 \frac{16KT}{3g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}} \right) df = \frac{4KT}{3C_L} \left(1 + \frac{C_1}{C_2} \right) \left(1 + \frac{g_{m2}}{g_{m1}} \right)$$



Sampled White Noise

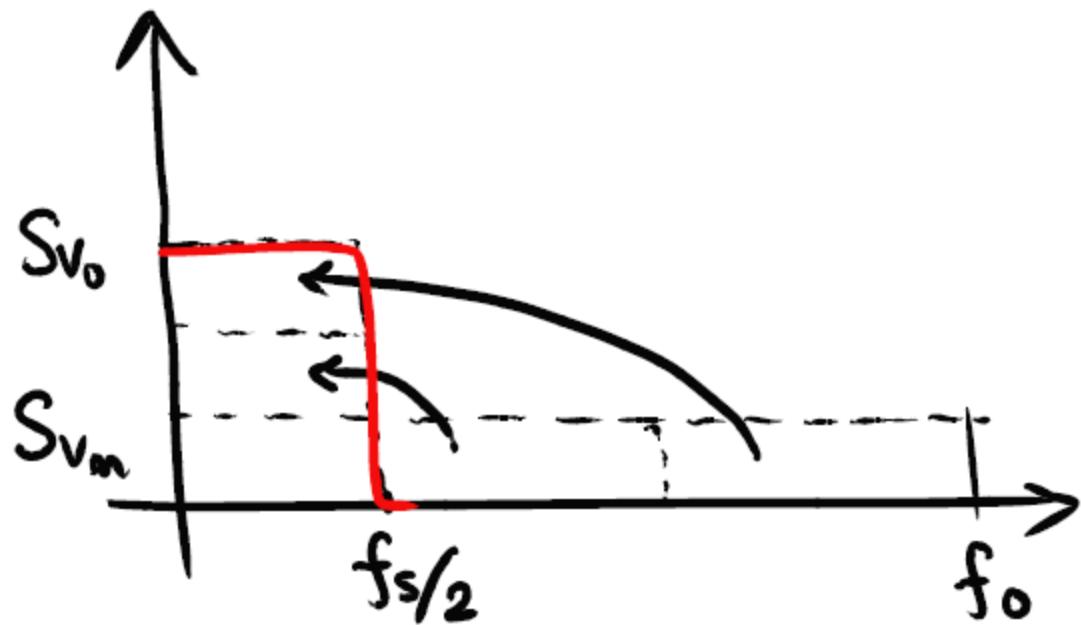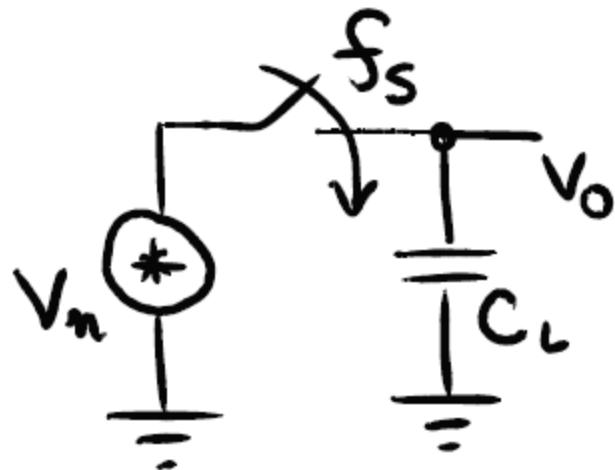


- After sampling the energy should still be conserved.
- Magnitude of sampled noise is larger but bandwidth smaller.

$$S_{v_n} f_0 = S_{v_0} \frac{f_s}{2}$$



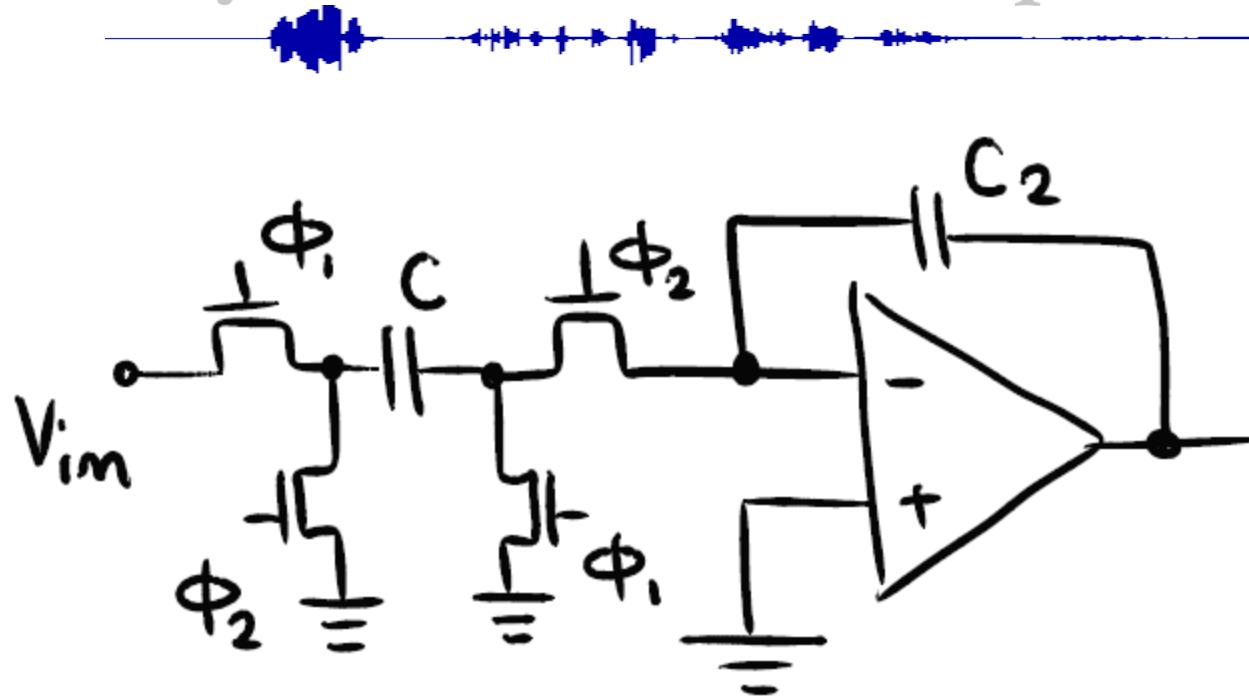
Noise Analysis of Switched Capacitor Circuits



- Fundamental noise in switched capacitor due to sampling noise on the capacitors.
- Noise due to the amplifier also contributes to the output noise.
- Fundamental noise typically smaller than other interference - clock feedthrough, channel charge injection (discussed later).



Phase I

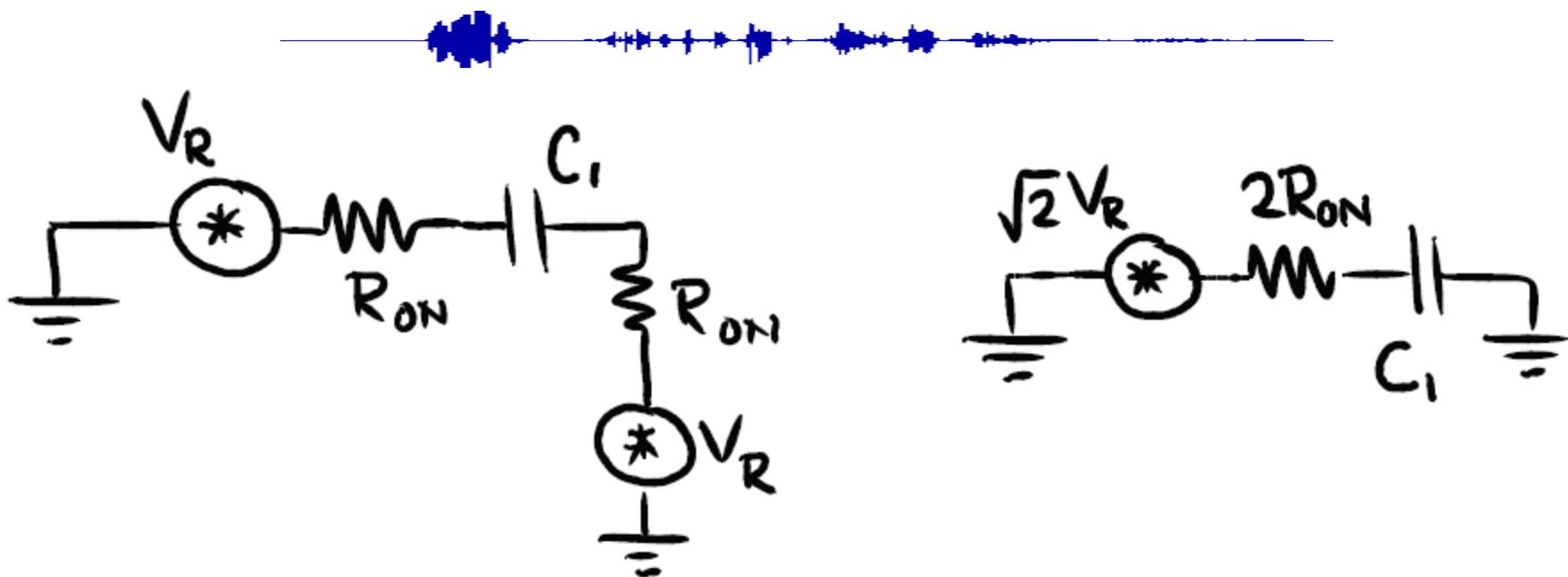

- Two switches form two noise sources which is integrated on the capacitor.


$$S_{C1}(f) = \frac{8KTR_{ON}}{1 + (4\pi f R_{ON} C_1)^2}$$

$$\overline{V}_{C1}^2 = \int_0^{\infty} S_{C1}(f) df = \int_0^{\infty} \frac{8KTR_{ON}}{1 + (4\pi f R_{ON} C_1)^2} df = \frac{8KTR_{ON}}{8R_{ON}C_1} = \frac{KT}{C_1}$$

- The noise sampled in phase I remains stored on the capacitor.



Phase II noise

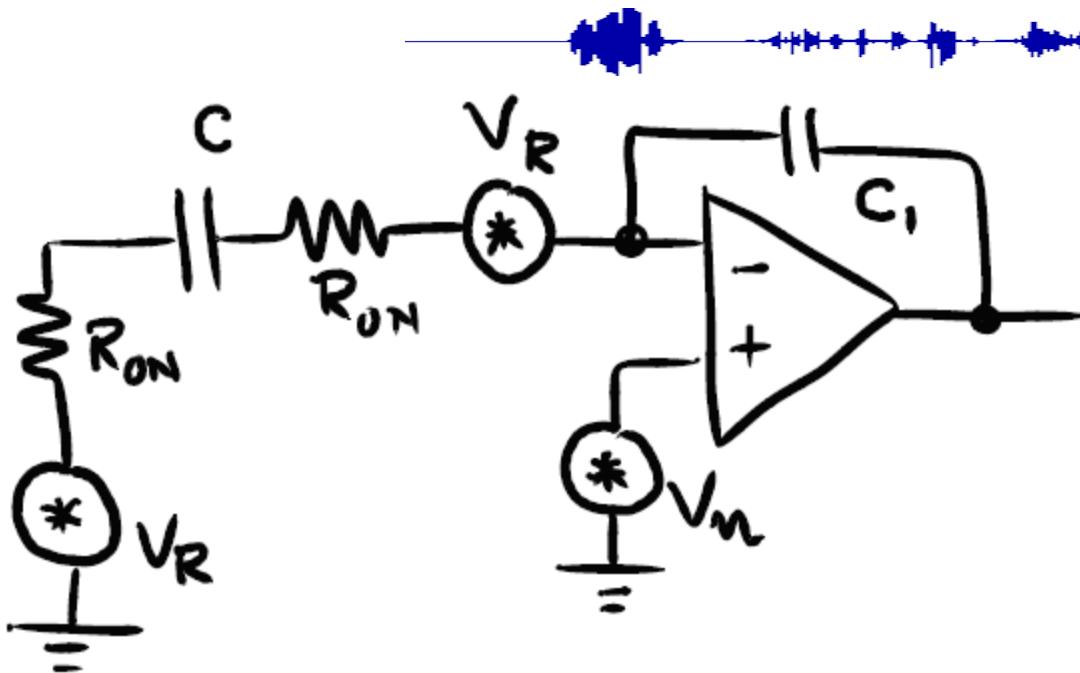

- Switch noise

$$S_{sw}(f) = 8KTR_{ON}$$

- Amplifier noise

$$S_{amp}(s) = \frac{16}{3} \frac{KT}{g_{m1}} \left(1 + \frac{g_{m3}}{g_{m1}} \right)$$


- Filter transfer function

$$H(s) = \frac{1}{(1 + s[2R_{ON} + 1/g_{m1}]C_1)}$$

- Integrate all the noise sources over the entire spectrum

$$\bar{V}_{sw,amp}^2 = \int_0^{\infty} |H(f)|^2 Adf = \frac{A}{4(2R_{ON} + 1/g_{m1})C_1}$$

Output Noise in SC integrator

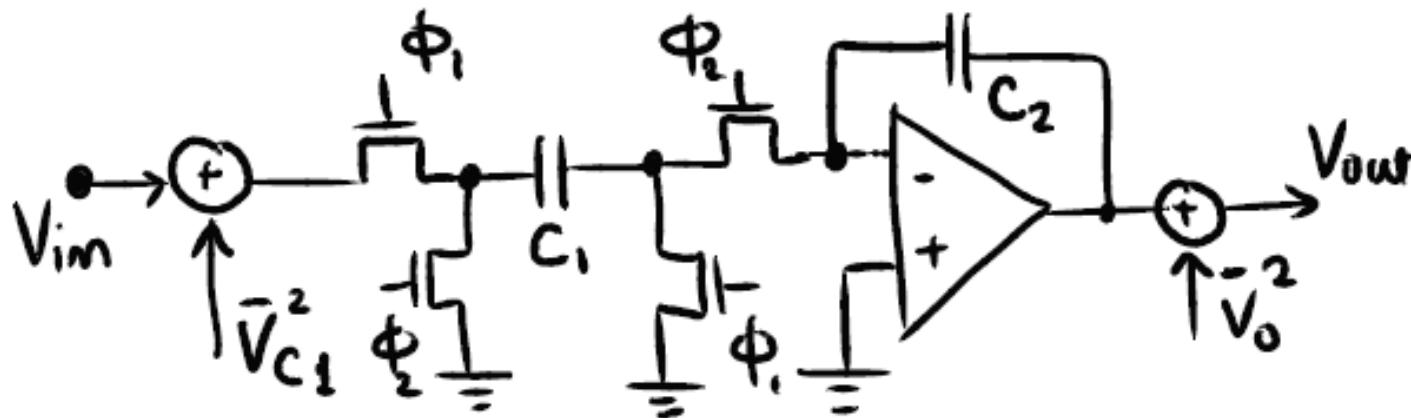

- Transfer function of the integrator


$$\bar{V}_{\text{int}}^2 = \int_0^{f_B} \left(|H(f)|^2 S_{c1}(f) + S_0(f) \right) df$$

- Output noise due to the amplifier.

$$\bar{V}_0^2 = \frac{4KT}{3C_L} \left(1 + \frac{C_1}{C_2} \right) \left(1 + \frac{g_{m2}}{g_{m1}} \right)$$

- How to get back the power spectrum ? Remember all the noise is sampled and the measurement bandwidth is f_B .

Noise in SC circuits

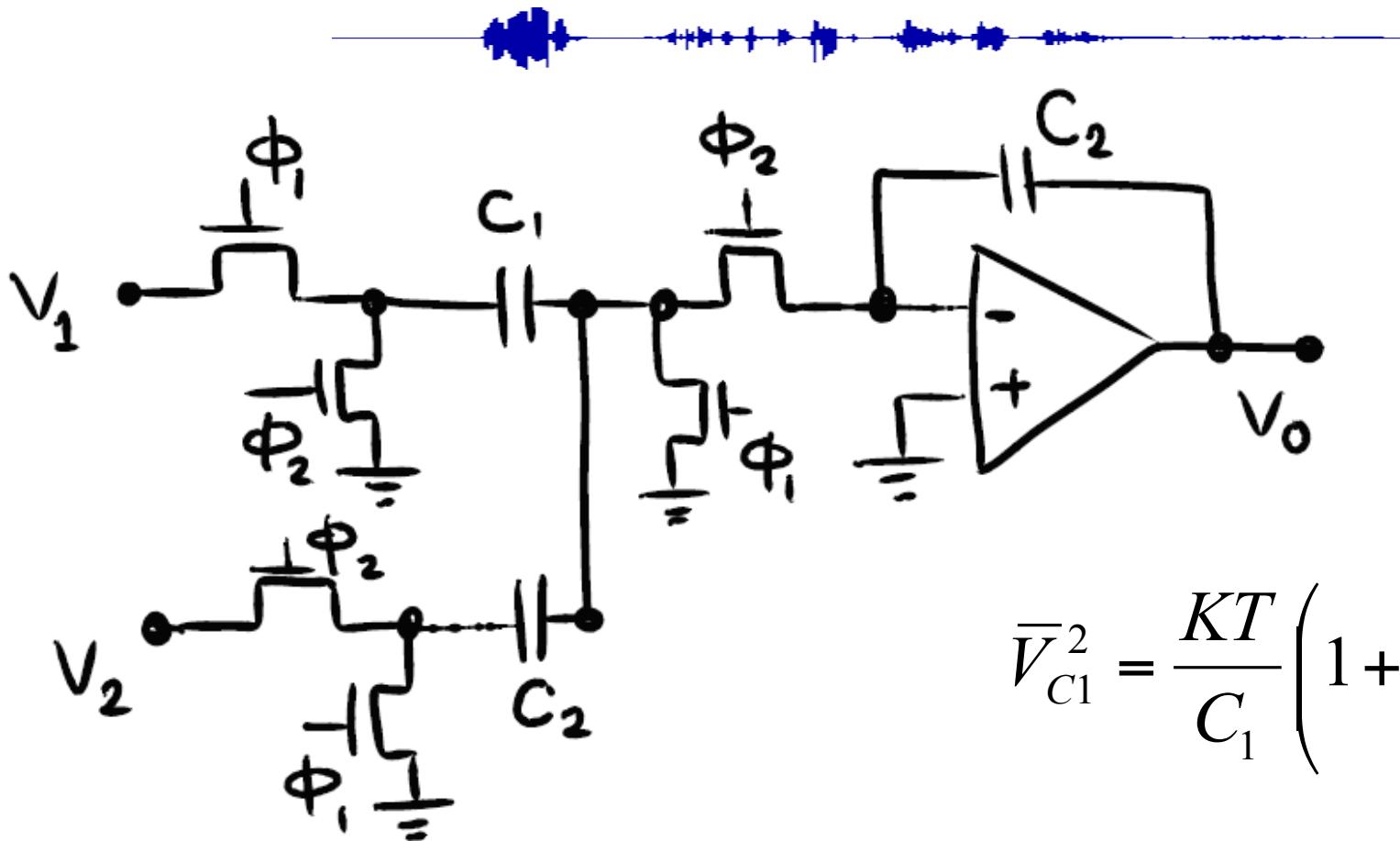


$$\bar{V}_{C1}^2 = \frac{KT}{C_1} \left(1 + \frac{C_{1a}}{C_1} + \dots \right)$$

- Each additional input capacitor adds to the total noise.
- Separate capacitors isolates V_1 and V_2 .



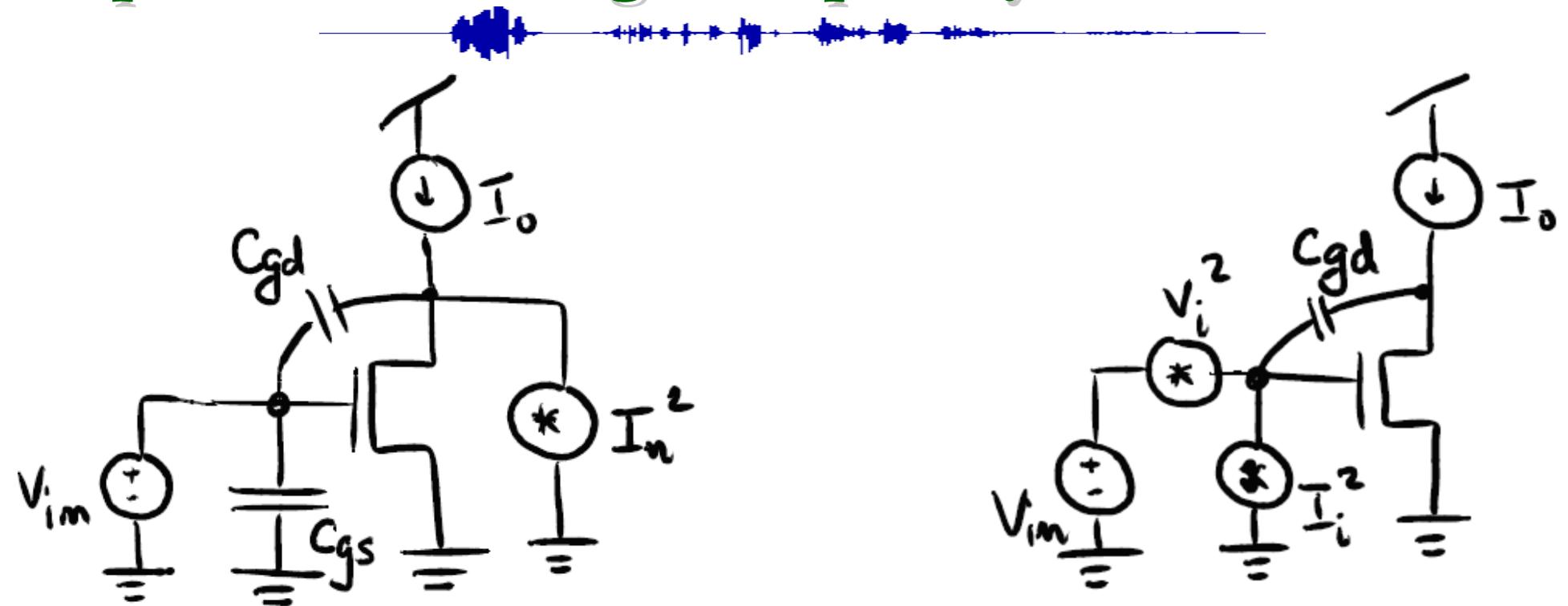Input referred High-frequency Noise Models



- At low frequencies, the gate is an insulator – any gate referred noise can be transformed into output noise through the transconductance.
- At high-frequencies, C_{gs} becomes a short-circuit, so only an input-referred voltage source wont work.
- High-frequency noise models – uses an input referred noise current.

External Noise



- Till now noise was considered to be random with known statistics.
- Localized inside circuit components.
- External Noise - not random but not correlated with the signal.
- Quasi-random - baseline fluctuations superimposed on desired signal.

Problems due to external noise

- Increasing detection threshold - degradation of resolution.
- Important to distinguish between - pickup of spurious signals from local or remote sources, or circuit provides feedback path that causes sustained oscillation - output reaching the input.



Interference Pickup





- **Light pickup**: pn junctions act as a photo-diode - pickup from the ambient light sources. Light pick-up in photomultiplier tubes, semiconductor detectors
- Interference is correlated with power line frequency- twice the line frequency - light intensity proportional to voltage square.
- **Solution**: switch off light, light shield
- **Vibration pickup**: Two capacitor plates at different potentials are susceptible to noise due to displacement currents. Signature: Look for harmonics in the signals at specific frequencies.
- **Solution**: Anti-vibration shield, coaxial shield to maintain zero potential difference or provide a path for the displacement current to easily flow away from the circuit.
- **RF pickup**: Everything is an antenna - goal is to make the circuit of interest a bad antenna.



Electrical Interference




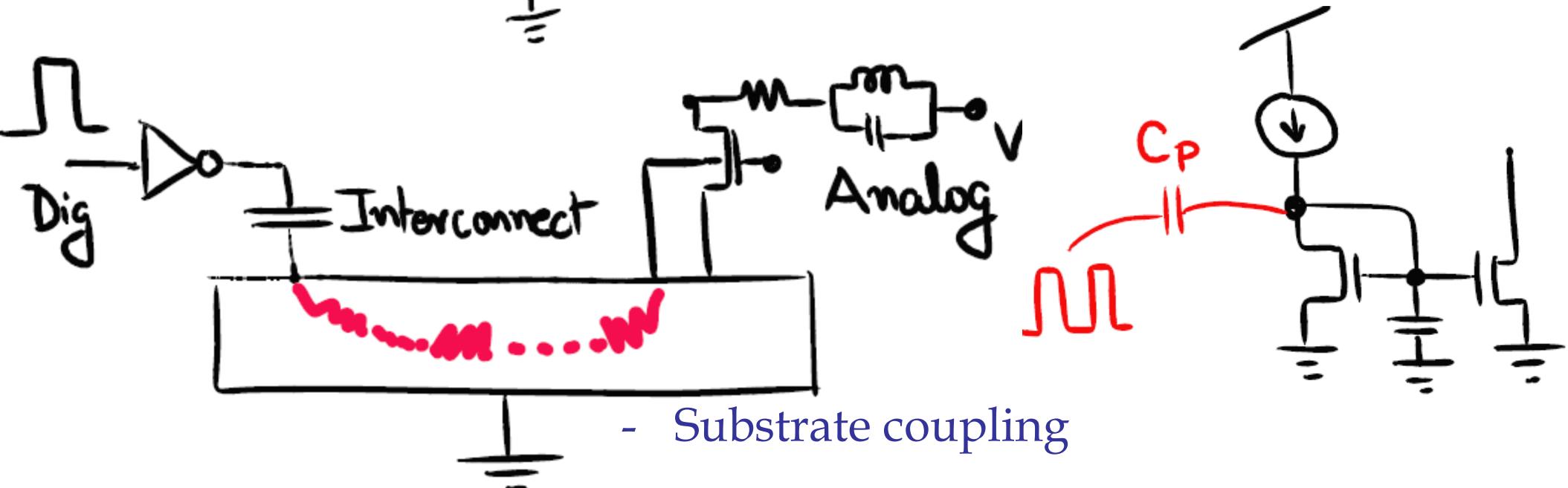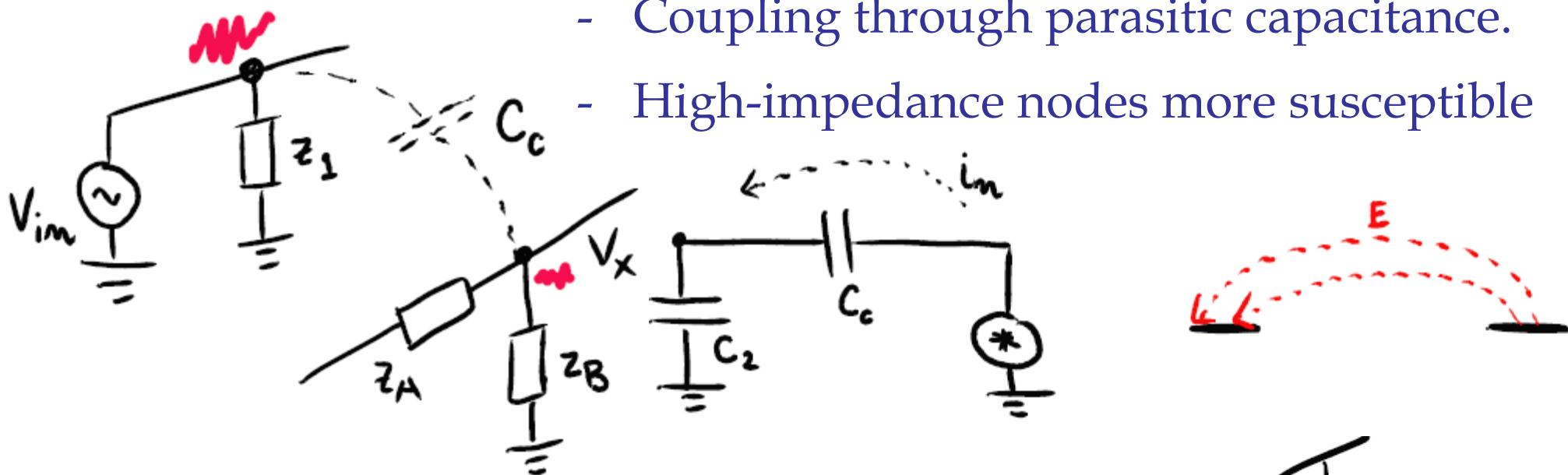- Coupling through parasitic capacitance.
- High-impedance nodes more susceptible




- Substrate coupling


Shielding

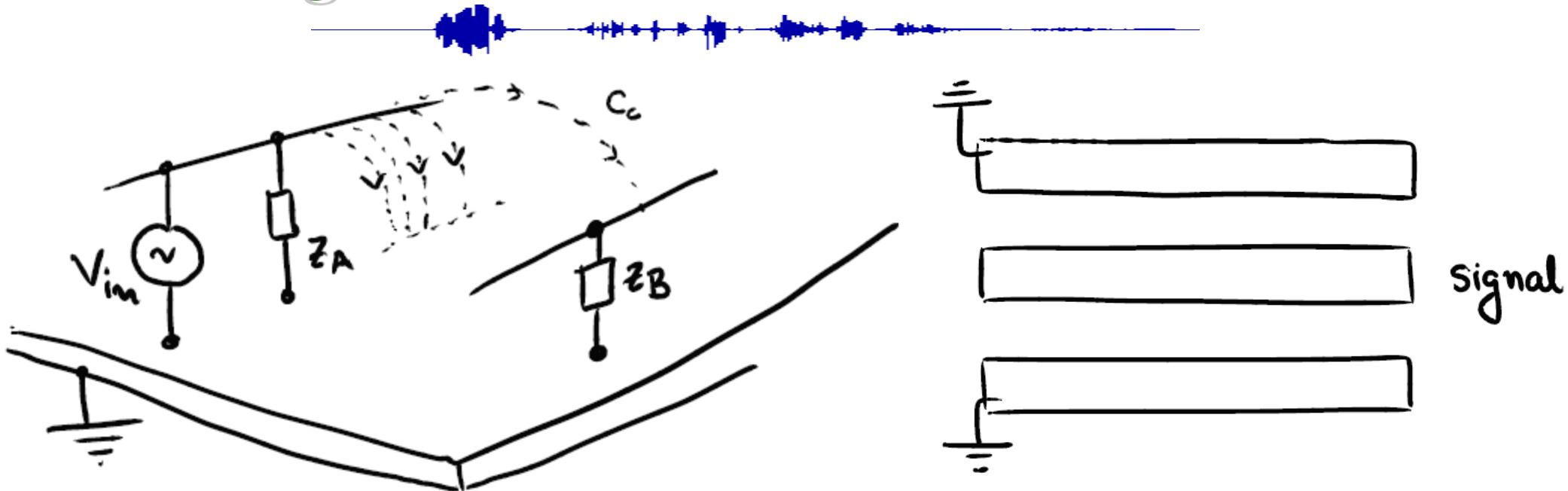


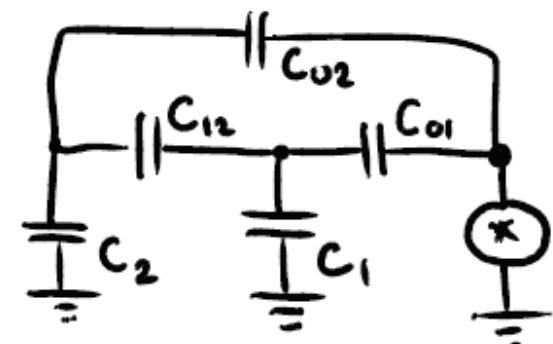
- Introduce a low-impedance node in between the interference and signal node.
- Use ground planes to capture fringing electric fields.





Faraday Cages

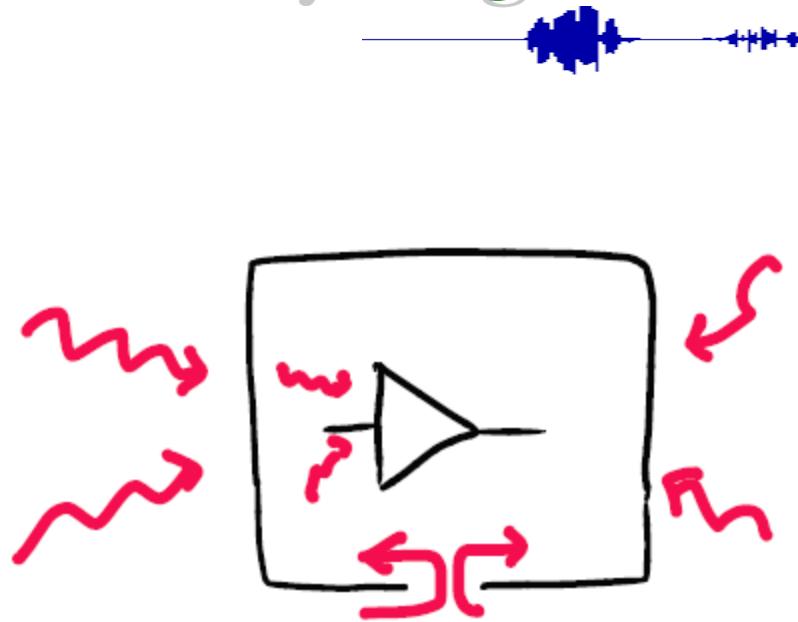

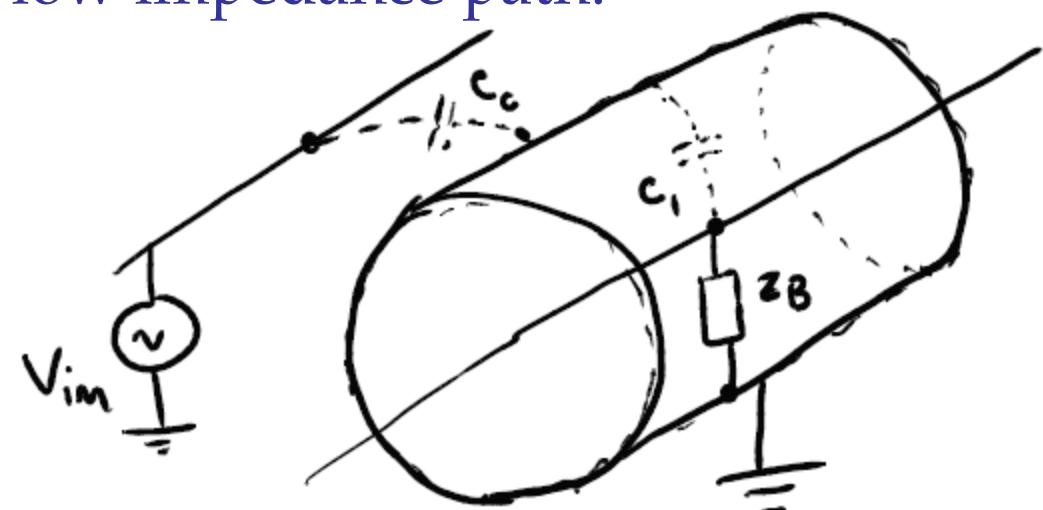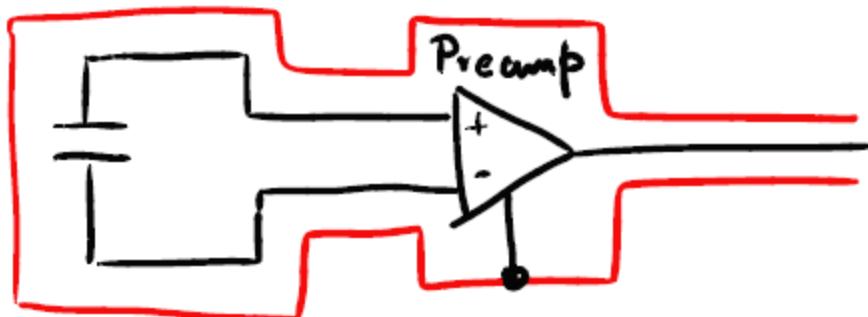- Completely surround the circuit by a thick conductor.
- Thickness greater than the skin depth.
- Holes need to be smaller than $1/10^{\text{th}}$ the wavelength.
- Ground the shield to provide a low impedance path.




Reducing effect of substrate coupling

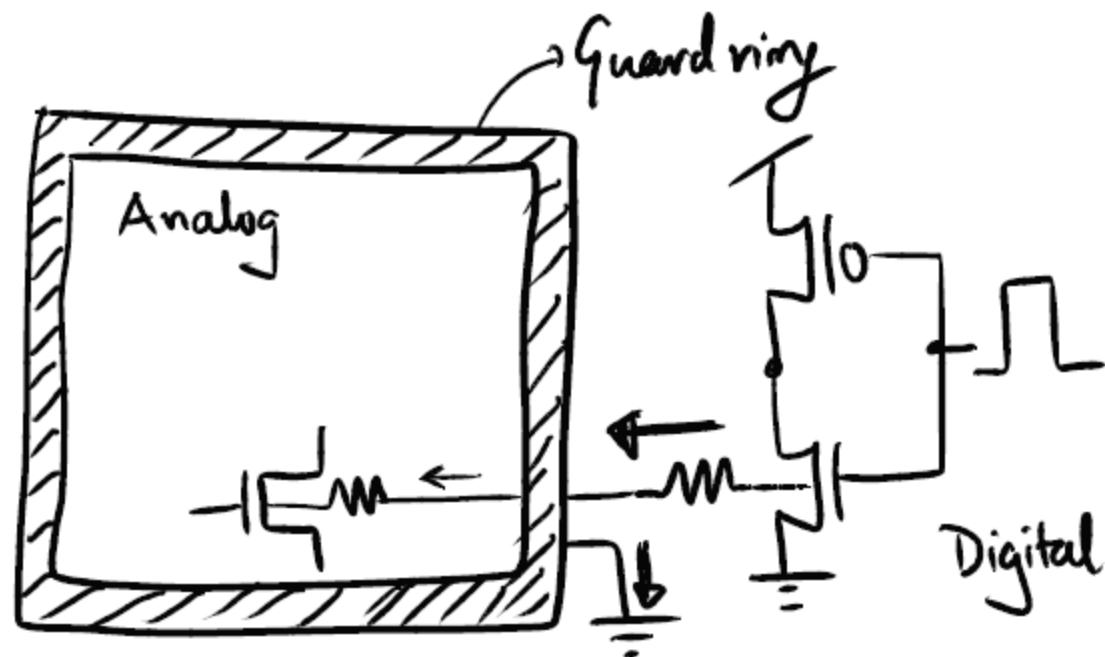
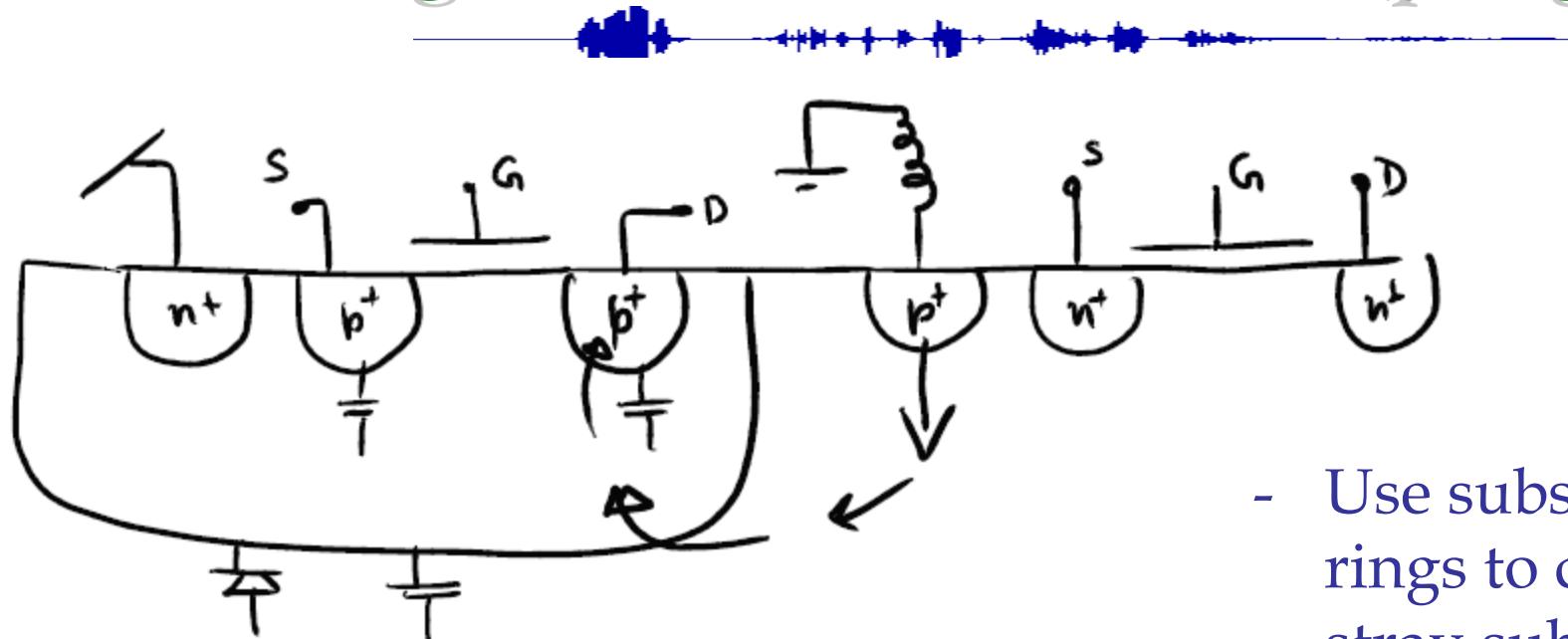


- Use substrate guard rings to capture any stray substrate current.
- Make sure to have a lot of substrate connections. It is difficult to control current that leaks into the substrate.




Magnetic pickup

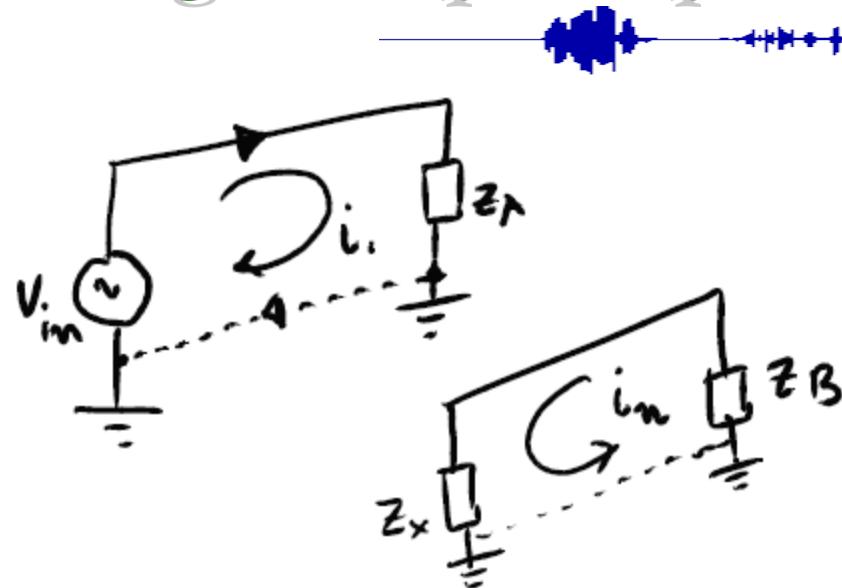

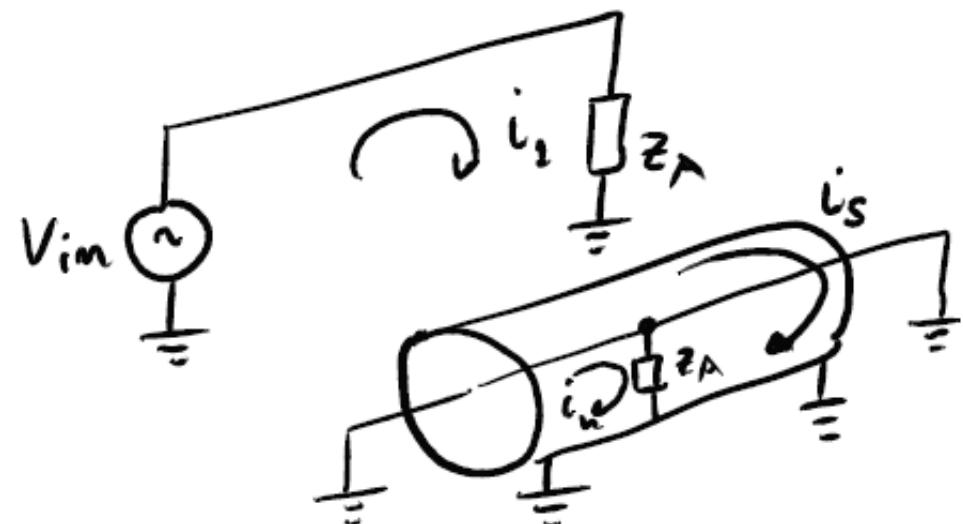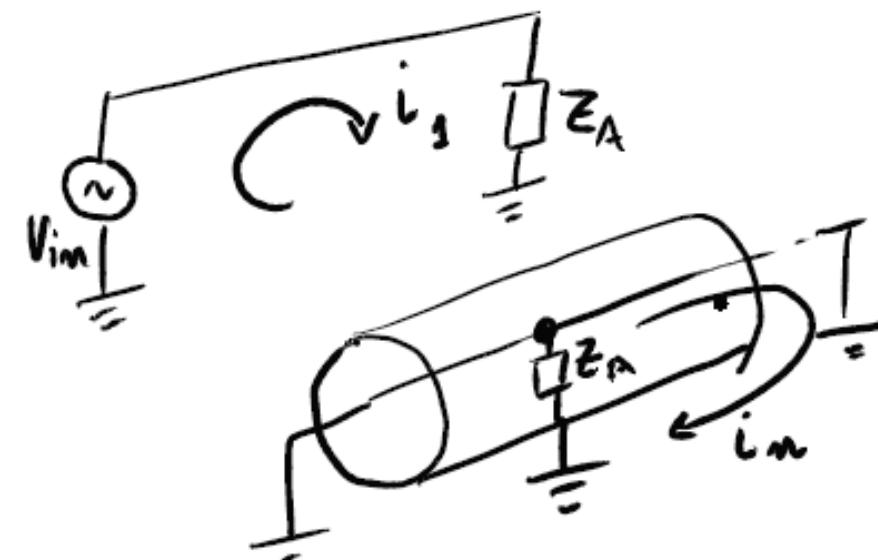- Faraday cage might not be useful for reducing magnetic interference.
- Ground shield at two end points.
- Return current path cancels the effect of interfering current.




Magnetic pickup due to ground loops

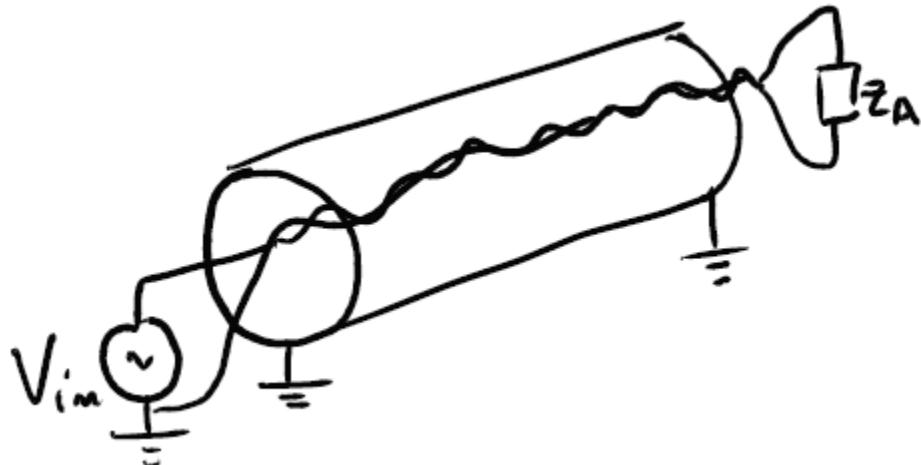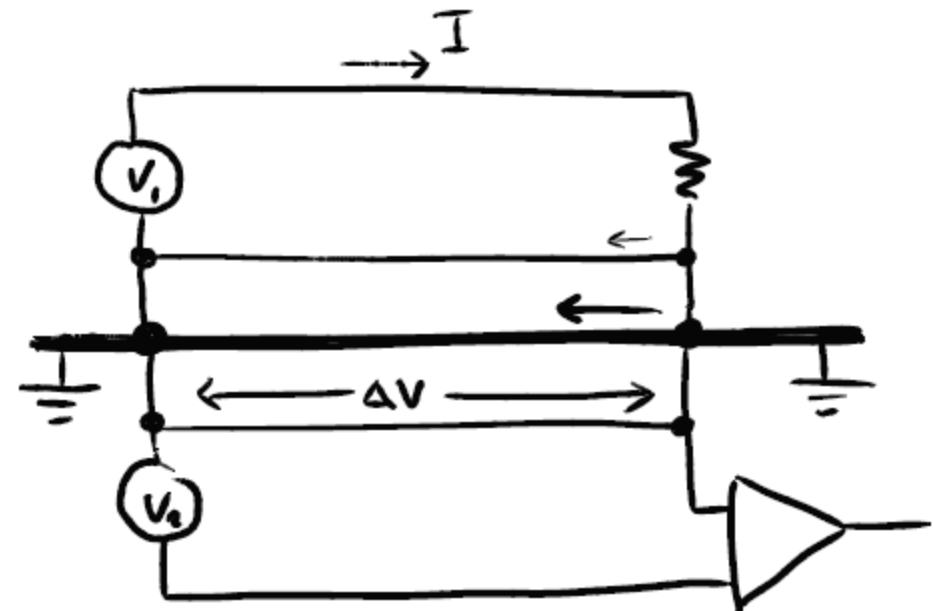
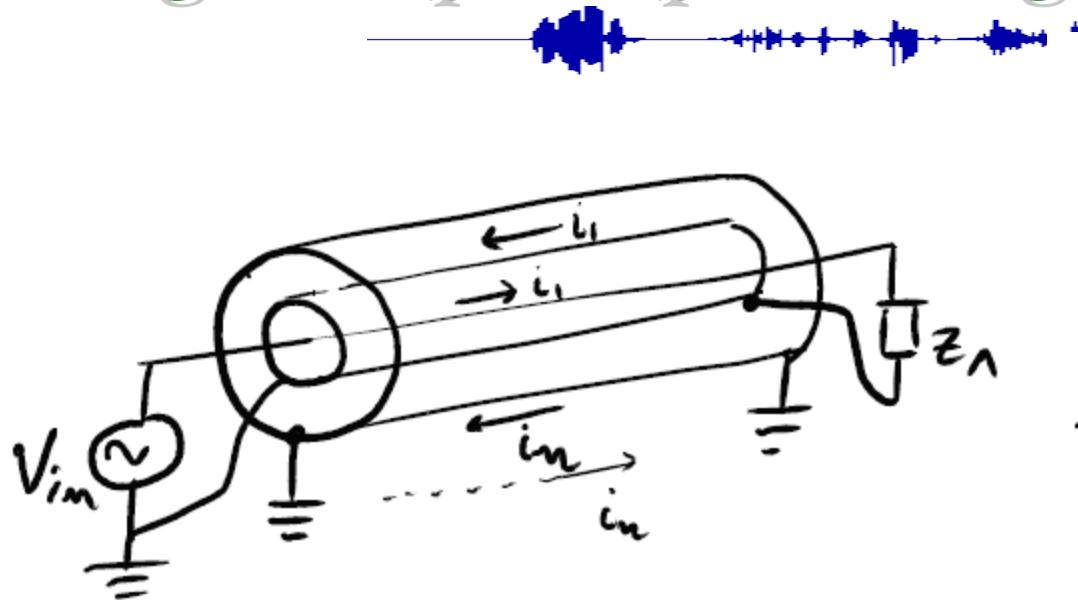


- Provide a separate return current path and not through the ground.
- Use a twisted cable to reduce the magnetic pickup by reducing the effective cross-sectional area.


Ground Noise

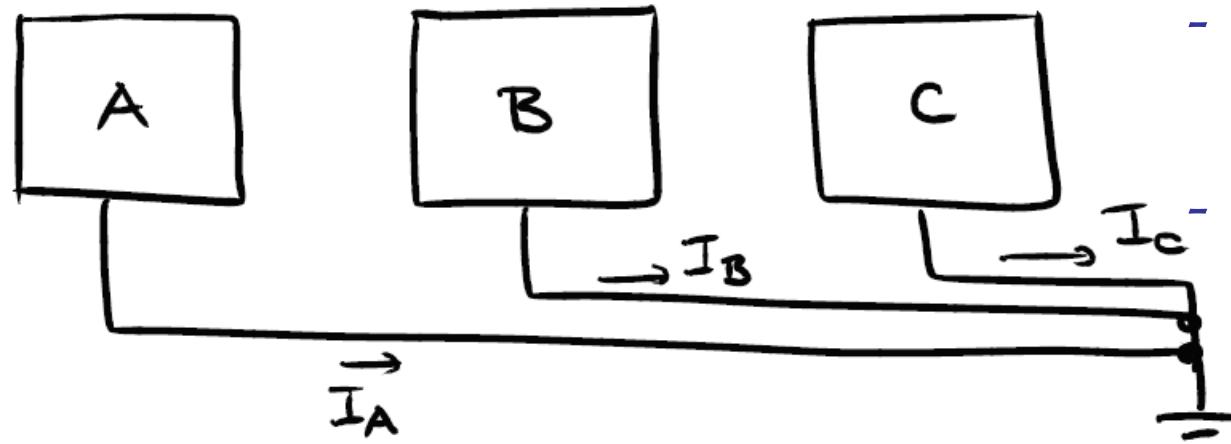

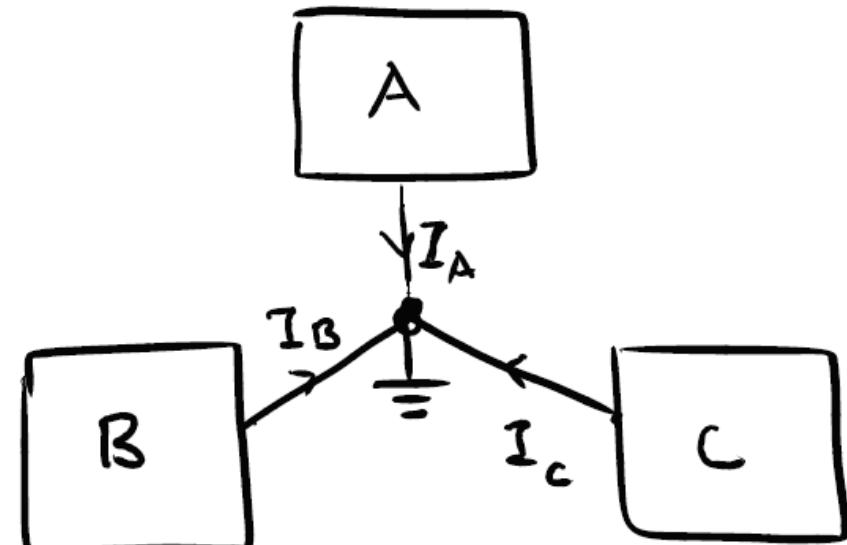
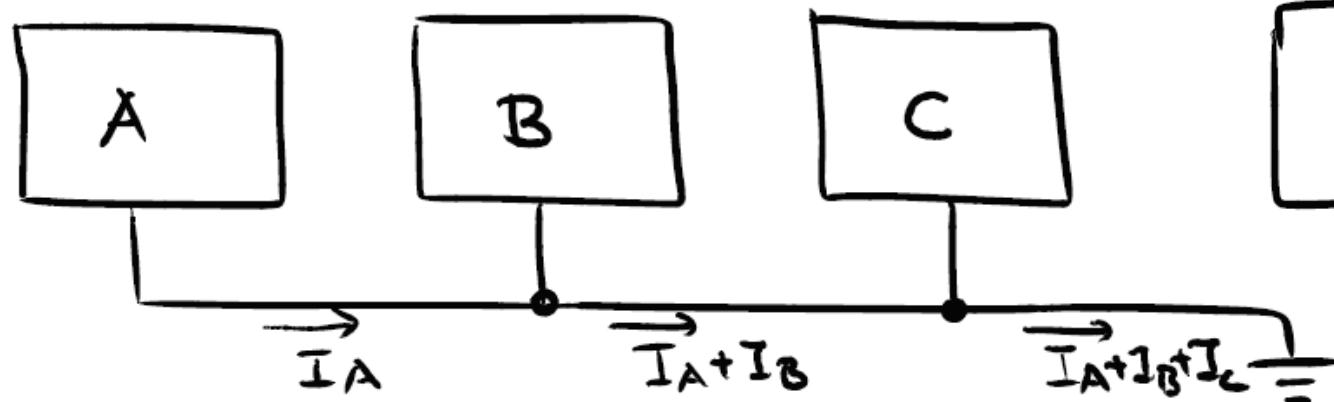
- Ground is never perfect - has a finite resistance.
- Use symmetrical ground connection when possible.




Effect of Ground Noise

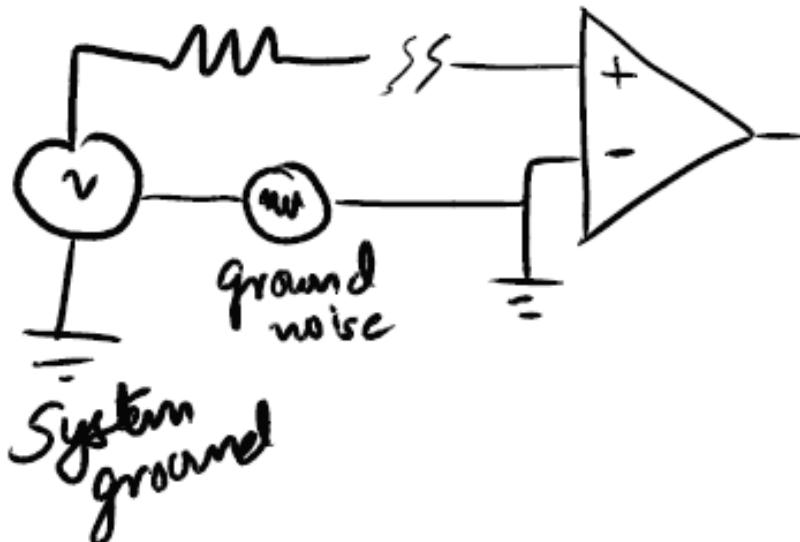


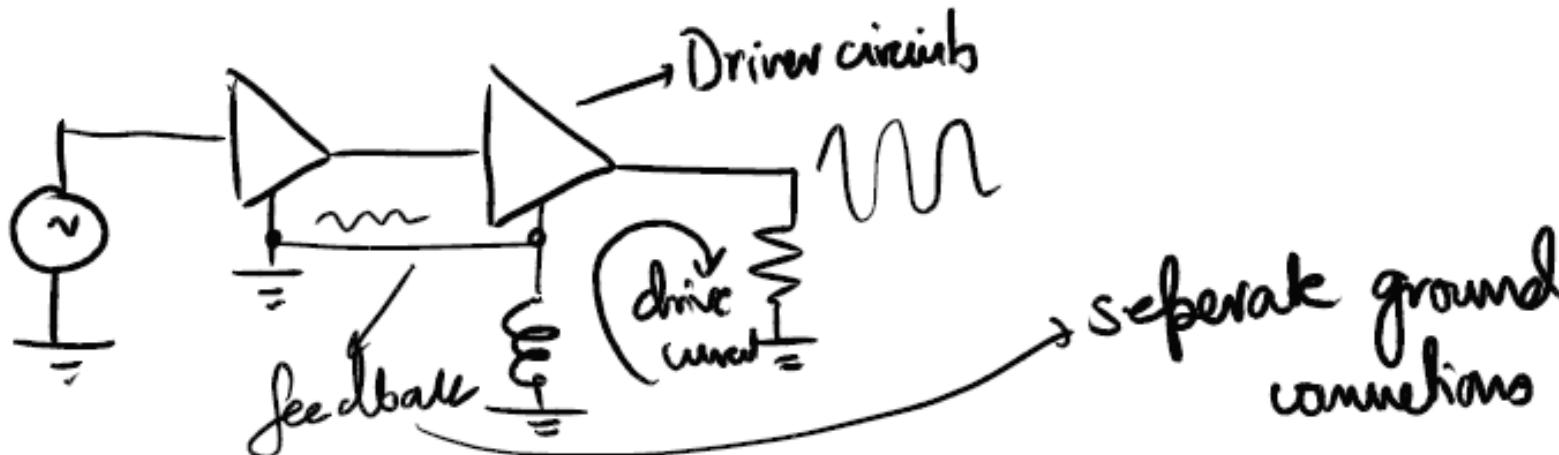
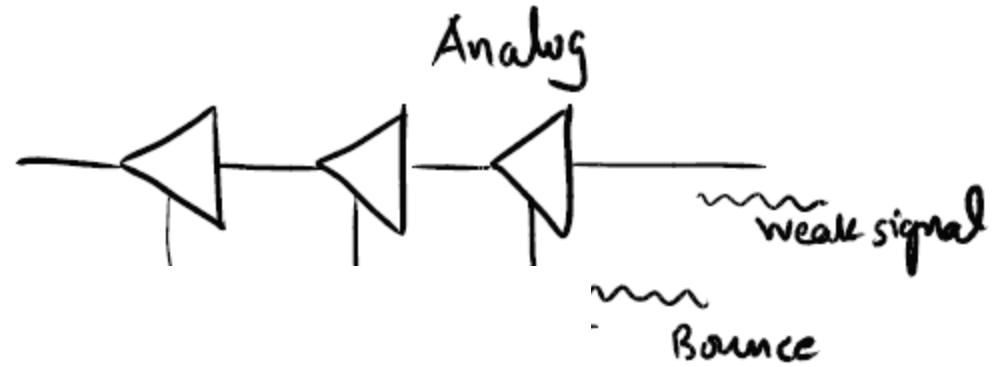
- Reduces signal-to-noise ratio.
- Could induce oscillations due to parasitic feedback.




Reducing effect of ground noise

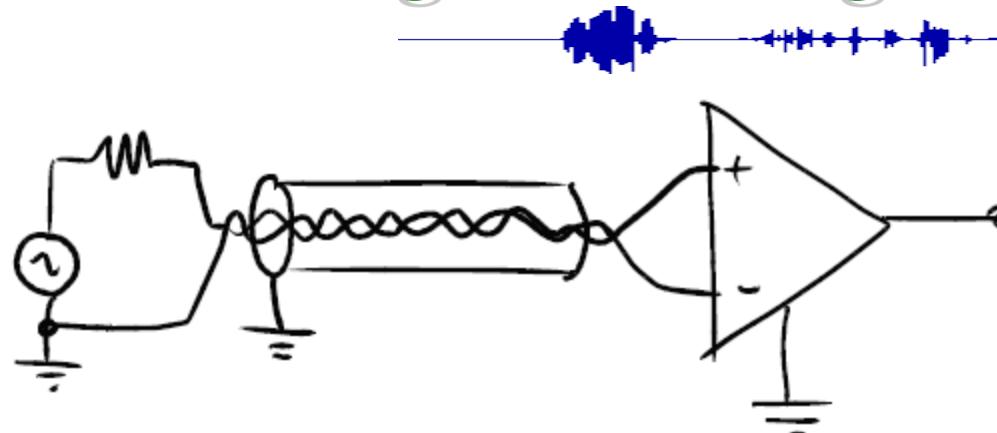

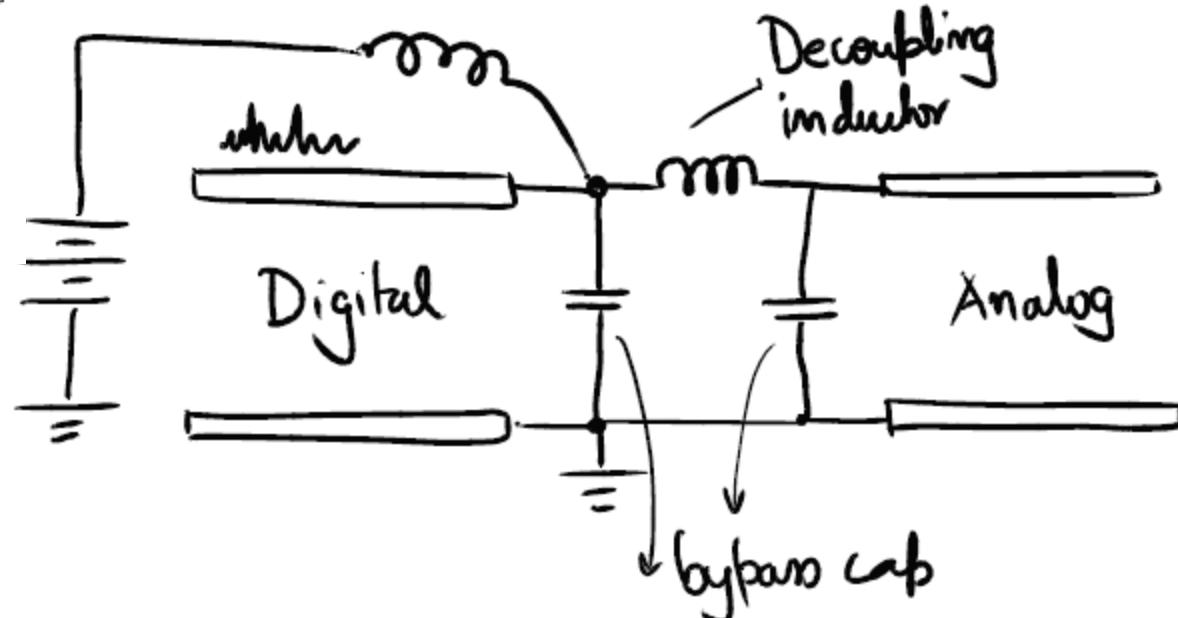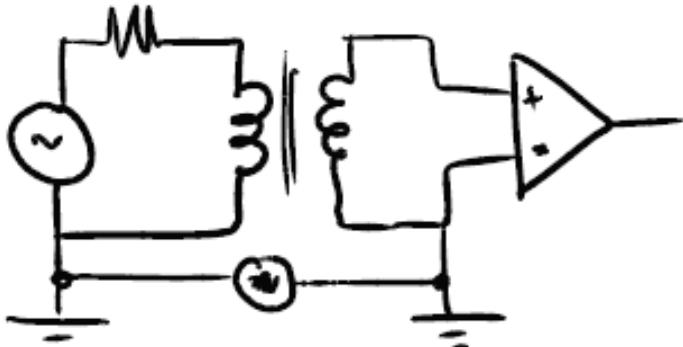
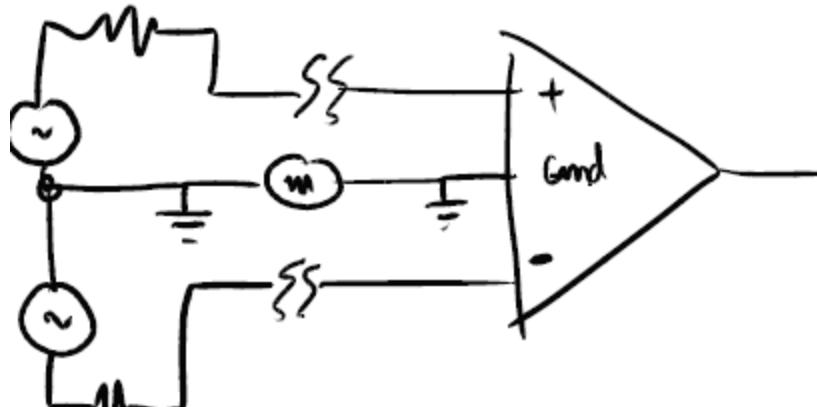
- Provide a separate return path using bypass capacitors.
- Isolate and decouple the ground and supplies.
- Use differential topologies.




Reducing effect of ground noise

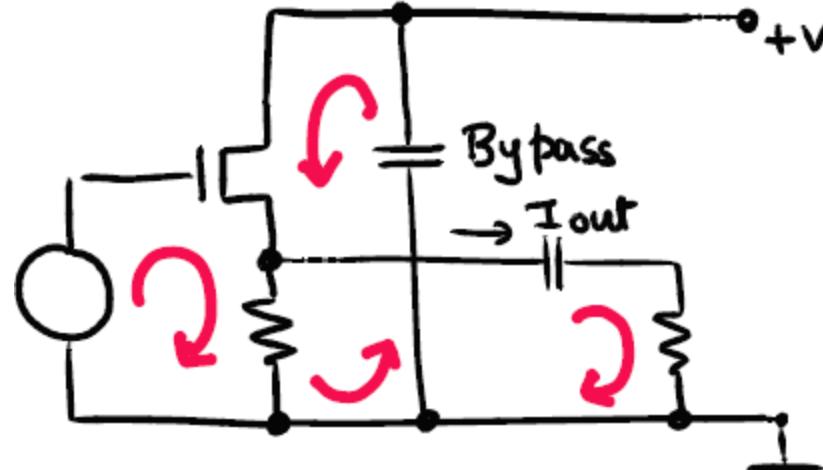

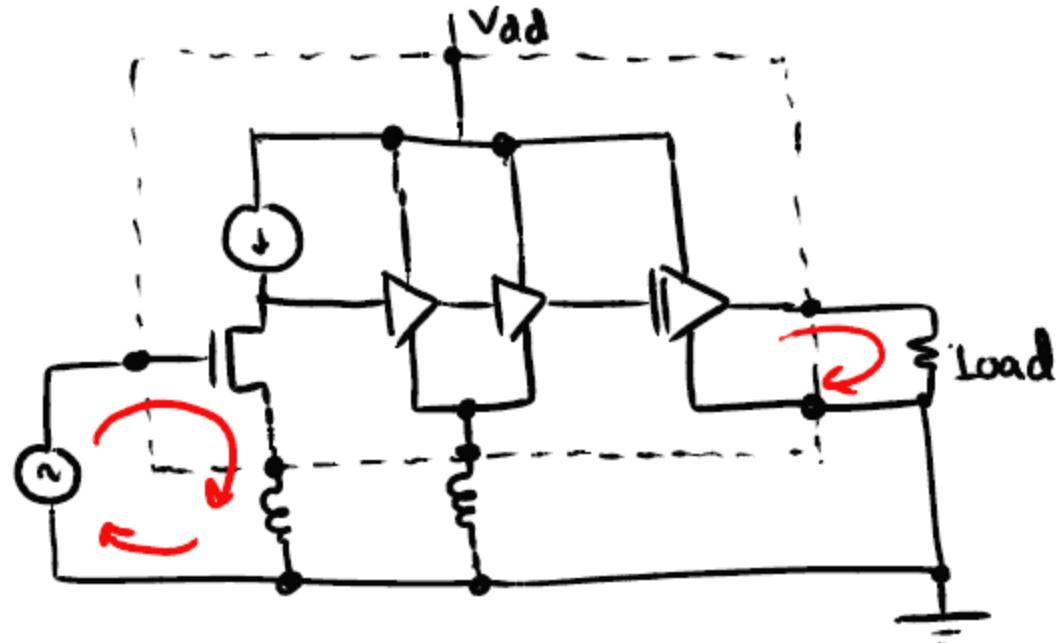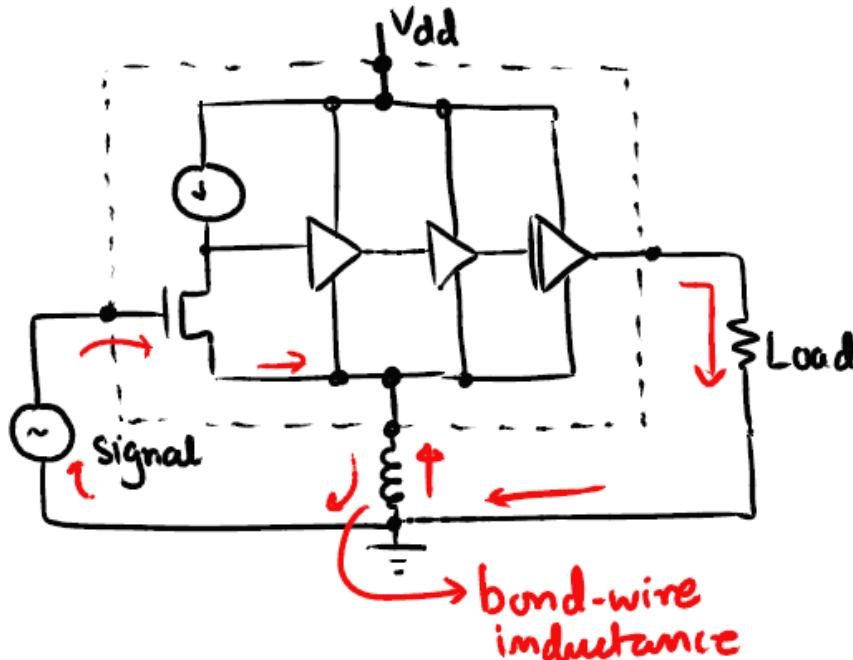- Closer the current return path less is the noise pickup.
- Avoid signal return path through global ground.



Signal connections

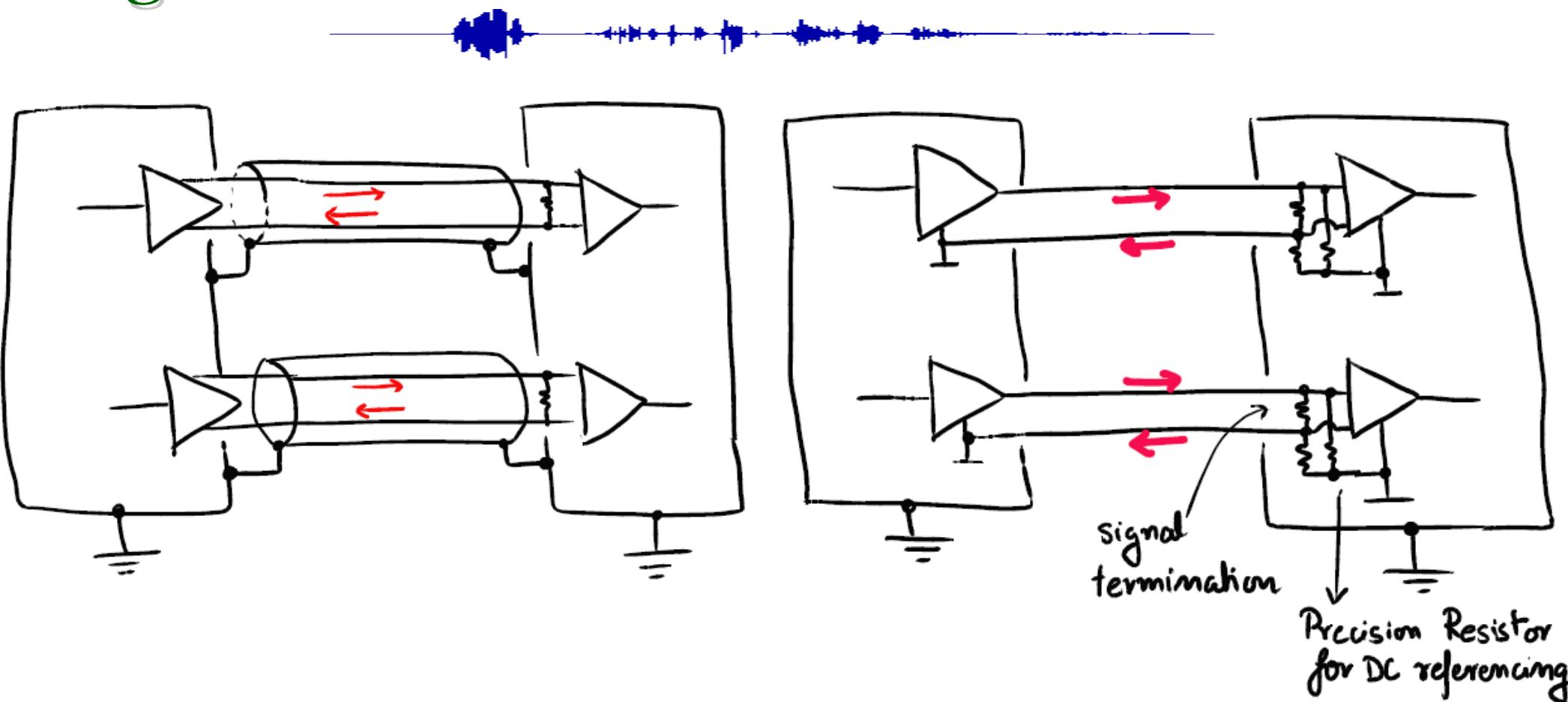

- Signal transmission using a triax.
- Isolate the signal return path using a coax and shield from chassis.

