




Data Converters




CSE562M: Analog Integrated Circuits


Shantanu Chakrabartty

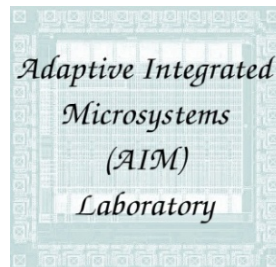

One of the most important blocks

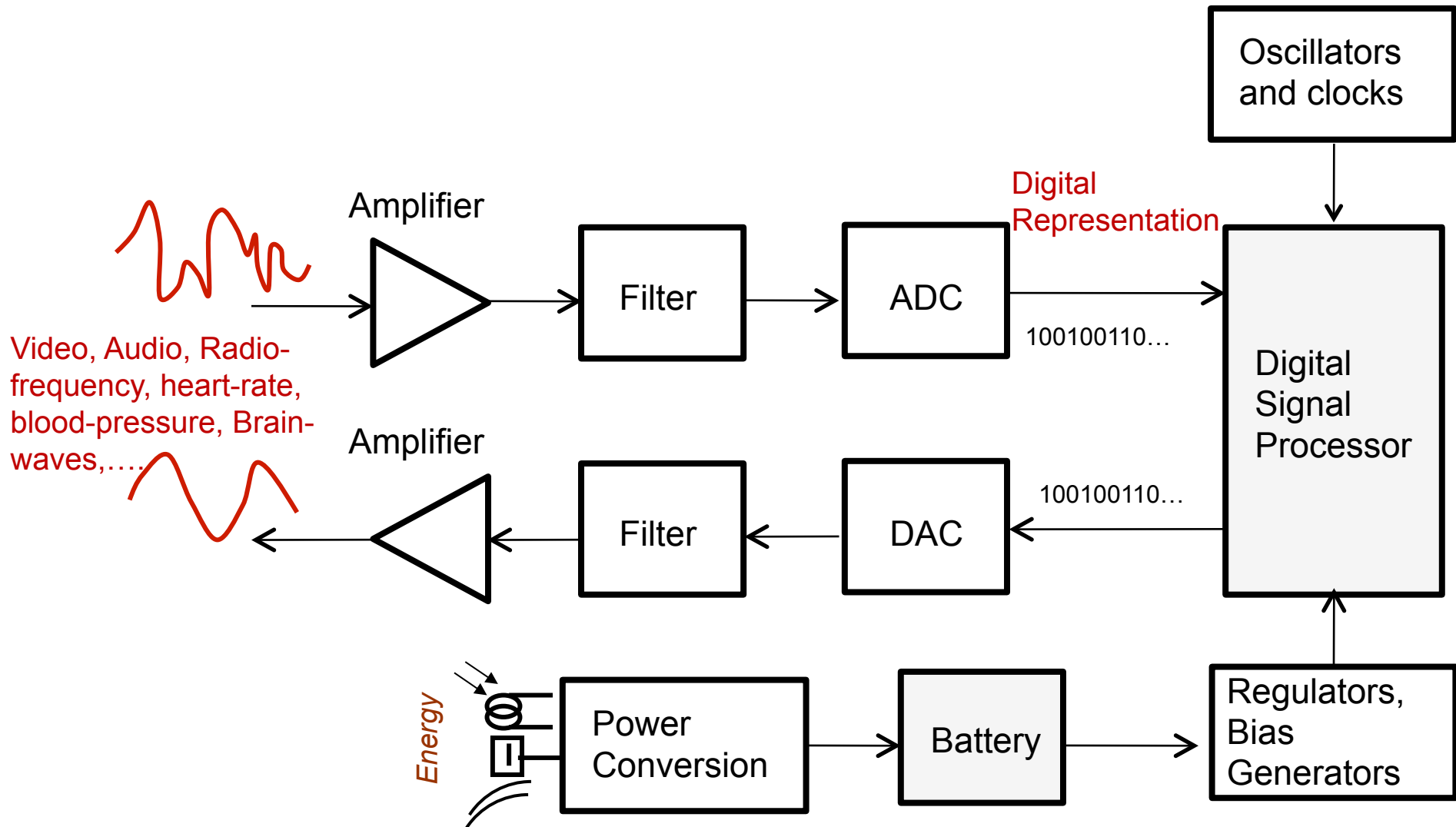


Classification of Data Converters

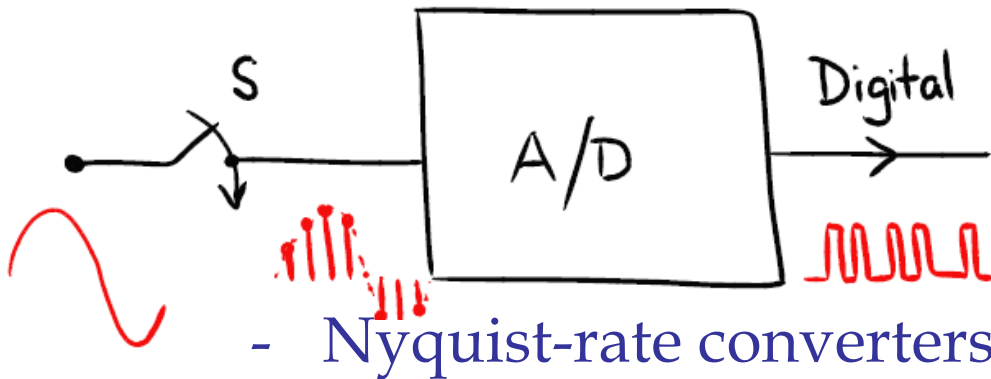


- Classification based on rate of sampling of the analog signal.

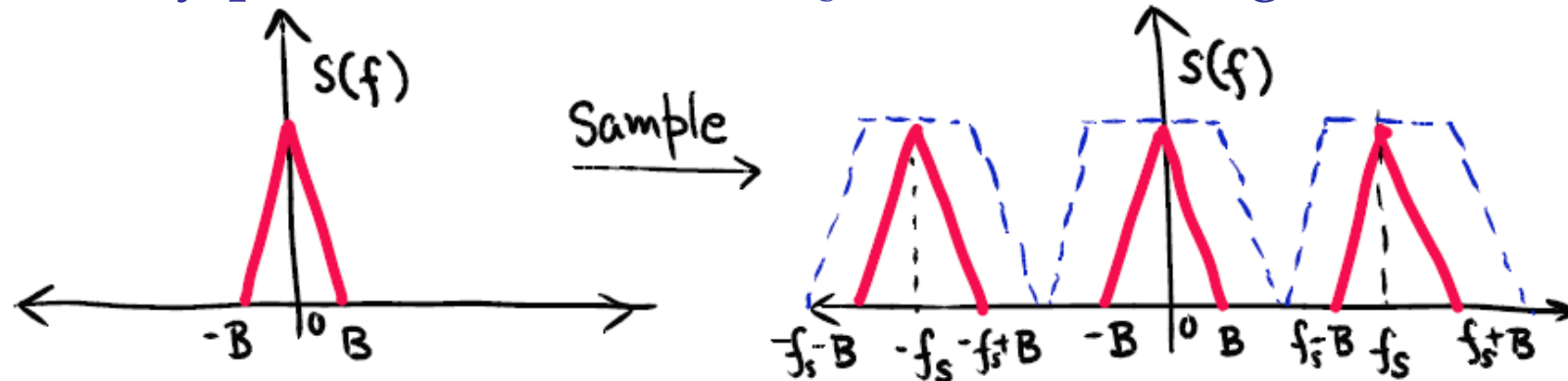- Nyquist-rate converters $f_s = 2\text{--}10$ times signal bandwidth (B)




- Oversampling converters $f_s \gg 2B$

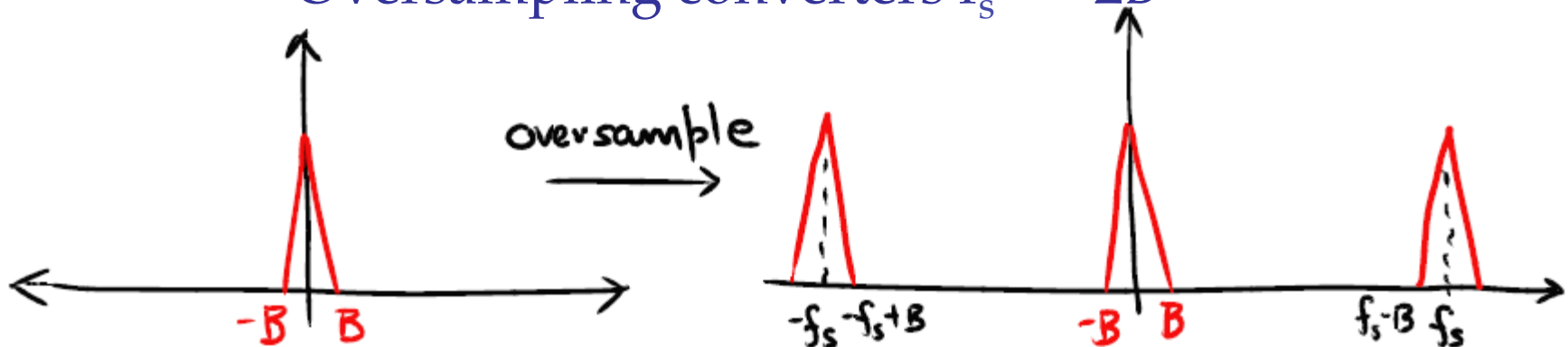

Digital to analog conversion

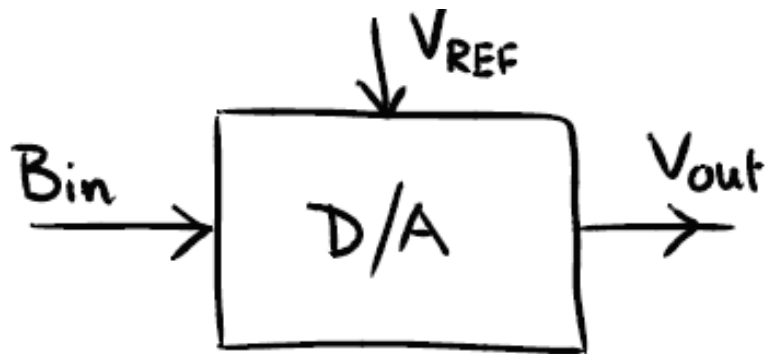- Different binary representations (minimal code, thermometer code, gray code, signed, twos complement, ...).




$$V_{out} = f(b_1, b_2, \dots, b_N) V_{ref}$$

$$B_{out} = \underset{\substack{\nearrow \\ \text{MSB}}}{2^{-1} b_1} + 2^{-2} b_2 + \dots + 2^{-N} \underset{\substack{\nearrow \\ \text{LSB}}}{b_N}$$

MSB


LSB

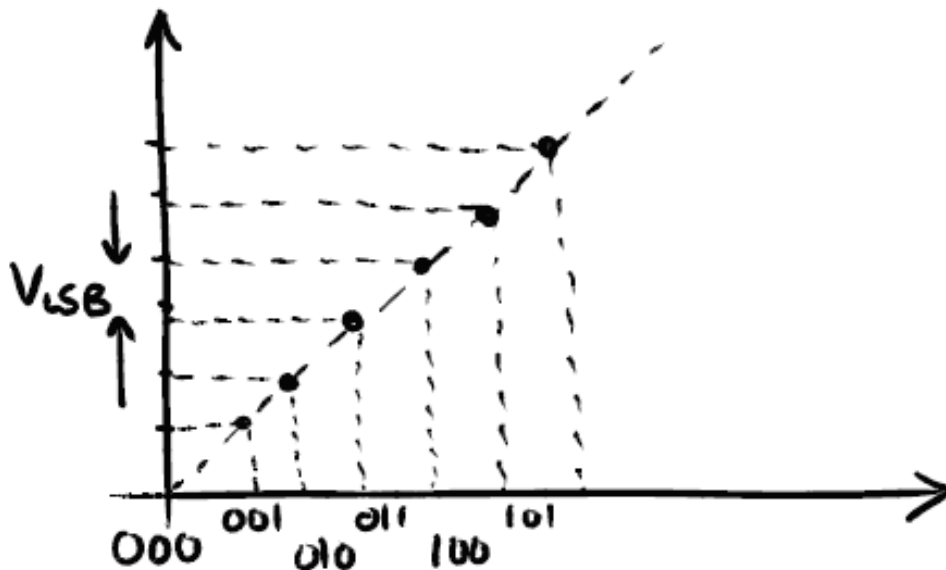

- For each binary input, an ideal DAC produces a unique analog signal output.
- Resolution of the DAC.

$$V_{LSB} = 2^{-N} V_{ref}$$


Analog to Digital Conversion

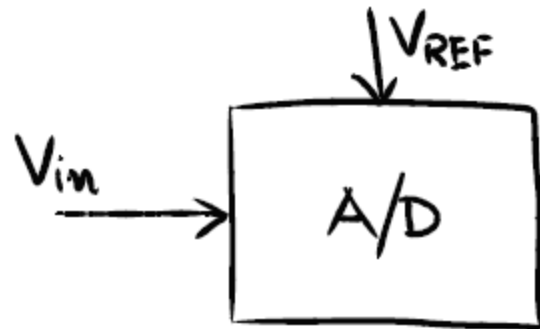

$$B_{out} = \underset{\text{MSB}}{2^{-1}b_1} + 2^{-2}b_2 + \dots + \underset{\text{LSB}}{2^{-N}b_N}$$

$$V_{in} \approx f(b_1, b_2, \dots, b_N) V_{ref}$$

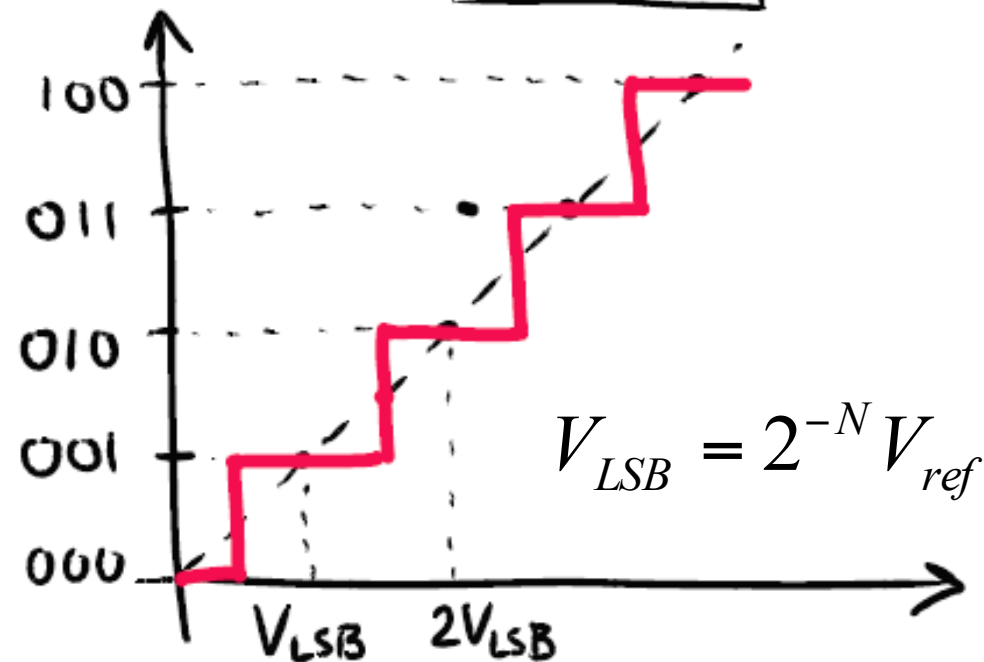- For a set of analog input an ideal ADC produces a unique binary output.
- 3 bit ADC.



- Approximation or resolution of an ideal ADC




$$-\frac{1}{2}V_{LSB} < V_{in} - f(b_1, b_2, \dots, b_N)V_{ref} < \frac{1}{2}V_{LSB}$$

$$-\frac{1}{8}V_{ref} < V_{in} < \frac{7}{8}V_{ref}$$


Quantization Noise



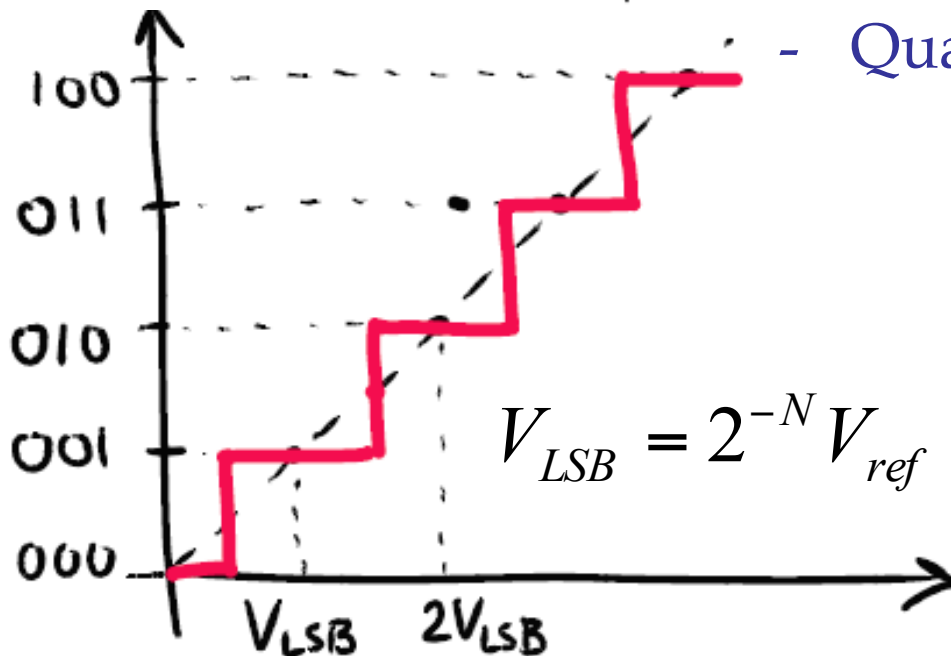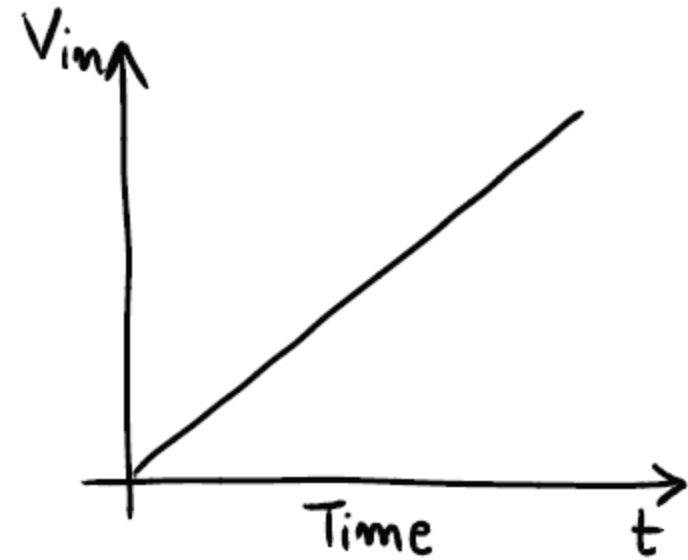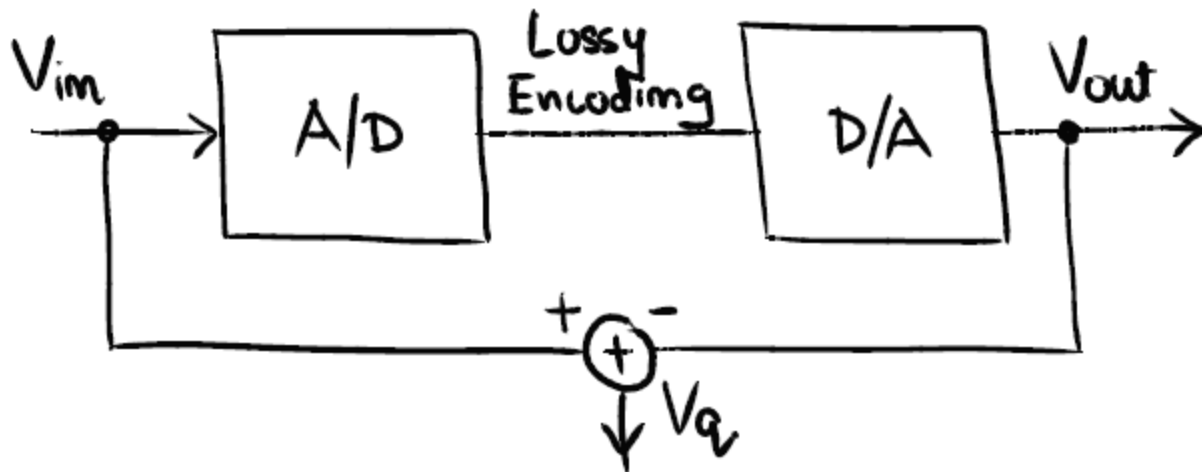
$$V_q = V_{in} - f(b_1, b_2, \dots, b_N) V_{ref}$$




- Quantization error is bounded

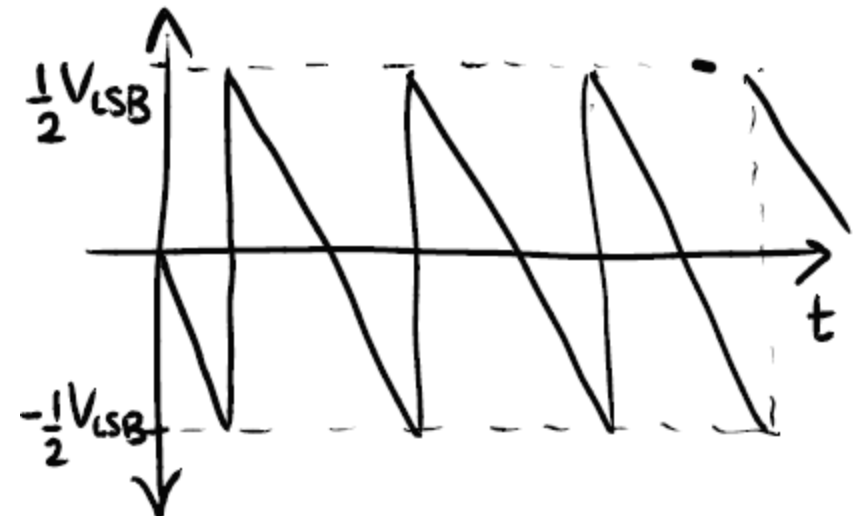

Quantization Noise Statistics

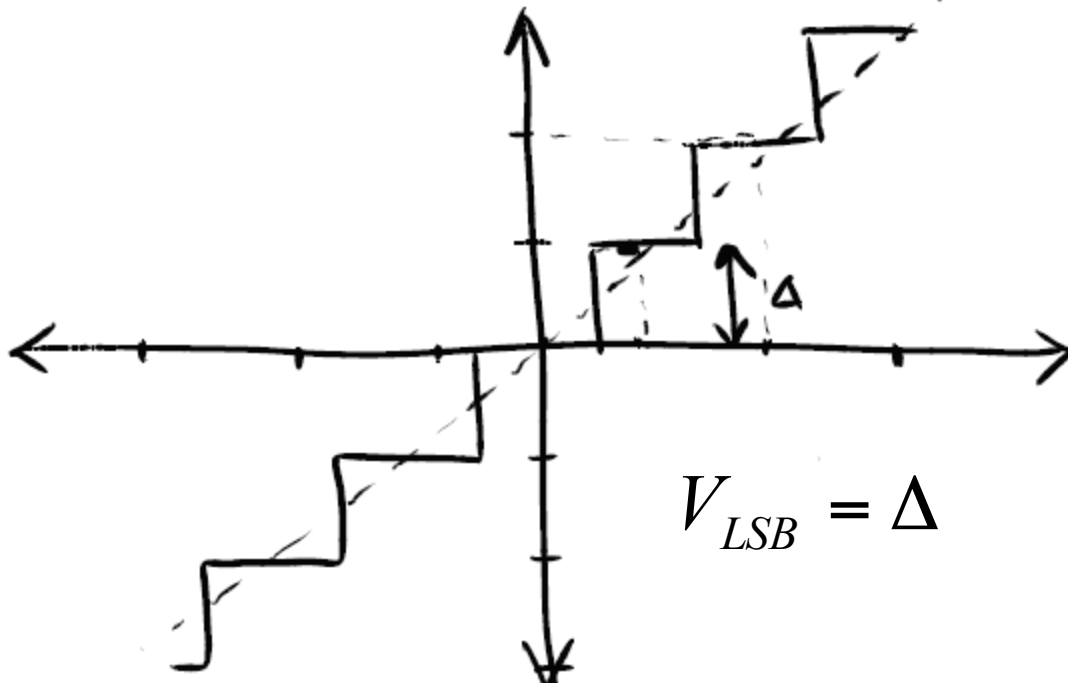


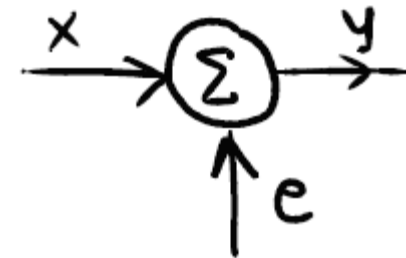
$$e = y - f(b_1, b_2, \dots, b_N) V_{ref}$$



- Random input signal, then quantization noise follows a uniform distribution and a white noise statistics.

$$\bar{e} = 0$$

$$\bar{e}^2 = \frac{\Delta^2}{12}$$

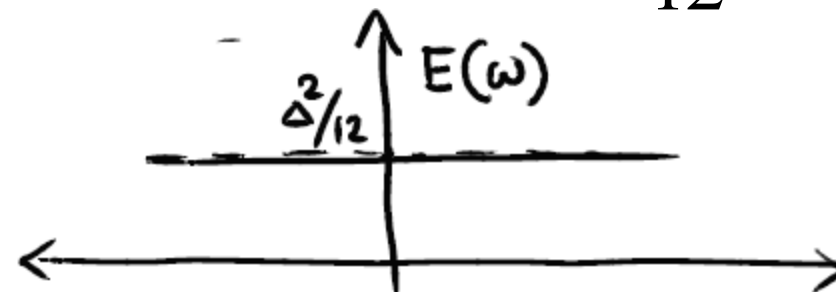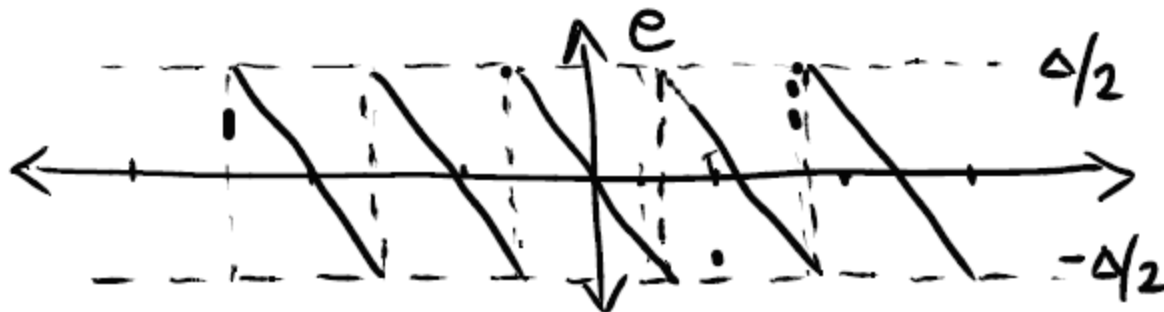

Data Converter Metrics



- Signal to quantization noise ratio $V_{LSB} = 2^{-N} V_{ref}$

$$SNR = 20 \log_{10} \left(\frac{V_{ref}}{\sqrt{12}} / \frac{V_{LSB}}{\sqrt{12}} \right) = 6.02 N$$


- Increasing the resolution by 1 bit increases the SNR by 6dB
- Estimating resolution from measurements
- For random input
- For sinusoidal input

$$ENOB = \frac{SNR_{measured}}{6.02}$$

$$ENOB = \frac{SNR_{measured} - 1.76}{6.02}$$

- Dynamic Range: $DR = \frac{Signal(RMS)}{Noise(RMS) + Distortion(RMS)}$

Data Converter Metrics

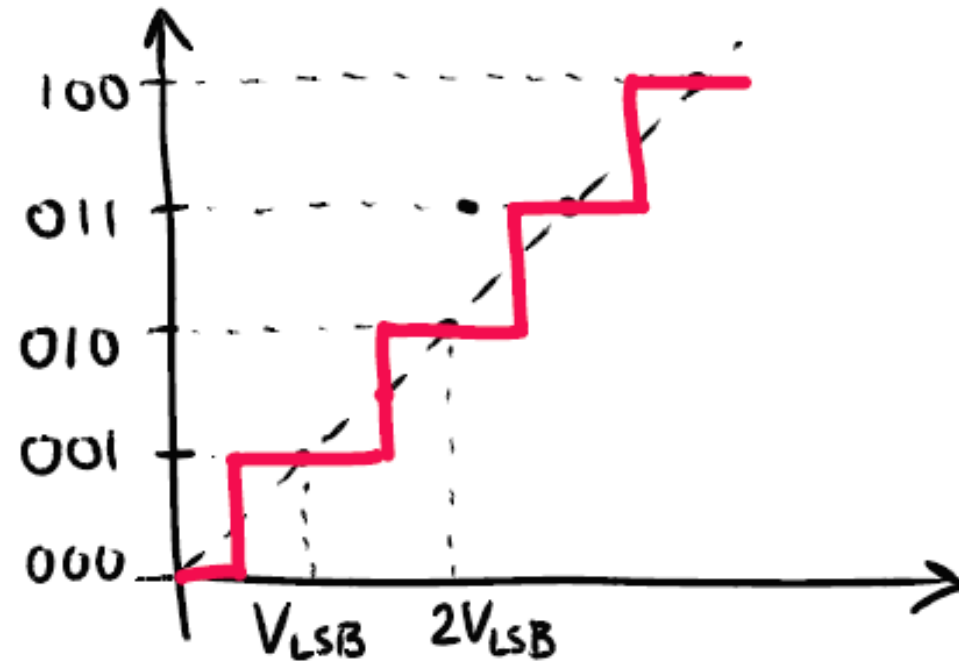

- Offset error

$$e_{off(ADC)} = \frac{V_{00..1}}{V_{LSB}} - \frac{1}{2}$$


$$e_{off(DAC)} = \left. \frac{V_{out}}{V_{LSB}} \right|_{V_{in}=0}$$

- Gain error

$$e_{gain(DAC)} = \left[\left. \frac{V_{out}}{V_{LSB}} \right|_{V_{in}=11..1} - \left. \frac{V_{out}}{V_{LSB}} \right|_{V_{in}=00..0} \right] - (2^N - 1)$$

$$e_{off(ADC)} = \left[\frac{V_{11..1}}{V_{LSB}} - \frac{V_{00..0}}{V_{LSB}} \right] - (2^N - 2)$$

Data Converter Metrics

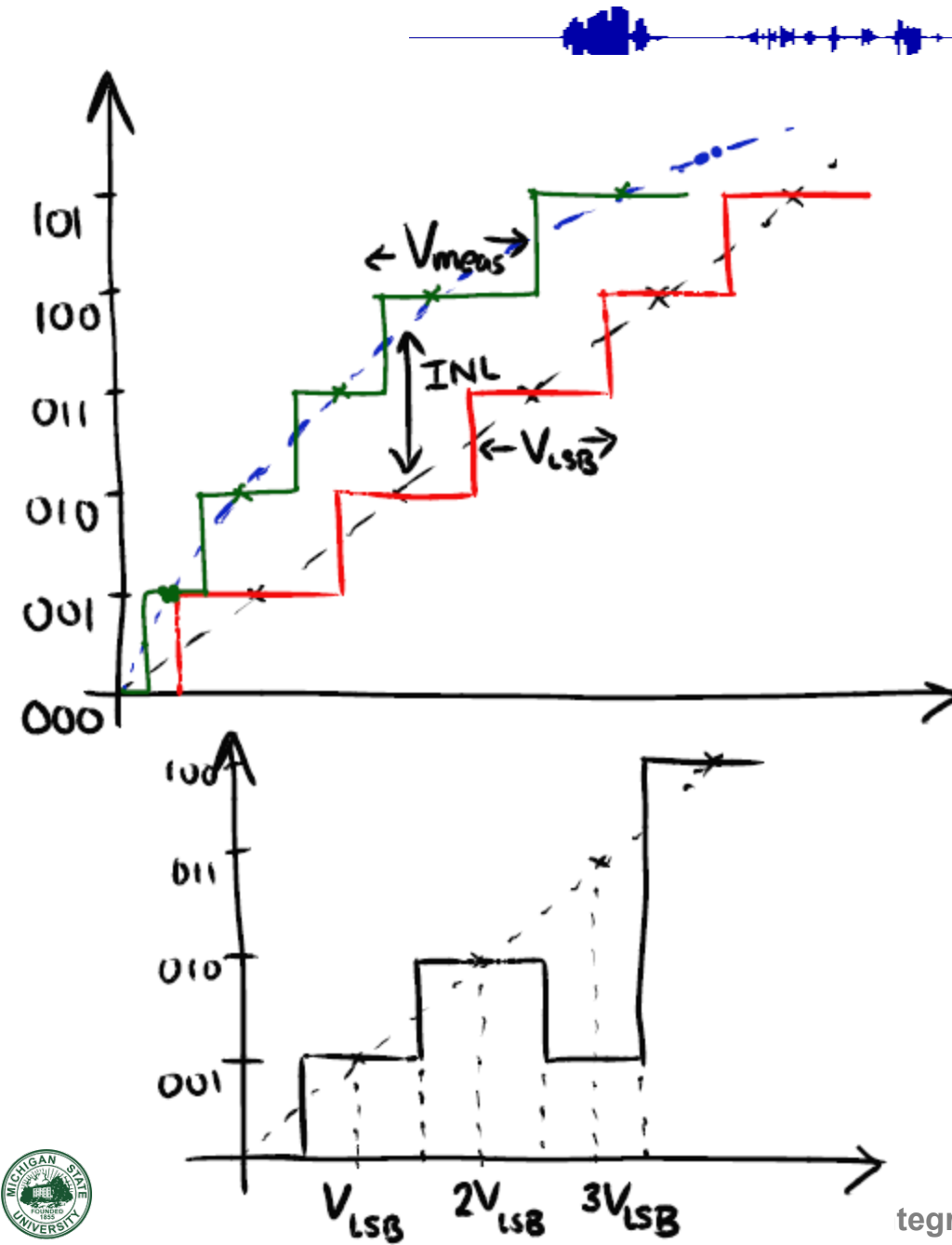

- Integral Non-Linearity (INL)

$$INL = \max_{\{00..0-11..1\}} \frac{|V_{meas} - V_{ideal}|}{V_{LSB}}$$

- Differential Non-linearity

$$DNL = \max_{\{00..0-11..1\}} \frac{|\Delta V_{meas} - V_{LSB}|}{V_{LSB}}$$


- Monotonicity
- Missing output codes
- Speed of ADC – acquisition time + measurement time
- Speed of DAC – time for the output to settle down to $0.5V_{LSB}$

Nyquist-rate DACs



- Tree based decoding

$$B_{out} = 2^{-1} b_1 + 2^{-2} b_2$$

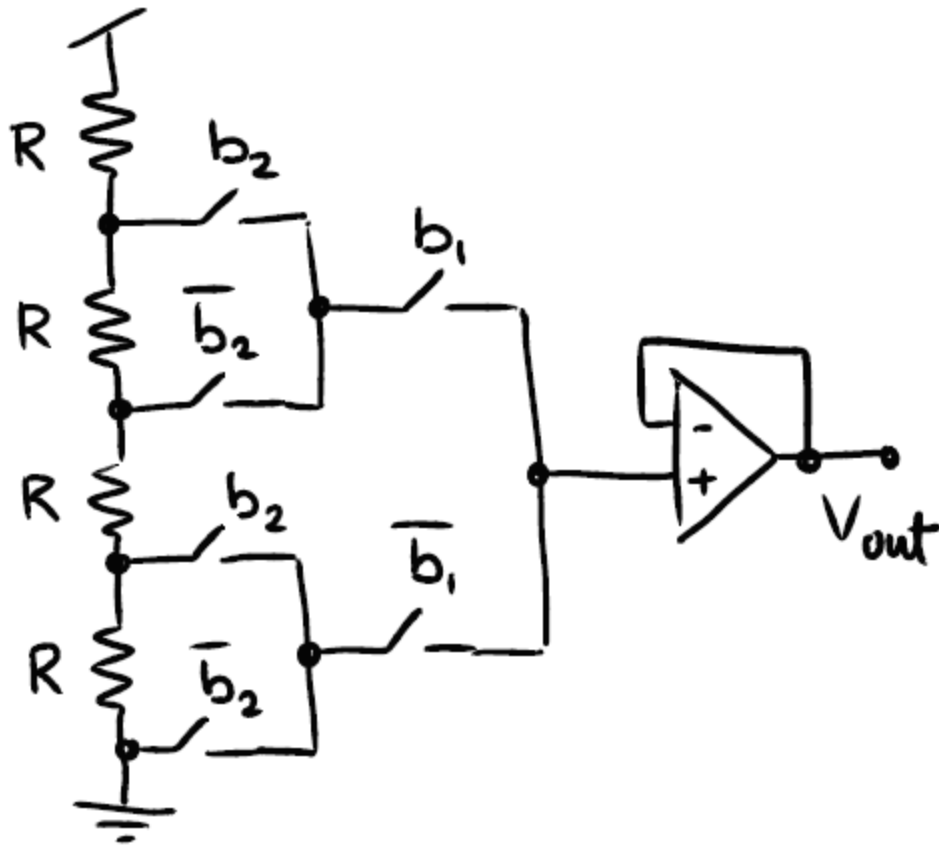


- Advantages
- Guaranteed monotonicity
- Resistive matching (up to 10 bits)
- Disadvantages:
- Speed ?
- Size ?

Nyquist-rate DACs



- Folded resistor network

$$B_{out} = 2^{-1}b_1 + 2^{-2}b_2$$

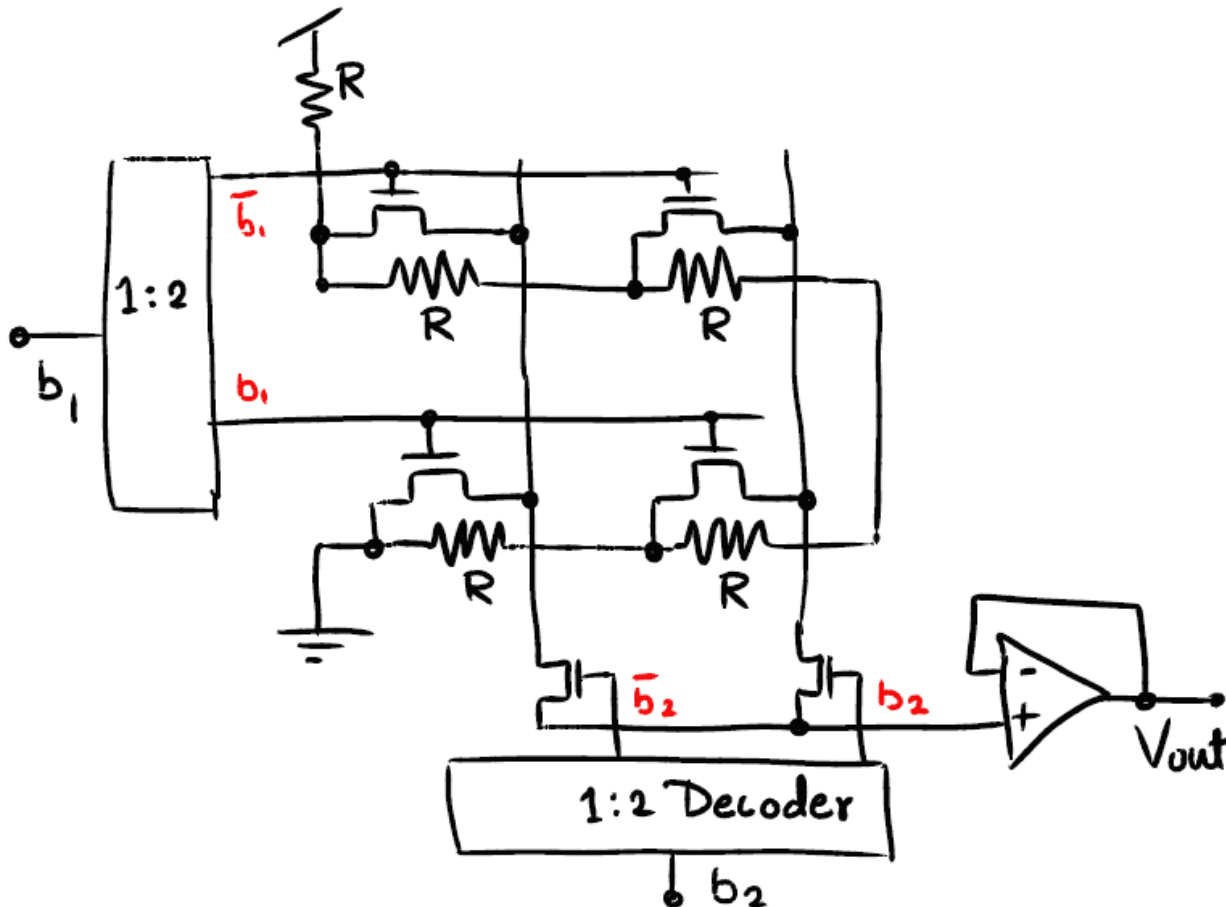


- Advantages
- Lower capacitance at the input of the opamp.
- Disadvantages:
- Size ?

Nyquist-rate DACs



- Ladder architecture
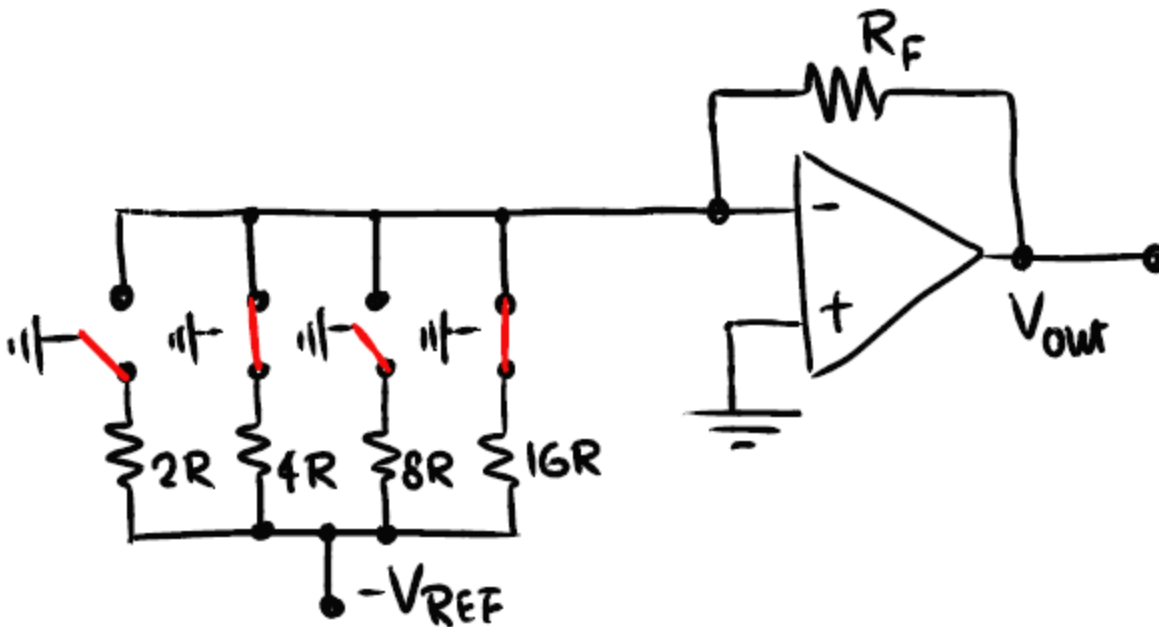
$$V_{out} = \frac{R_F}{R} V_{ref} (2^{-1} b_1 + 2^{-2} b_2 + \dots + 2^{-N} b_N)$$




- Advantages
- Simplicity.
- Disadvantages:
- Size ?

Nyquist-rate DACs



- Ladder architecture
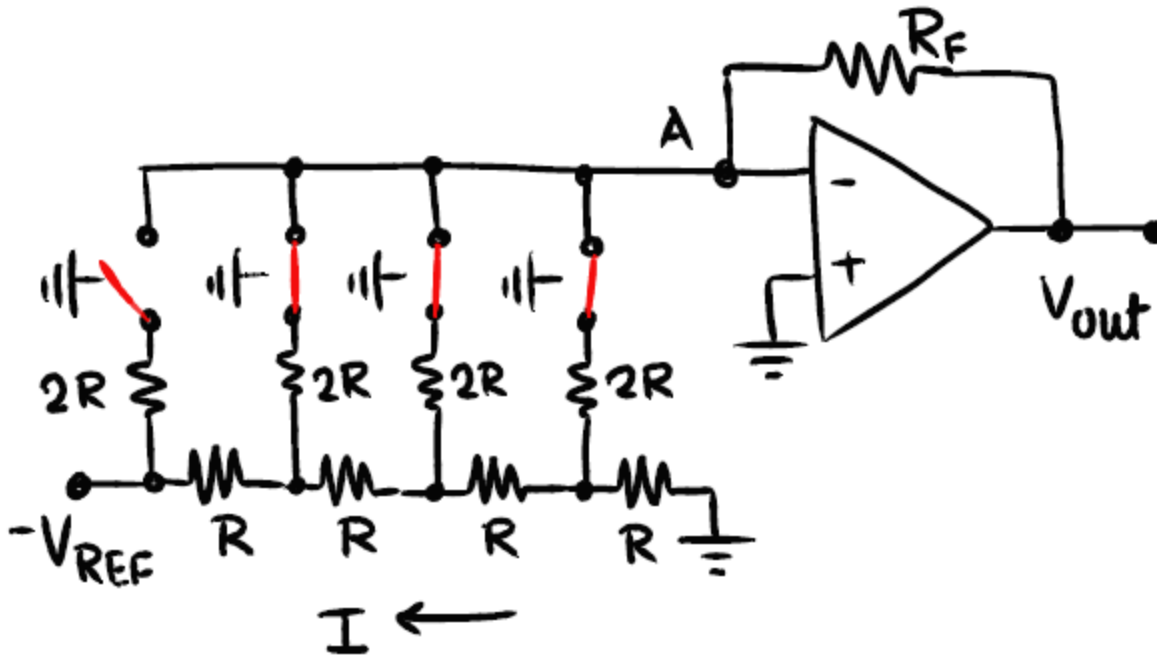
$$V_{out} = \frac{R_F}{R} V_{ref} (2^{-1} b_1 + 2^{-2} b_2 + \dots + 2^{-N} b_N)$$




- Advantages
- Simplicity.
- Size
- Disadvantages:
- Speed ?

Nyquist-rate DACs



- Switched capacitor converters
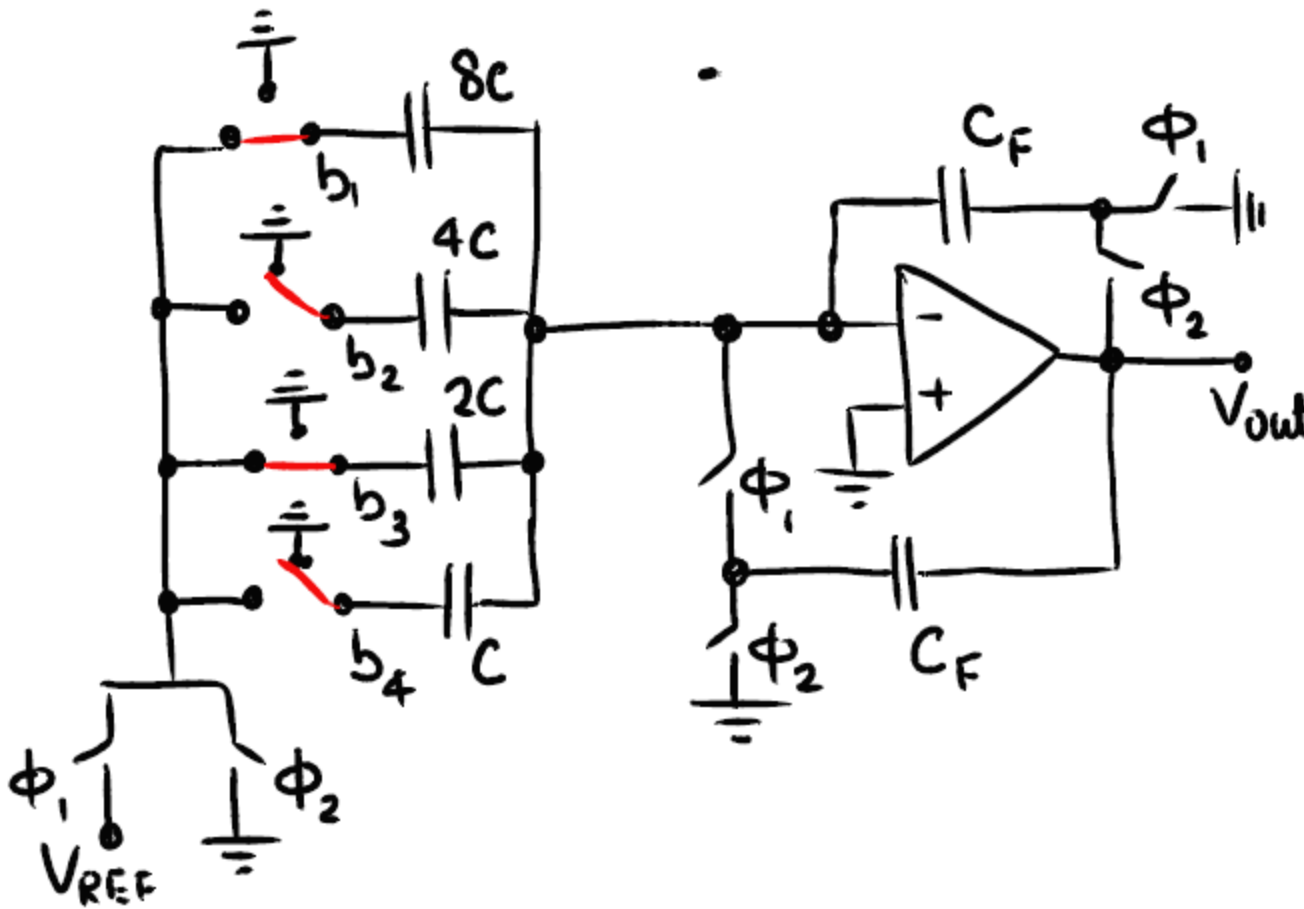
$$V_{out} = \frac{C}{C_F} V_{ref} (2^{-1} b_1 + 2^{-2} b_2 + \dots + 2^{-N} b_N)$$




- Advantages
- Simplicity.
- Matching
- Disadvantages:
- Sampling ?

Nyquist-rate DACs




- Current mode thermometer code
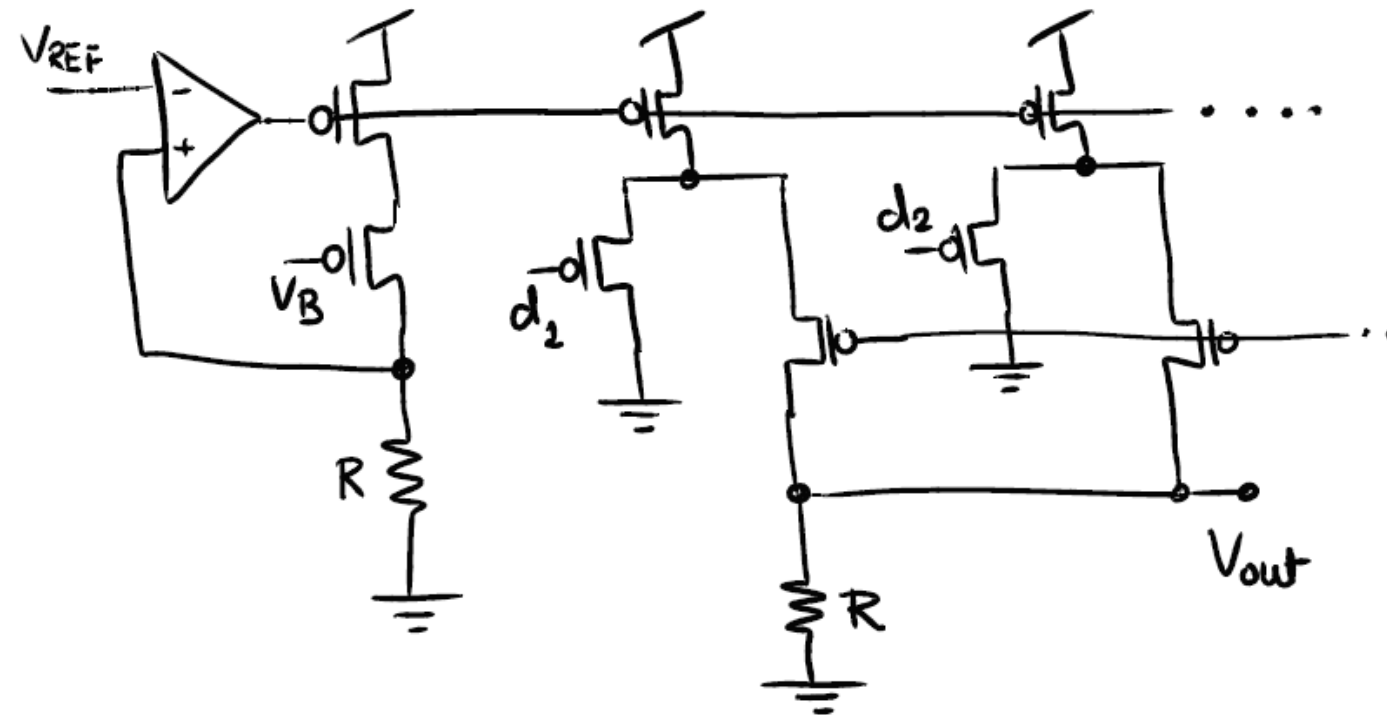
$$V_{out} = V_{ref} (d_1 + d_2 + \dots + d_N)$$




- Advantages
- Avoids glitching.
- Simplicity
- Matching
- Disadvantages:
- Size ?

Nyquist-rate DACs

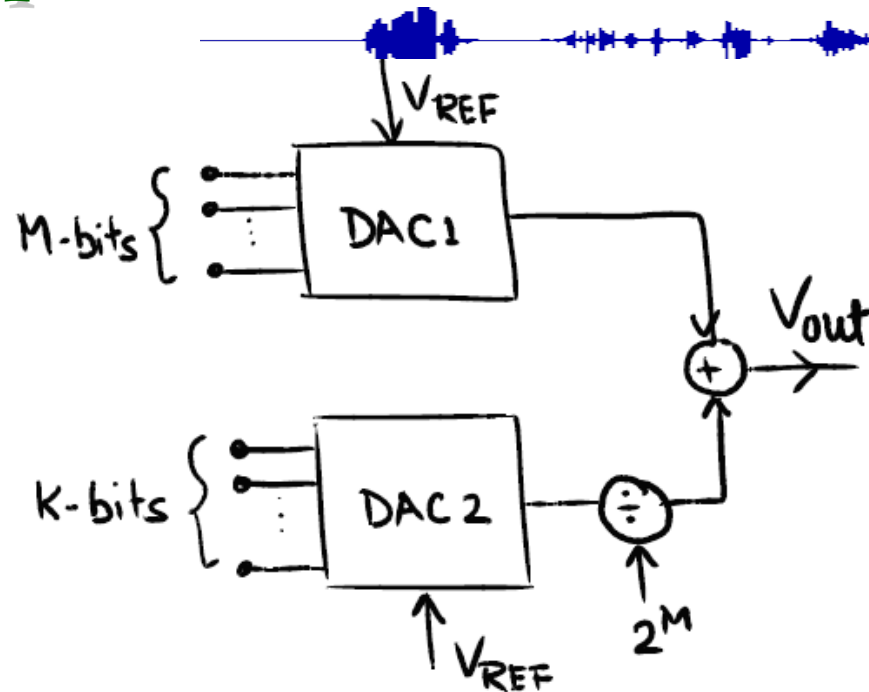

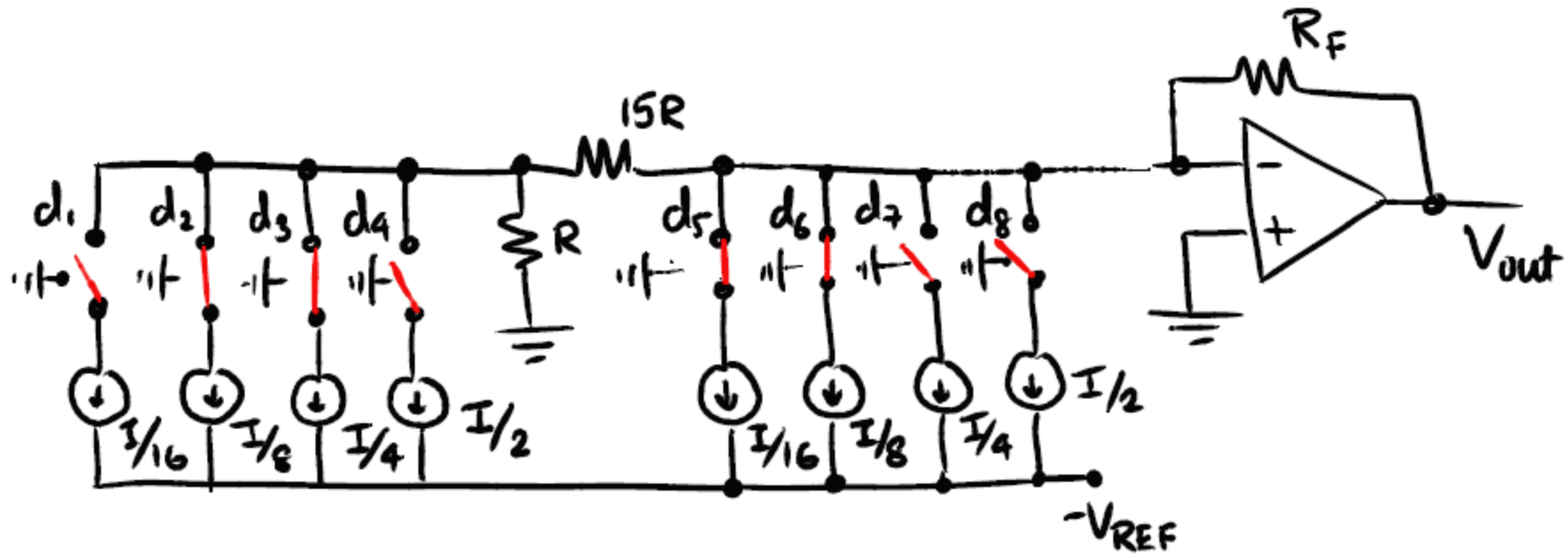
- Parallel DAC
- Advantages
- Size
- Disadvantages:
- Size ?



Nyquist-rate Serial DACs




- Charge distribution DACs

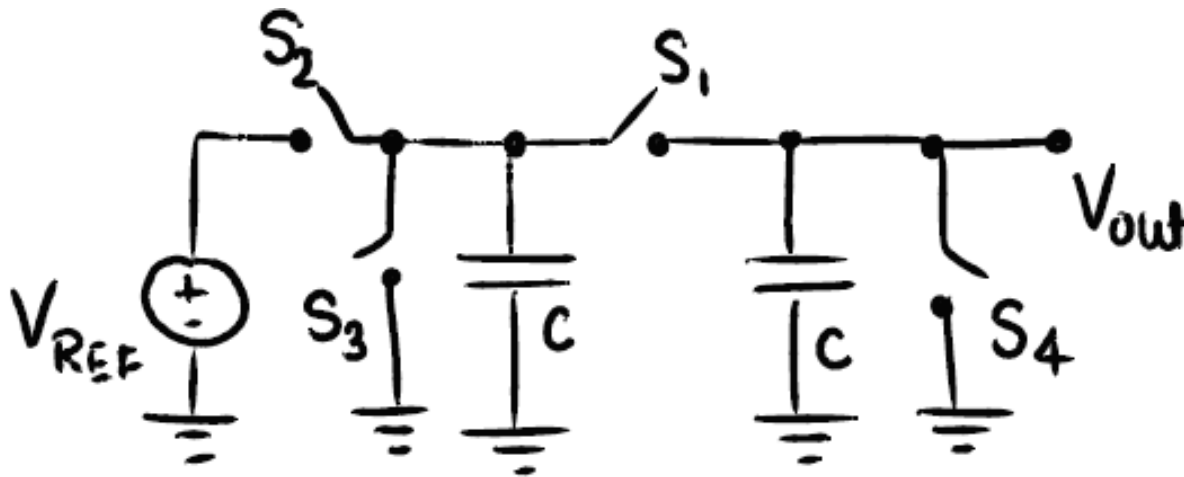


- S_4 turns ON only once before the conversion begins.
- S_2 turns ON if bit is 1 otherwise S_3 turns ON
- S_1 turns ON
- Repeat

Nyquist-rate Algorithmic DACs


- Bit serial configuration

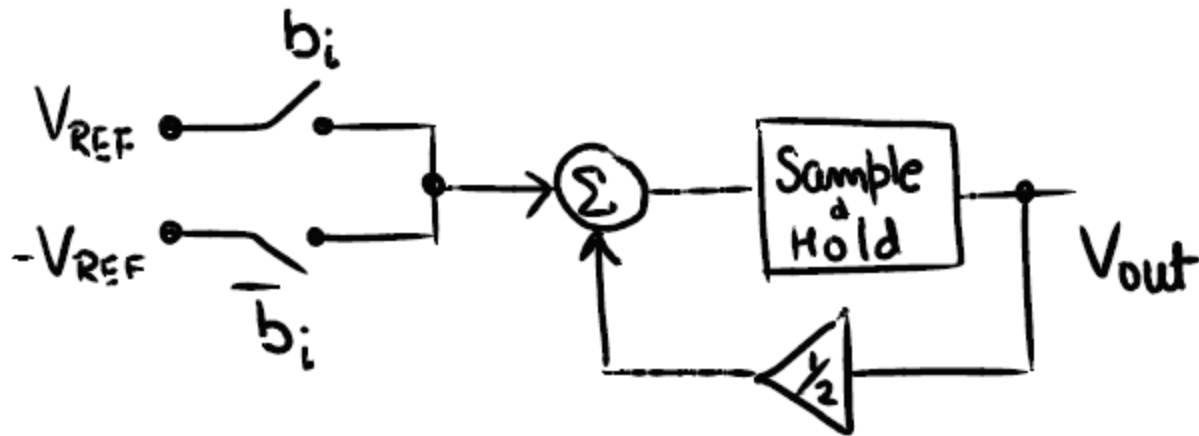


- Pipelined configuration

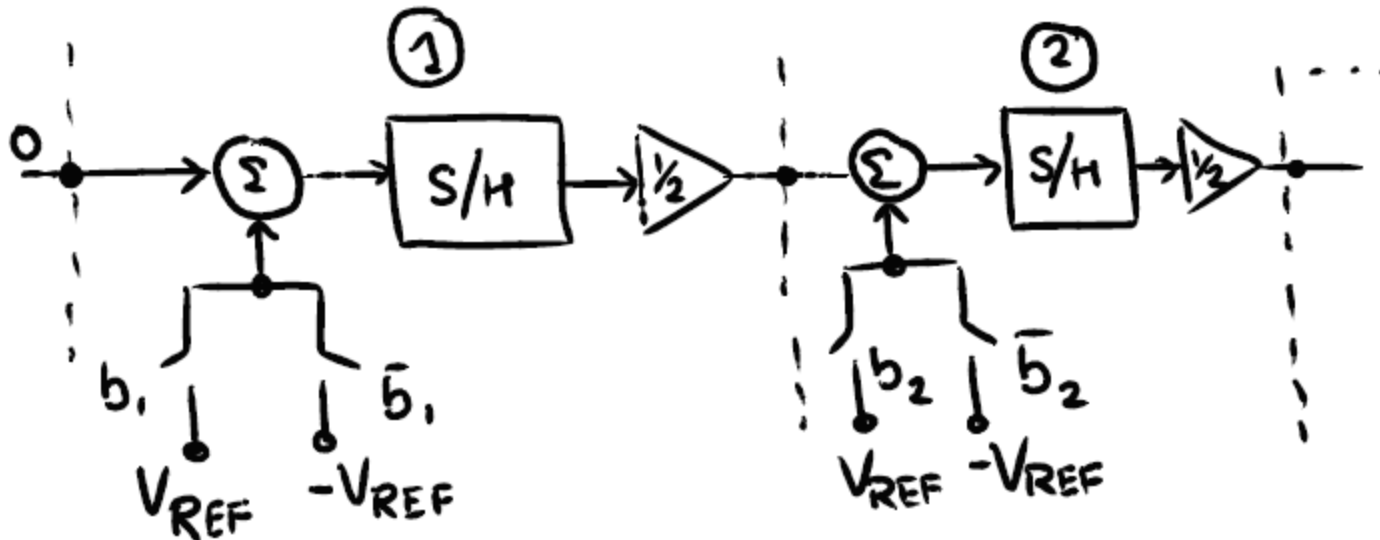

Nyquist-rate Integrating ADC

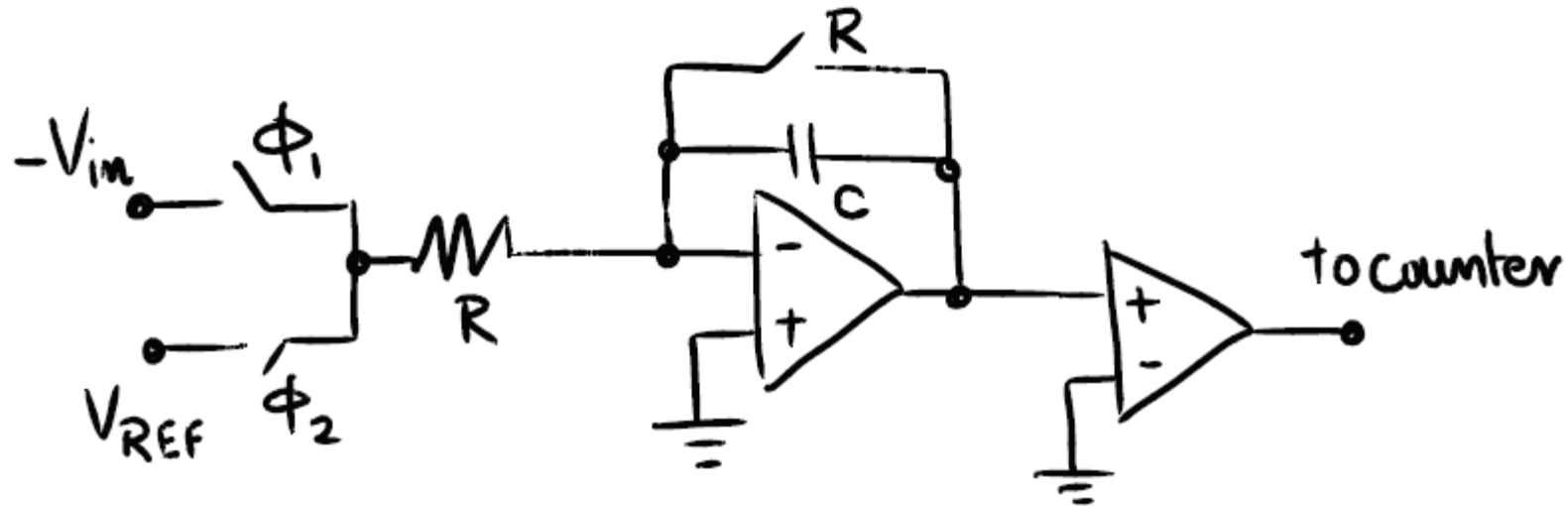

- Dual-slope ADC

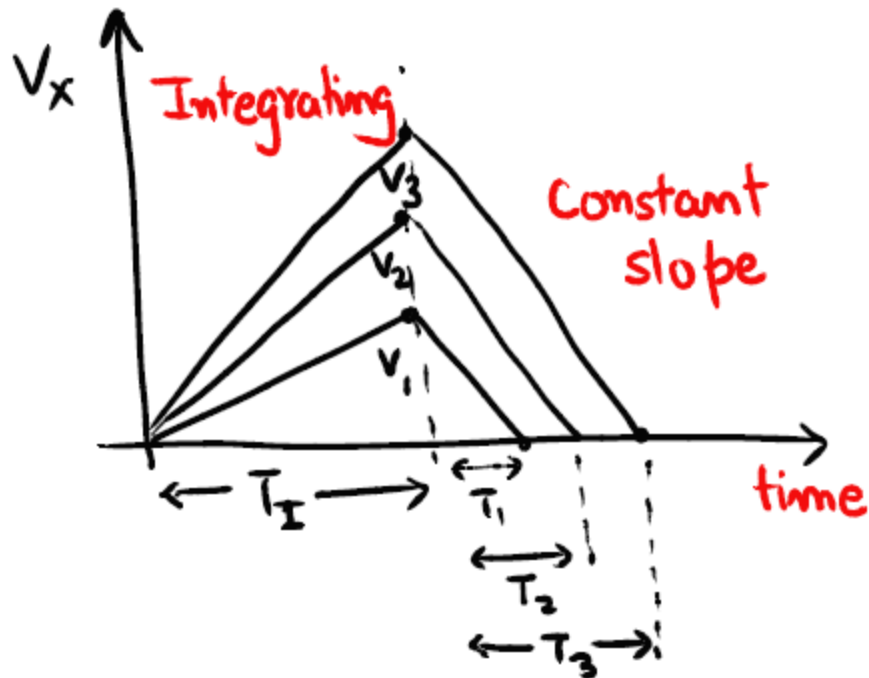

$$T_1 = T_I \frac{V_{in}}{V_{ref}}$$


Nyquist-rate ADC



- Algorithmic ADC



$$V_0 = V_{in}; b_i = \text{Cmp}(V_{i-1})$$

$$V_i = 2V_{i-1} - b_i V_{ref}$$

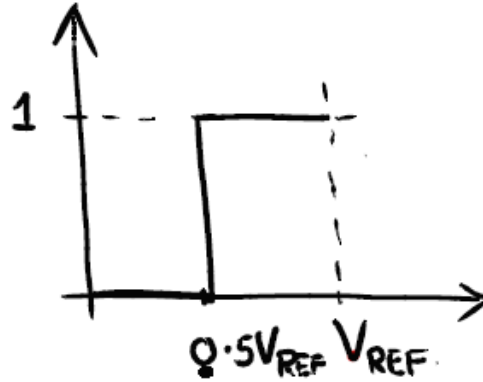

- Flash ADC


- Pipelined ADC

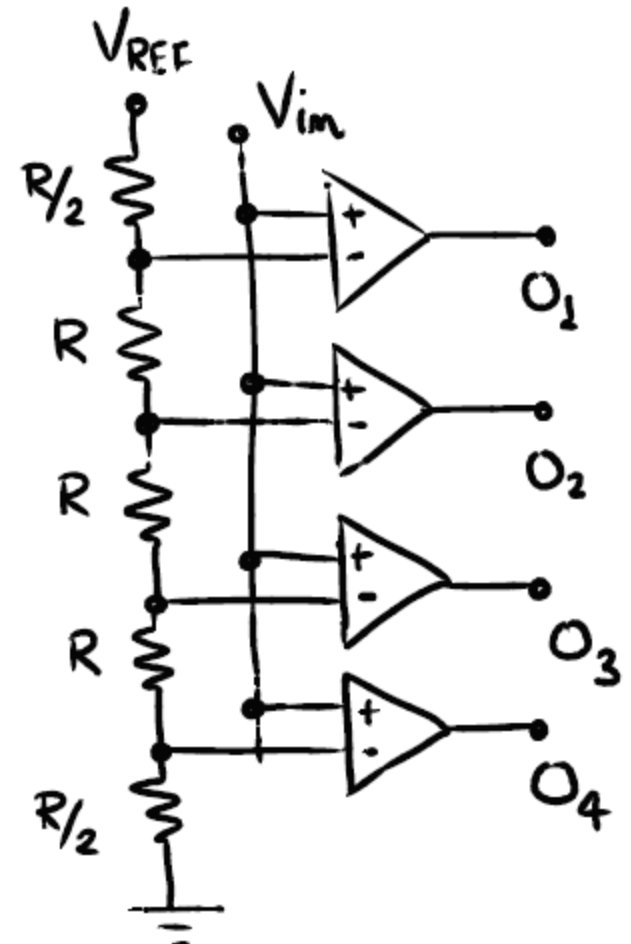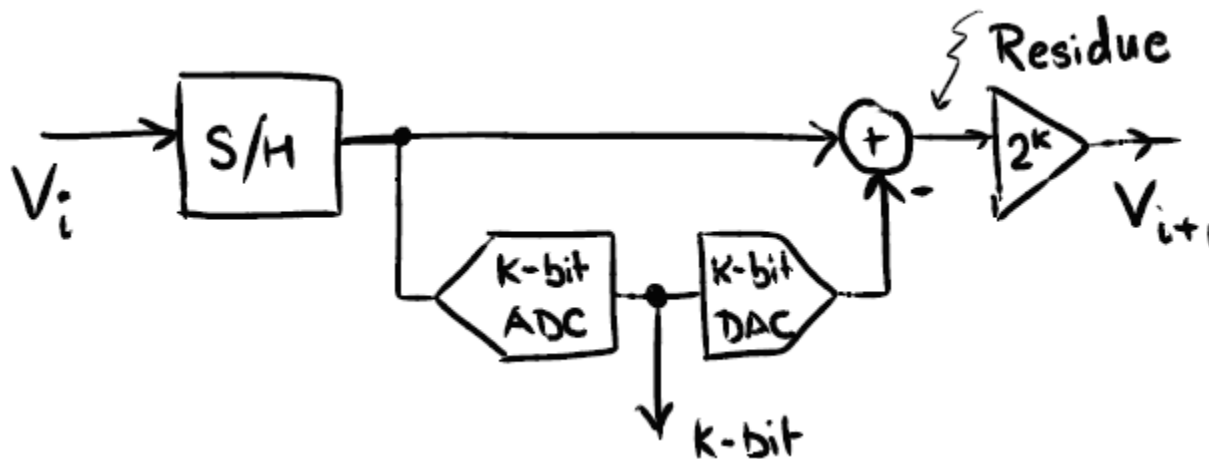

Oversampling ADC



- First order Sigma-Delta Modulator

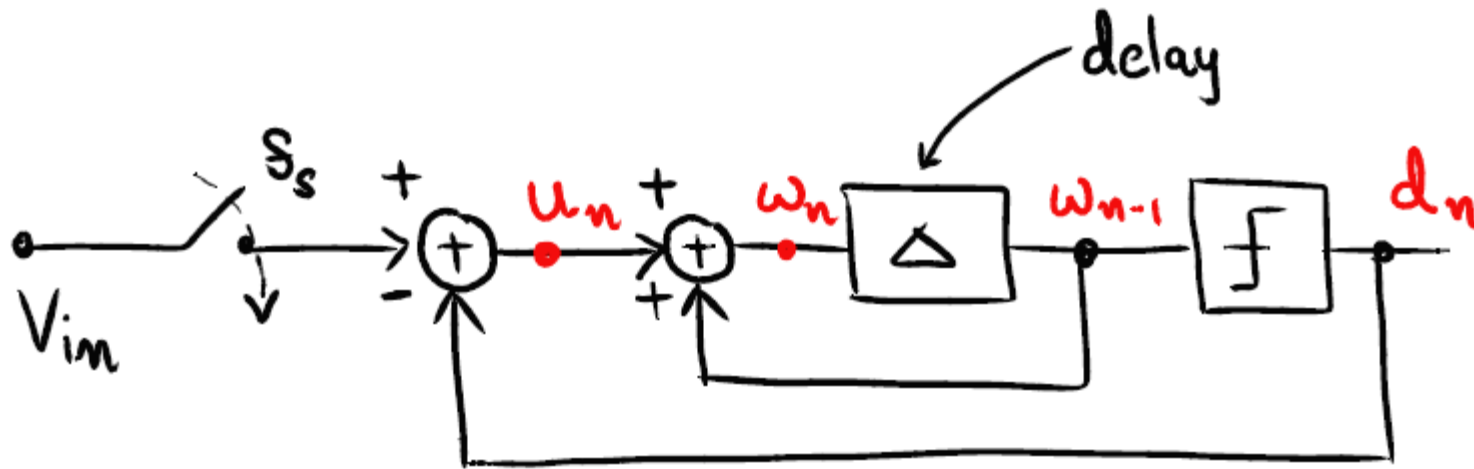


- Worksheet -

$$\omega_n = \omega_{n-1} + (V_{in} - D_n V_{ref})$$

Oversampling ADC – Time domain analysis

- First order Sigma-Delta Modulator

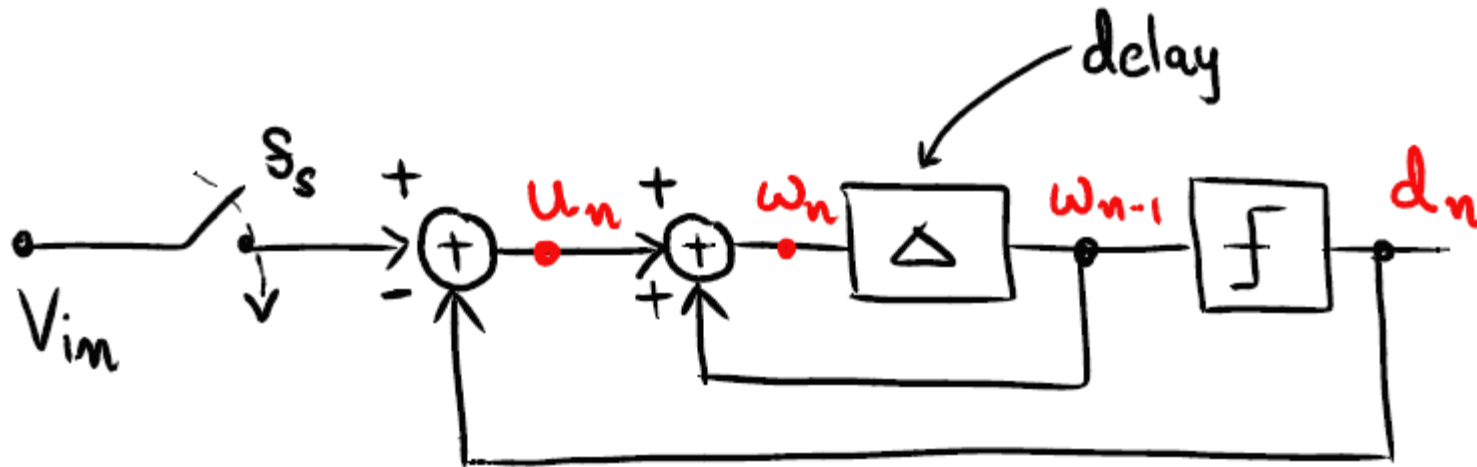


$$\omega_n = \omega_{n-1} + (V_{in} - D_n V_{ref})$$

$$\omega_N = \omega_0 + \left(N V_{in} - \sum_n D_n V_{ref} \right)$$

$$\boxed{\frac{1}{N} \sum_n D_n V_{ref} \rightarrow V_{in}}$$

$$\frac{1}{N} \omega_N = V_{in} - \frac{1}{N} \sum_n D_n V_{ref}$$

Oversampling ADC – Frequency analysis

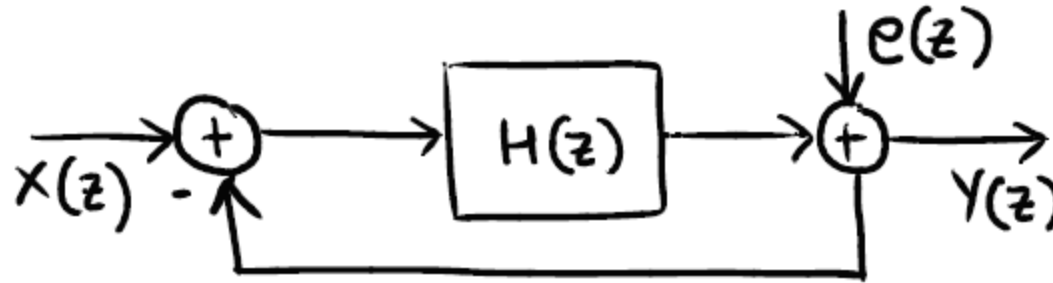

$$Y(z) = e(z) + H(z)[X(z) - Y(z)]$$

$$Y(z) = \left[\frac{H(z)}{1 + H(z)} \right] X(z) + \left[\frac{1}{1 + H(z)} \right] e(z)$$

Signal Transfer Function (STF)


Noise Transfer Function (NTF)

$$H(z) = \frac{1}{z - 1}$$

$$Y(z) = z^{-1}X(z) + (1 - z^{-1})e(z)$$

$$NTF = e[n] - e[n - 1]$$

Oversampling ADC – Frequency analysis

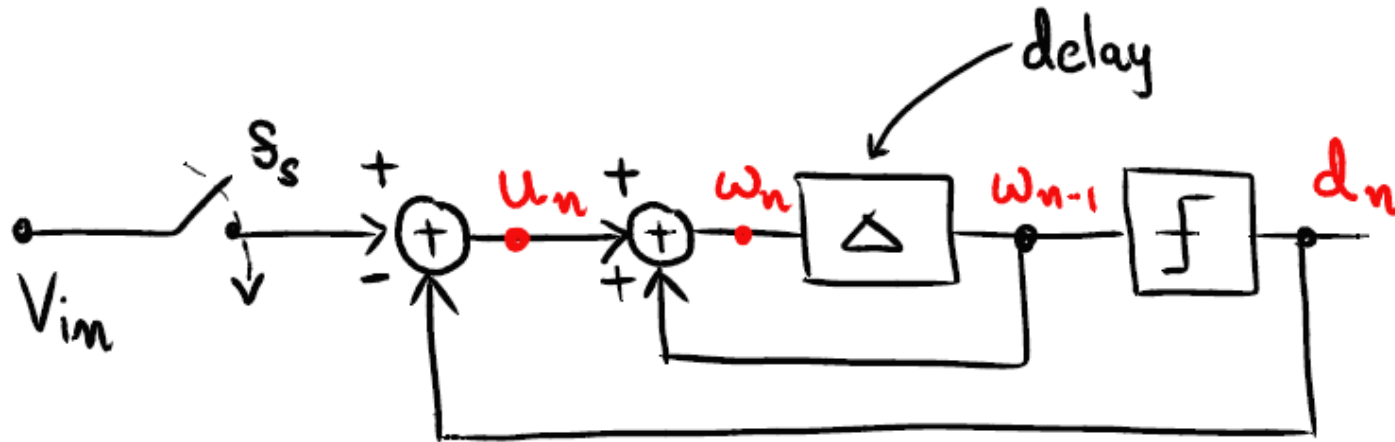


$$Y(z) = z^{-1}X(z) + (1 - z^{-1})e(z)$$

$$NTF(f) = 1 - e^{-j2\pi f / f_s}$$


$$NTF(f) = \sin\left(\frac{\pi f}{f_s}\right) 2je^{j\pi f / f_s}$$

$$|NTF(f)| = 2\sin\left(\frac{\pi f}{f_s}\right)$$
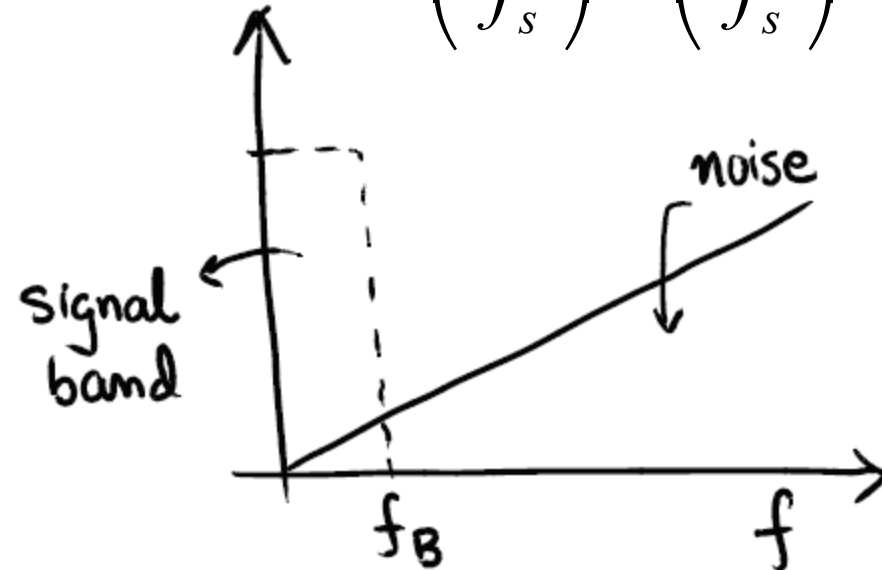
$$\sin\left(\frac{\pi f}{f_s}\right) \approx \left(\frac{\pi f}{f_s}\right)$$




Oversampling ADC – Frequency analysis

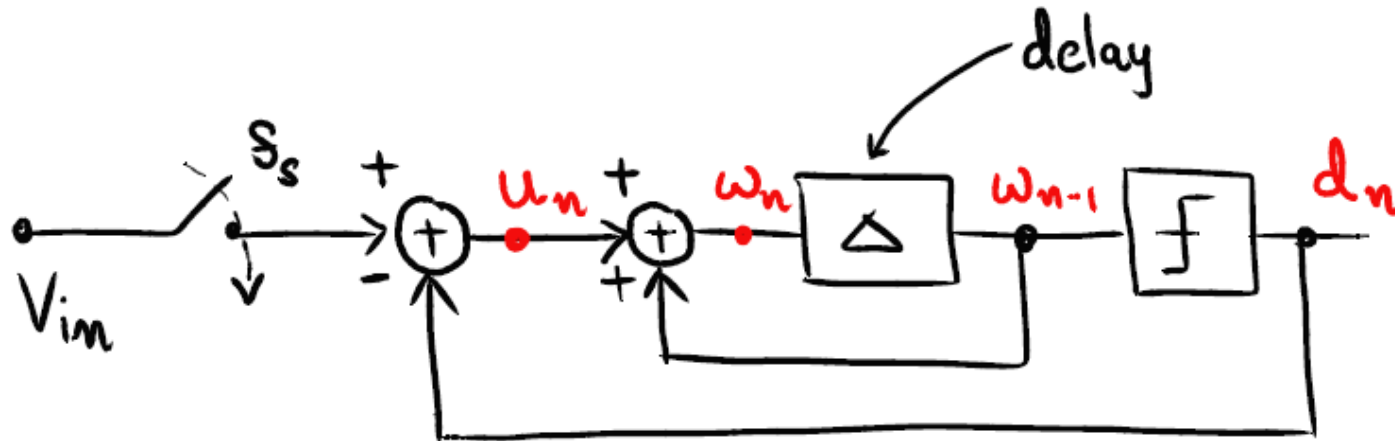


$$P_e = \int_{-f_0}^{f_0} S_e(f) |NTF(f)|^2 df$$

$$P_e = \int_{-f_0}^{f_0} \frac{\Delta^2}{12 f_s} \left[2 \sin\left(\frac{\pi f}{f_s}\right) \right]^2 df$$
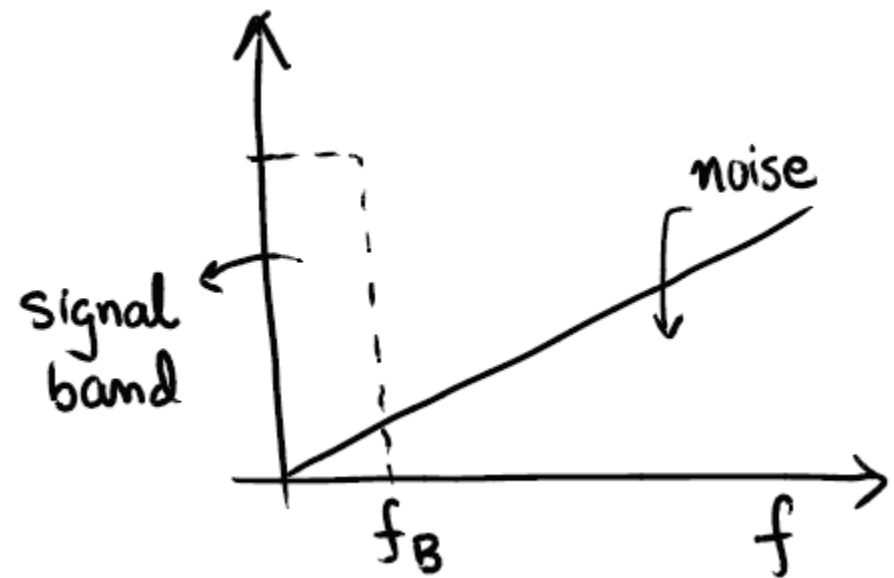
$$P_e = \frac{\Delta^2 \pi^2}{36} \left[\frac{2f_0}{f_s} \right]^3 = \frac{\Delta^2 \pi^2}{36} \left[\frac{1}{OSR} \right]^3$$



Higher order Sigma-Delta Modulator

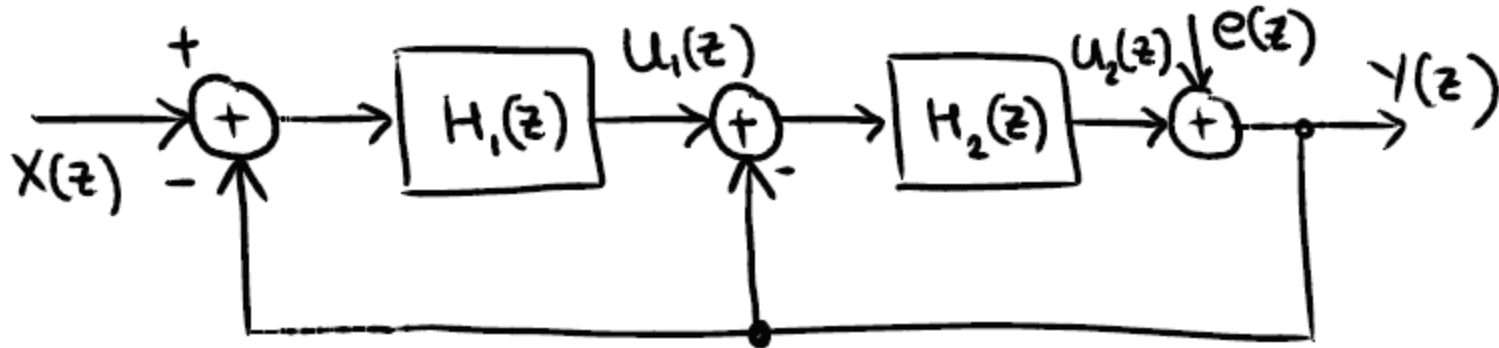


$$P_e = \int_{-f_0}^{f_0} S_e(f) |NTF(f)|^2 df$$

$$H_1(z) = \frac{1}{z-1} \quad H_2(z) = \frac{z}{z-1}$$


$$P_e = \frac{\Delta^2 \pi^4}{60} \left[\frac{1}{OSR} \right]^5$$

$$SNR = 10 \log P_{sig} + 110 \log OSR + const.$$



L^{th} order Sigma-Delta Modulator

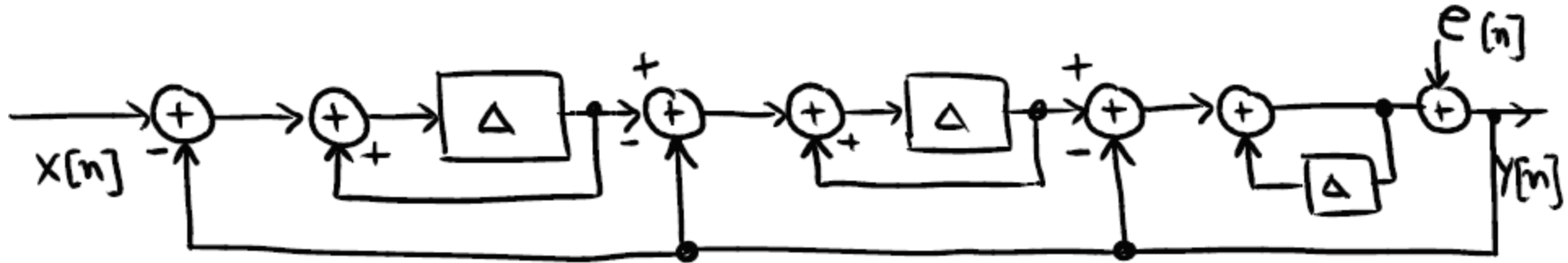
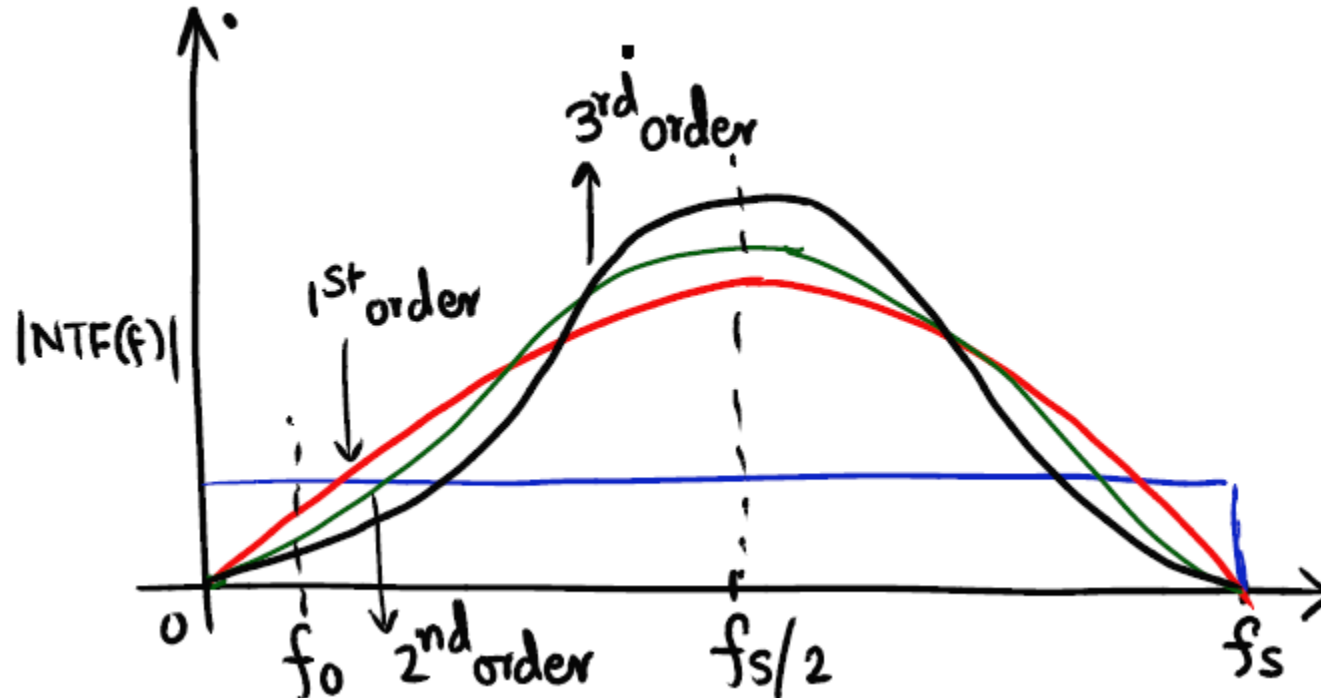
$$SNR = 10 \log P_{sig} + (2L + 1)10 \log OSR + const.$$



Oversampling ADC – Implementation

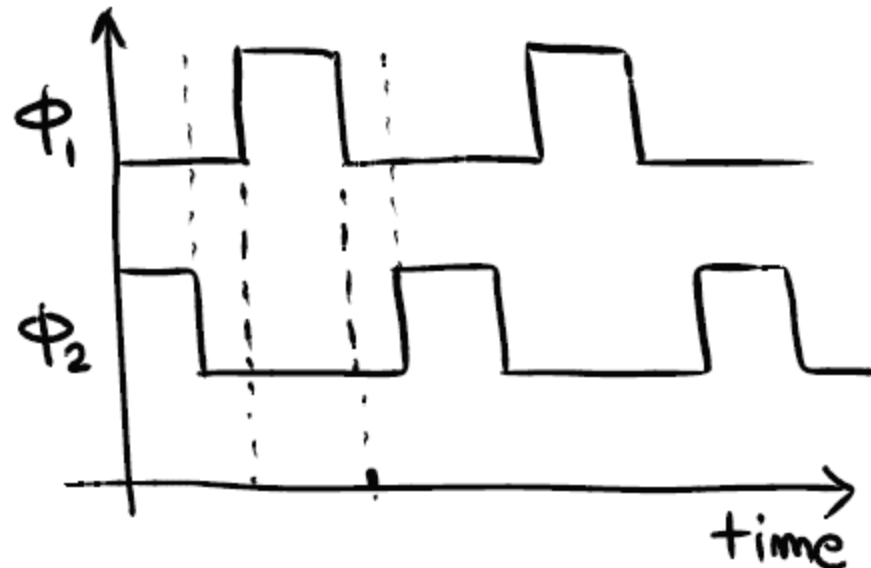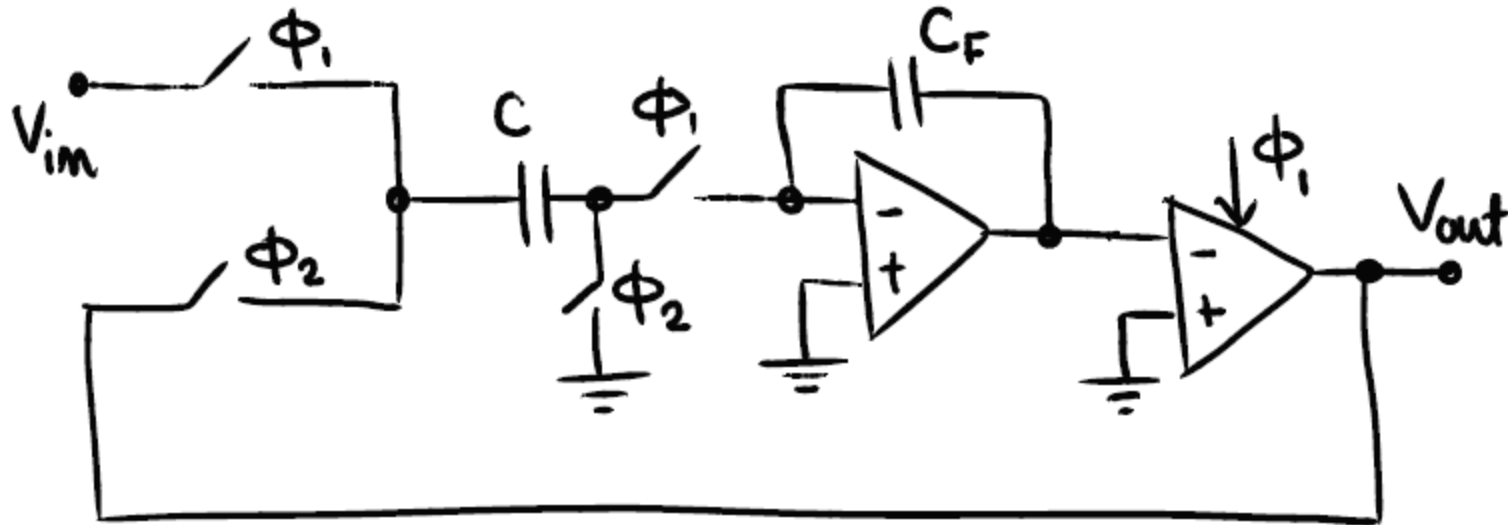

ADC Comparison

