



Digital and Analog Computing Circuits



CSE562M: Analog Integrated Circuits

Shantanu Chakrabartty






Digital computing circuits



- Complementary logic
- Pass transistor logic
- Dynamic logic
- Sequential logic
- Asynchronous logic
- Adiabatic logic

Complementary logic

  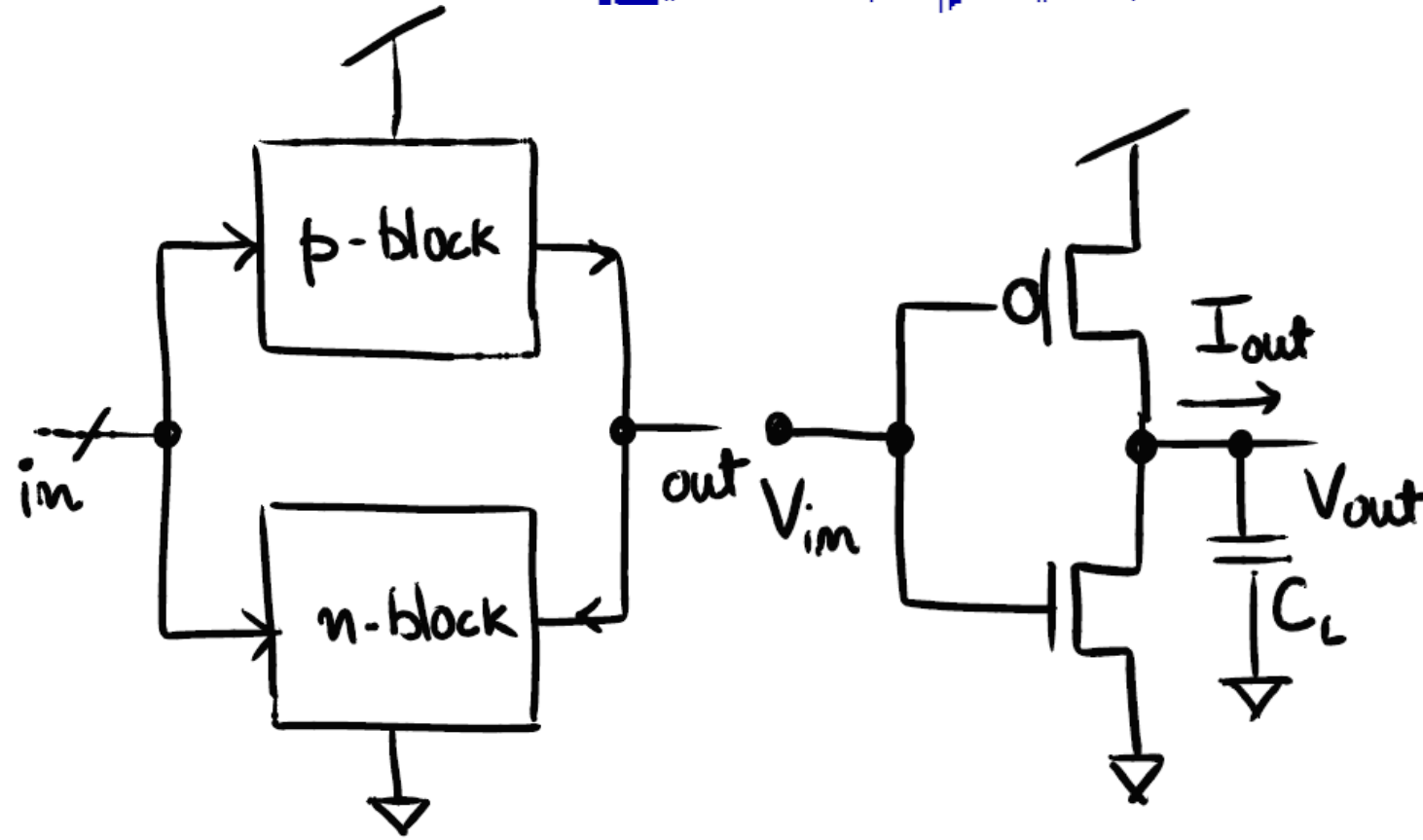

- Simplest complementary logic implementation



Power-speed trade-off



- Power Dissipation
 - Static Dissipation – Sub-threshold leakage
 - Dynamic Dissipation – $f \times C_L \times V_{dd}^2$
- Speed – rise/fall time
$$\tau \approx \frac{C_L}{C_{ox} \mu \frac{W}{L} V_{dd}}$$
- Reduce V_{dd} by a factor of 2, Power = ?; Speed = ?
- Reduce C_L by a factor of 2, Power = ?; Speed = ?
- Reduce f by a factor of 2, Power = ?; Speed = ?




Pass transistor logic: Switch

  


- R-C effect
- Long chains of pass transistors requires buffering.

Example: NOR logic

 

- Complementary logic


- Hi-Z input
- Low-Z output

 


- Pass transistor logic

- Low-Z input
- Low-Z output


Cascading effect

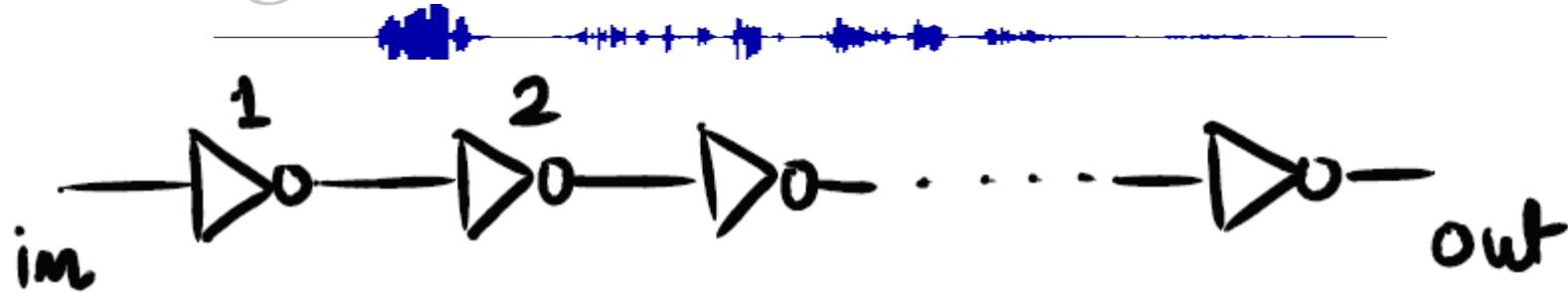

 - Complementary logic: $Delay = N \times \tau_{stage}$



 
- Pass transistor logic: $Delay = N^2 \times \bar{\tau}_{stage}$
- But: $\tau_{stage} > \bar{\tau}_{stage}$
- Introduce buffers every four stages of pass transistor logic.



Hybrid logic




 - What logic does this circuit implement ?




- Is this a better logic than complementary and pass transistor logic ?

Dynamic Complementary logic

 

 
- Inputs and outputs are enabled only during the evaluate phase of the clock.




CMOS Domino logic



 - Can be used to implement cascaded logic functions.




 
- Use positive feedback to speed up evaluate phase.




Sequential logic



 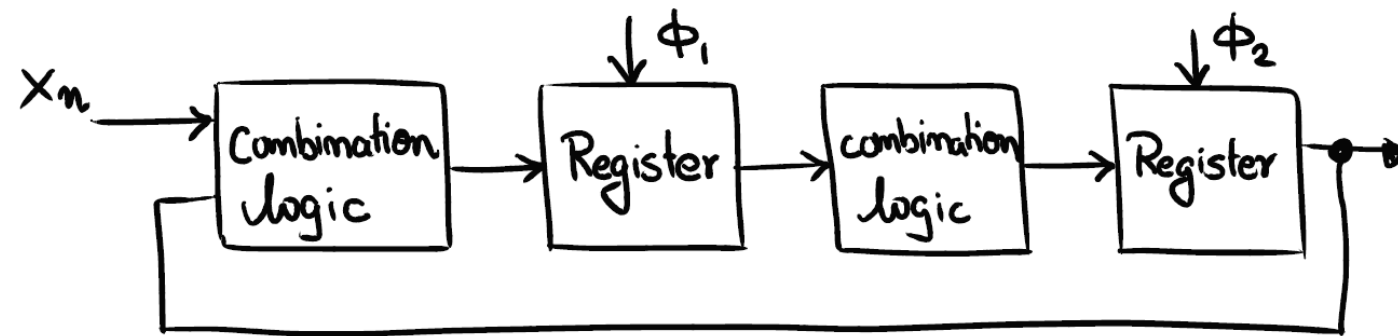
- Finite state machines, shift registers, ...



- Static

 


- Dynamic

 


Pipelining



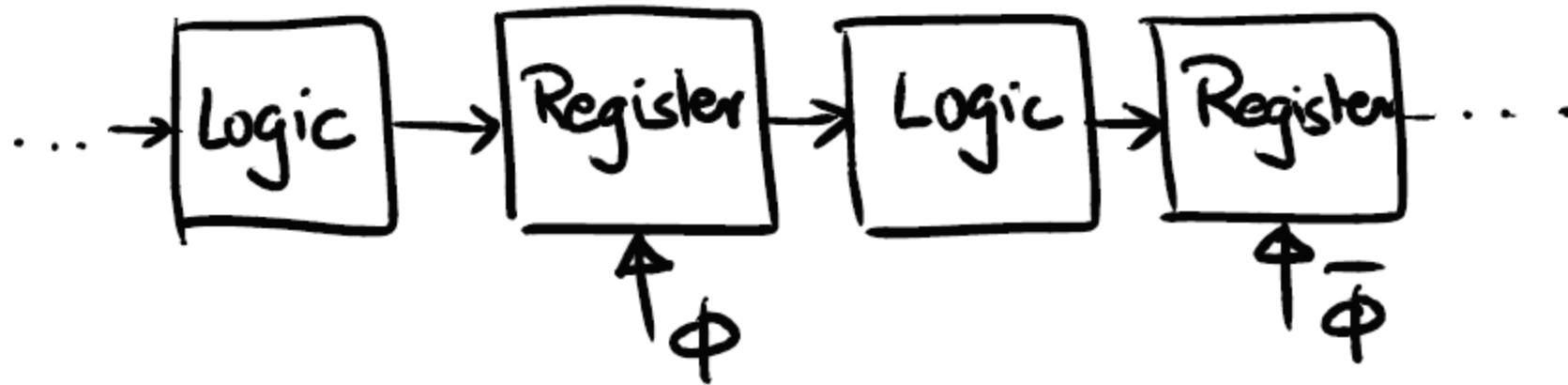- Increasing throughput by sequential logic decomposition



- Simplest example: Shift register

 

Analog computing circuits



- Precision not important
- Pattern recognition systems
- Ultra-low-power
- Ultra-high-speed – where analog-to-digital converters are too power hungry.
- Fewer transistors or high computational density
- Parallel implementations
- **Example:** Most biological computations are “analog” in nature.

Principles of analog computing




- Represent numbers as physical quantities – current, voltage, impedance, charge, time, ratios,...
- Use the physics of the device for implementing mathematical functions.
- Use conservation laws to achieve scalability and portability.

Analog adders




- Conservation of current or charge.

- Ideal

 

$$I_{out} = \sum_{k=1}^N I_k$$


- Non-Ideal

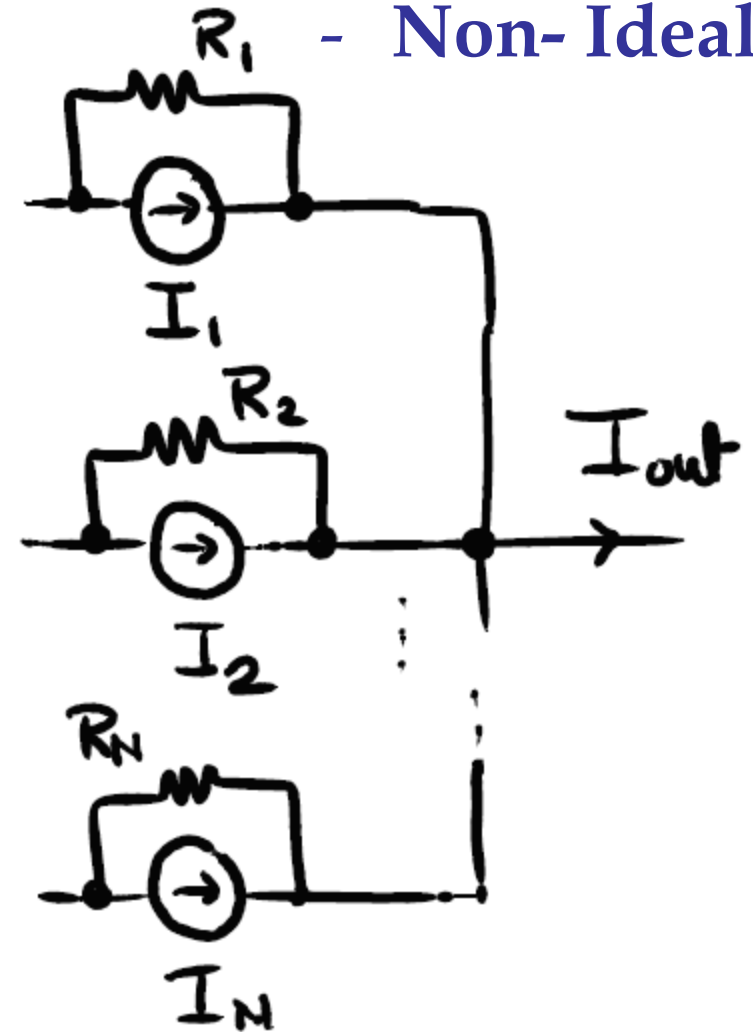

Single transistor as a computer



 - **Sub-threshold:** $I_d \propto \exp\left(\frac{kV_G}{U_T}\right) \exp\left(\frac{-V_S}{U_T}\right) \approx \exp\left(\frac{V_{GS}}{U_T}\right)$
- Exponential function “practically” for free.



- What function does this circuit implement where I_{in} is the input?
- What happens if the transistor is biased in above threshold?
- Can we ignore the effect of the drain terminal?
- What is the disadvantage of such implementation?


Representations



- **Voltages:** Easy to distribute but requires dissipates more energy. Lower dynamic range
- **Current:** Easy to sum but difficult to distribute. Higher dynamic range. Sub-threshold current: 100fA – 100nA.
- **Charge:** Best only for linear functions – even charge-mode multiplication is complicated.
- **Time:** Easy to transmit and is more robust – but difficult to compute with (Biological computation is time-based)

Scalable Analog Computing

 
- Only relies on conservation laws: KCL, KVL or charge conservation.



Scalable Analog Computing



$$I_{out} = \max(I_1, I_2)$$

 


- How to implement $I_{out} = |I_1 - I_2|$

Scalable Analog Computing



 
- What function does this circuit implement ?



How to build an analog search engine ?






Compressive functions: Sigmoid or Tanh

 

- Transistors biased in sub-threshold.

$$I_1 = I_0 \frac{1}{1 + \exp\left(-\kappa \frac{V_1 - V_2}{U_T}\right)}$$


Gilbert multiplier

  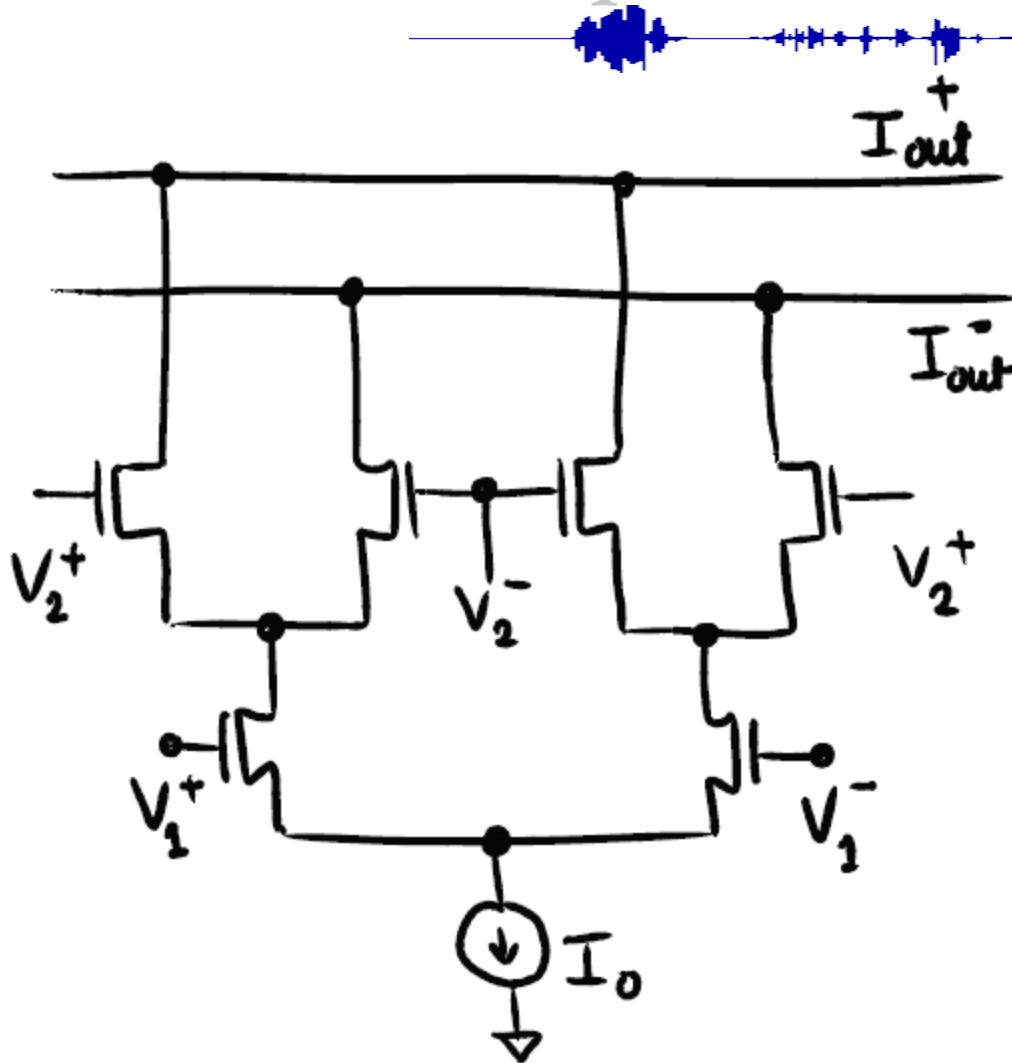


$$I_{out}^+ - I_{out}^- \propto (V_1^+ - V_1^-)(V_2^+ - V_2^-)$$

Winner-take-all

 - Only one of the output is high and corresponds to the maximum of the input – digital encoding.



Better Winner-take-all

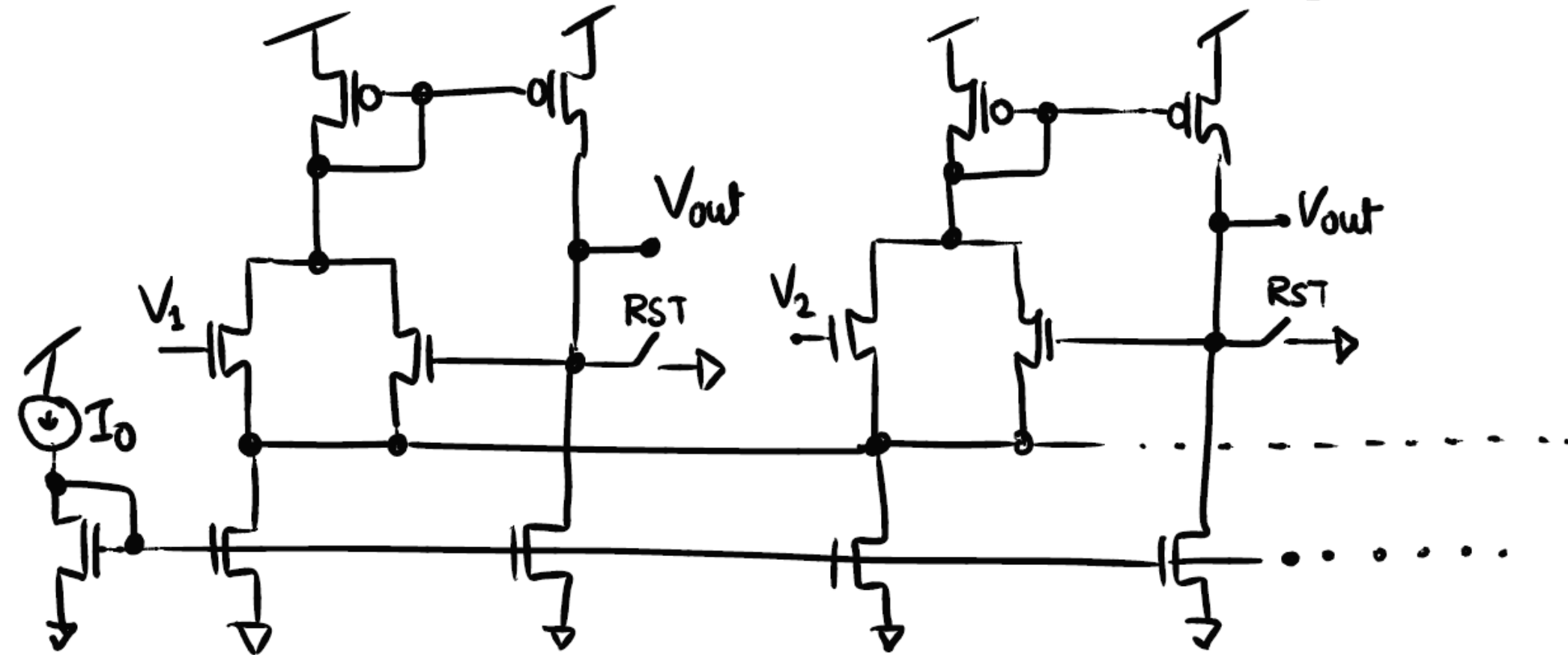


- Implements a parallel search – speed limited by the system time-constant.

Translinear principle

- Applies to circuit elements with a diode type behavior
 
$$I_k \approx I_S \exp\left(\frac{V_k}{U_T}\right)$$



$$V_1 + V_3 = V_2 + V_4$$

$$\exp\left(\frac{V_1 + V_3}{U_T}\right) = \exp\left(\frac{V_2 + V_4}{U_T}\right)$$


$$\exp\left(\frac{V_1}{U_T}\right) \exp\left(\frac{V_3}{U_T}\right) = \exp\left(\frac{V_2}{U_T}\right) \exp\left(\frac{V_4}{U_T}\right)$$

$$I_1 I_3 = I_2 I_4$$

MOSFET Translinear principle

- Drain current and gate-to-source voltage have a translinear relationship.

 
$$I_d \approx I_s \exp\left(\frac{V_{GS}}{U_T}\right)$$



$$I_1 I_2 = I_3 I_{out}$$

$$I_{out} = \frac{I_1 I_2}{I_3}$$


Squaring circuit

 

$$I_{in} I_{in} = I_B I_{out}$$


$$I_{out} = \frac{I_{in}^2}{I_B}$$

Yet another analog search engine ...

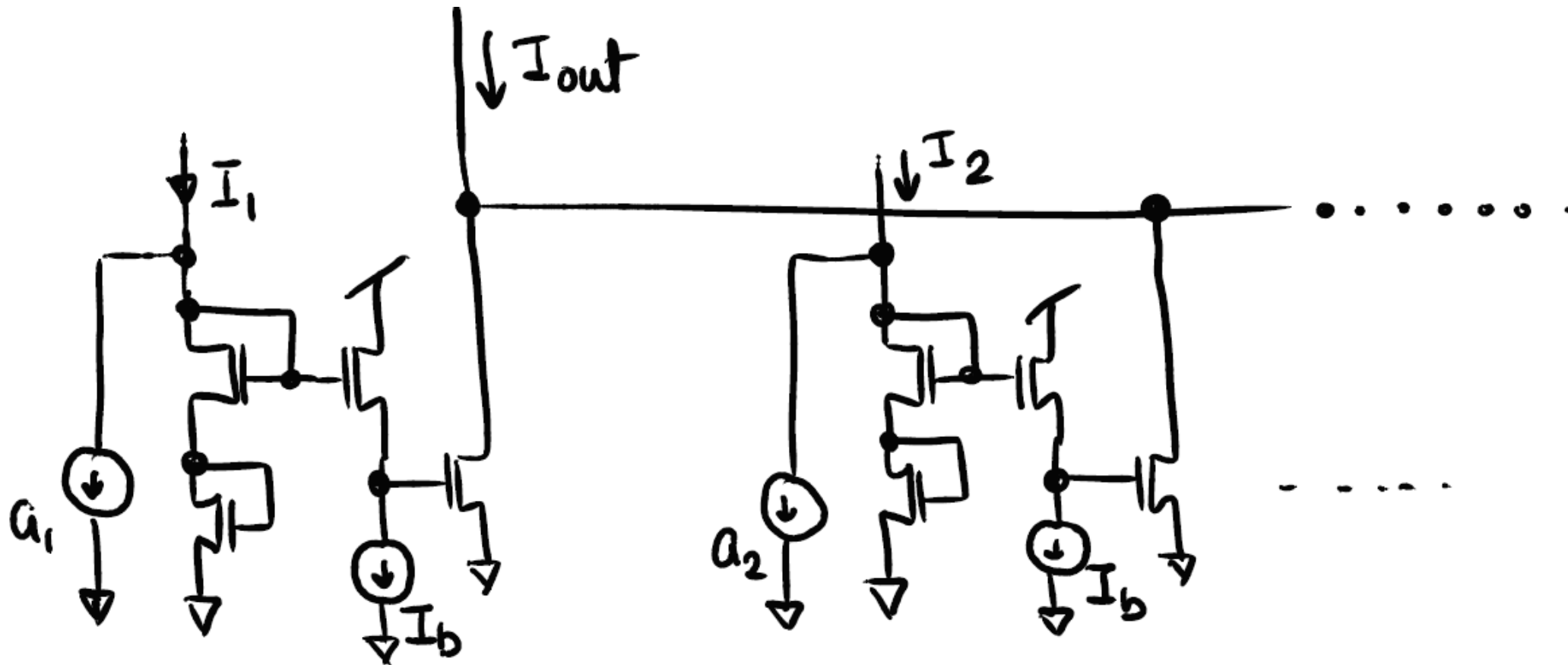


pMOS translinear circuits

- What about this circuit ?

 

Floating-gate translinear circuits

- Gate of the transistor – floating.

 


- Multiple inputs capacitively couple to the gate.

$$I_d \approx I_s \exp\left(\kappa \frac{V_1 + V_2 + V_3}{U_T}\right) \exp\left(\frac{-V_s}{U_T}\right)$$

- The charge on the floating-gate needs to be zeroed post fabrication.

 What function does this circuit implement ?




Stochastic analog computing




- Value encoded as Bernoulli probabilities.
- $0.2 = \{0\ 0\ 0\ 1\ 1\ 0\ 0\ 0\ 0\ 0\ \dots\}$ or $\{0\ 1\ 0\ 0\ 0\ 1\ 0\ 0\ 0\ 0\ \dots\}$


- Addition

 

- Matching

 

- Multiplication

 

- Division

